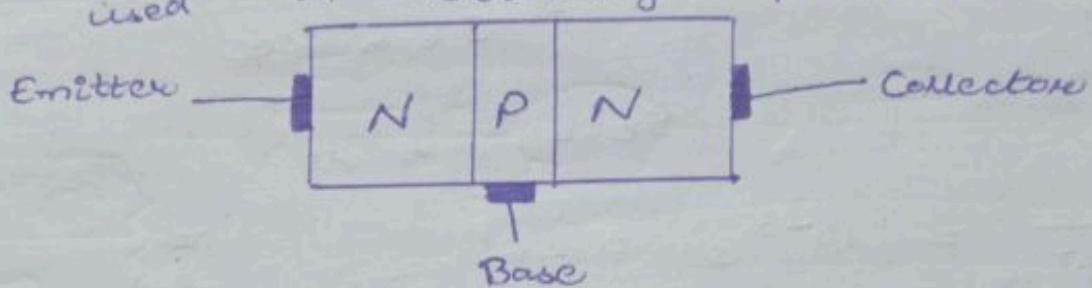


Bipolar

Junction

Transistor


* Used in amplification of weak signals and switching operations.



Emitter → Heavily Doped

Base → Lightly Doped.

Collector → Moderately Doped.

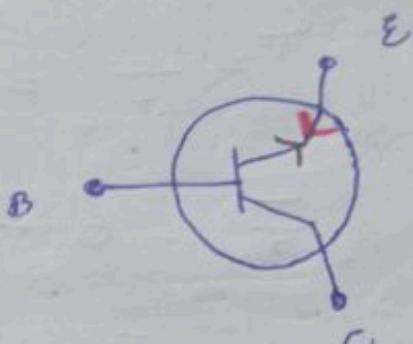

npn
pnp

Width

Collector > Emitter > Base.

Advantages of BJT

- (i) Low operating voltage.
- (ii) Higher efficiency.
- (iii) Small size and ruggedness.
- (iv) Does not require any filament power.

$$\text{Transistor} = \text{Transfer} + \text{Resistor}$$

Active mode

$$J_1 \rightarrow F \cdot B \cdot R_{\text{est}} = 0$$

$$J_2 \rightarrow R \cdot B \cdot R_{\text{est}} = \infty$$

Bipolar → Involves holes and e^-


Regions of operations.

J_1	J_2	Region of operation.
F.B.	R.B.	Active \rightarrow Amplifier
F.B.	F.B.	Saturation \rightarrow "ON"
R.B.	R.B.	Cutoff \rightarrow OFF
R.B.	F.B.	Inverted \rightarrow rarely used Emitter & collector switch their roles.

Transistor Operation

n-p-n transistor

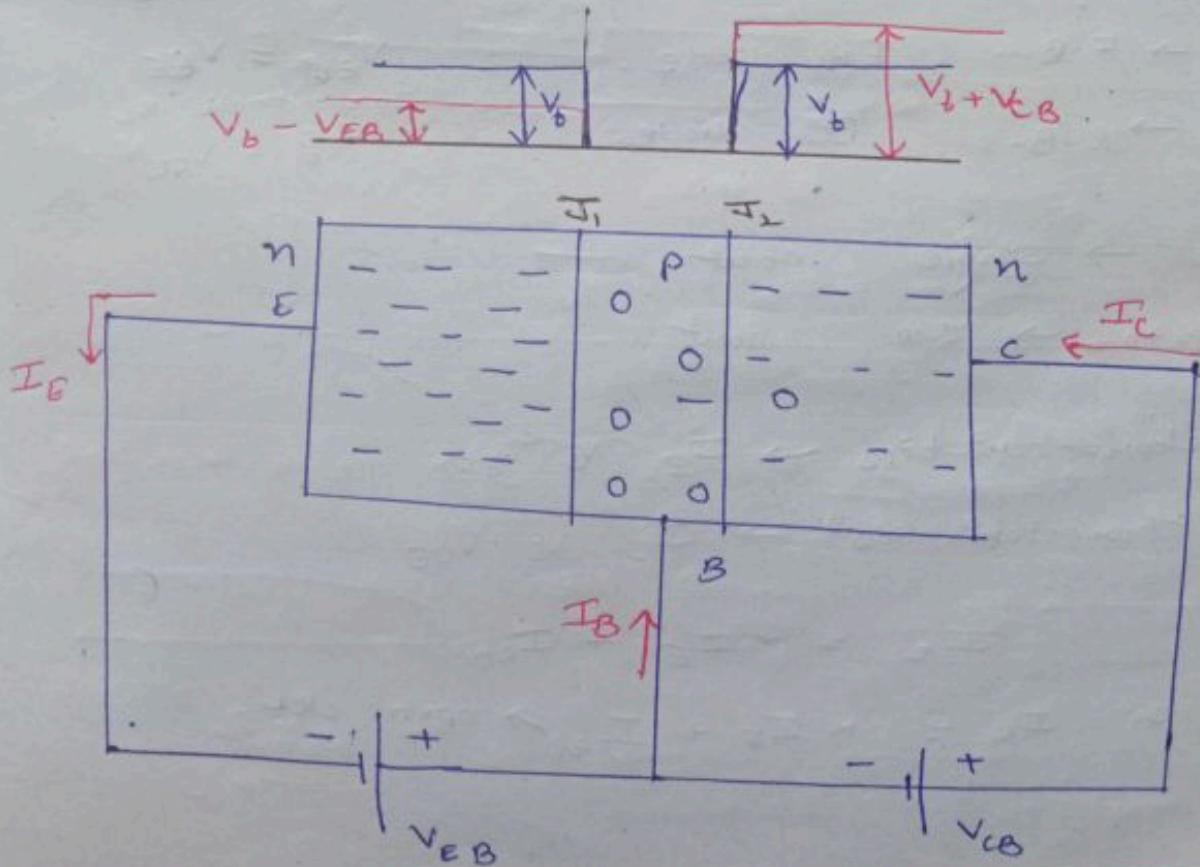- * Only 2% to 5% e⁻ combine with base holes.
- * 85% - 98% enter into collector.
- ..




$I_{CO} \rightarrow$ reverse saturation current
or leakage current.

Measure it when emitter terminal is open circuit.
 I_{CO} Due to minority charge carriers

$$I_C = \alpha I_E + I_{CO}$$

$$I_E = I_B + I_C$$

Common Base Configuration of Transistor

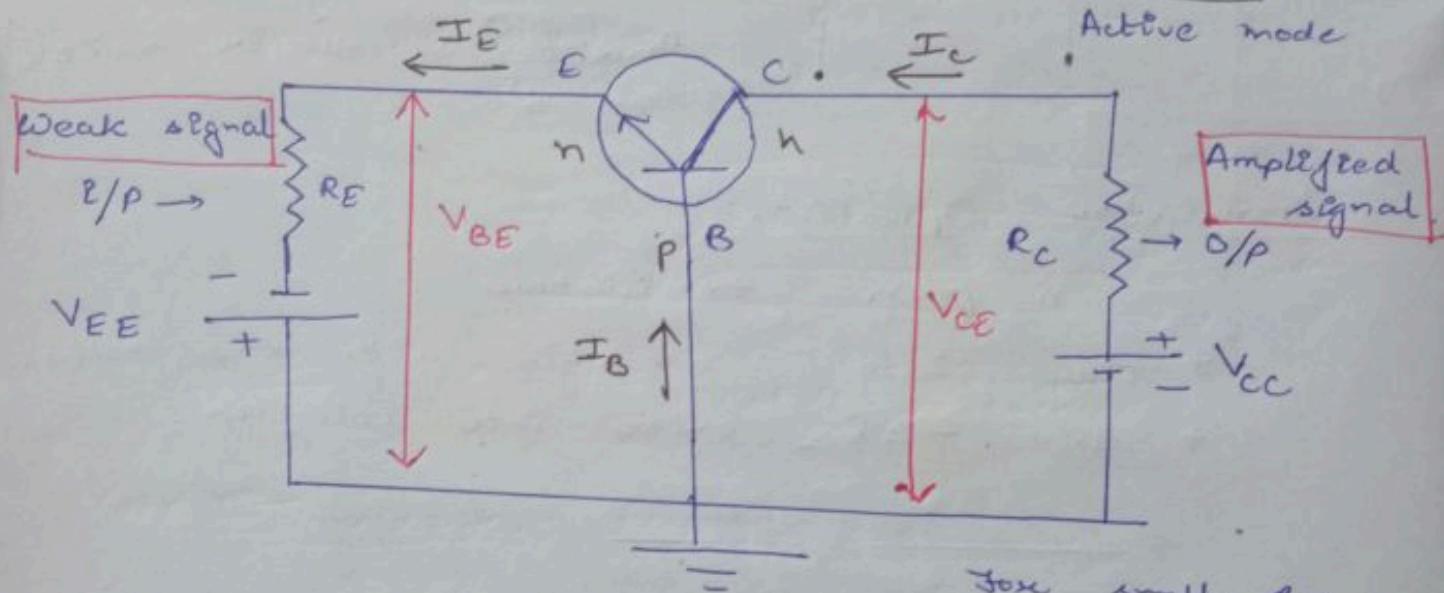

For small R_E

$J_1 \rightarrow$ F.B. EB diode.

$J_2 \rightarrow$ R.B. BC diode.

$V_{BE} = V_{GE}$
For small R_C
 $V_{CE} = V_{CC}$

Diode \rightarrow single port

Transistor \rightarrow two port

I/P characteristics $\rightarrow I_E$ vs V_{BE}

O/P characteristics $\rightarrow I_C$ vs V_{CE}

$$I_C = \alpha I_E + I_{CO}$$

$$\text{or } I_C = \alpha I_E + I_{CBO} \rightarrow \text{open circuit.}$$

$$I_E \gg I_{CBO}$$

$$I_C = \alpha I_E$$

$$\lambda = \frac{I_C}{I_E}$$

$\lambda \rightarrow$ common base current gain / amplification factor


$$\lambda = \frac{\text{O/P current}}{\text{I/P current}}$$

λ ranges from 0.95 to 0.98.

$$[I_B = (1-\alpha) I_E]$$

Input Characteristics

Characteristics of F.B. diode.

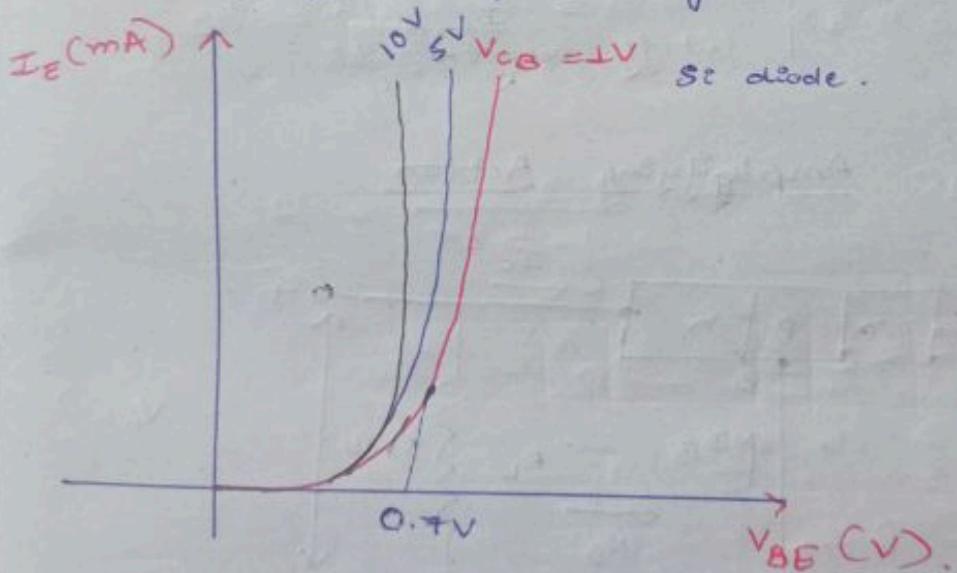

Early Effect or Base width modulation:

As $V_{CB} \uparrow$ depletion layer around CB will increase
As width of base excluding depletion layer decreases, I_E will increase because of low
combination in base holes.


Conc. grad: \uparrow

$I_E: \uparrow$



Output Characteristics \rightarrow r.b. diode
 O/P I (I_C) vs O/P V (V_{CB}) for various
 levels of E/P I (I_E).

$$I_C = \alpha I_E + I_{CBO} \text{ (Independent of } V_{CB})$$


$$I_C \approx \alpha I_E$$

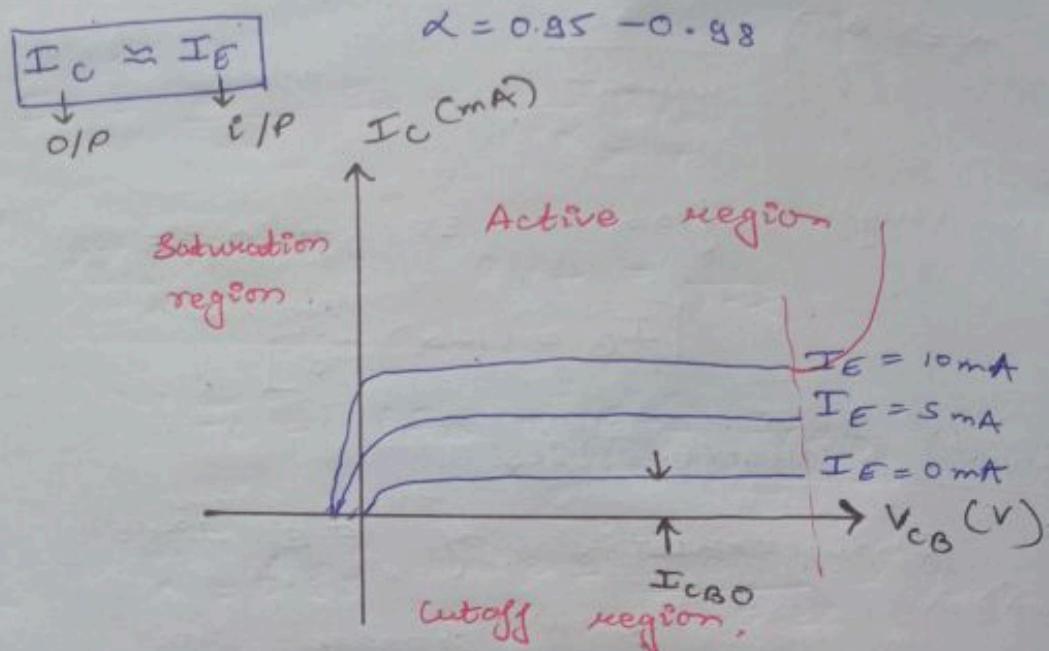

Transistor Amplifying Action

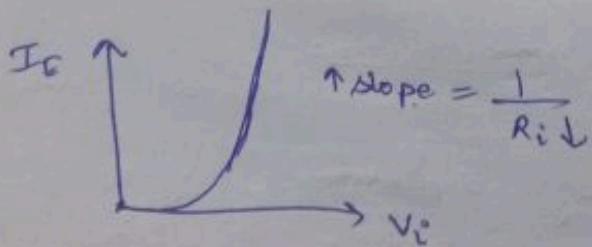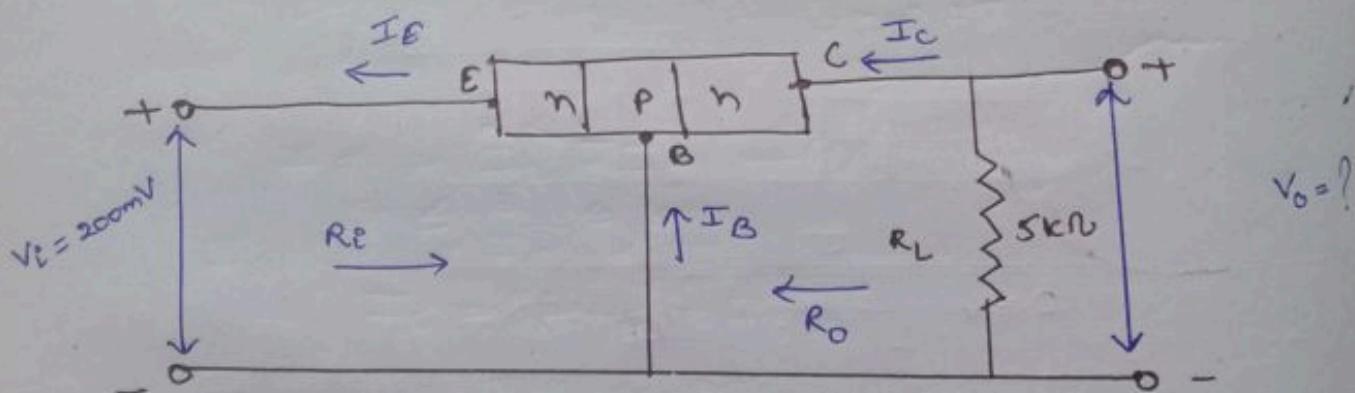

$$R_i = 20\text{ }\Omega$$

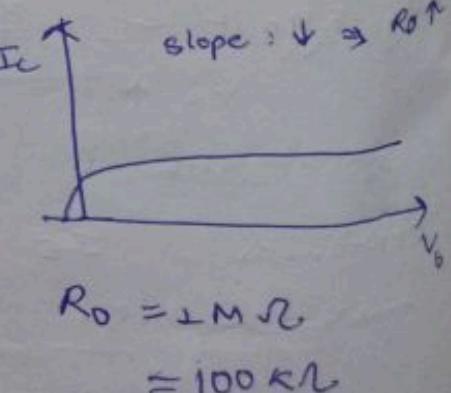

$$R_o = 1M\Omega$$

$$\approx 100\text{ k}\Omega$$

$$V_i = I_i R_i = I_E R_i$$

$$I_E = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C \approx \alpha I_E$$

$$I_C \approx I_E \quad I_C = 10 \text{ mA}$$

$$V_o = I_C R_L = 10 \text{ mA} \times (5 \text{ k}\Omega) \\ = 50 \text{ V}$$

Voltage Amplification


$$A_V = \frac{V_o}{V_i} = \frac{50 \text{ V}}{200 \text{ mV}} = 250$$

Current Amplification $\ll 1$.

$$\frac{I_C}{I_E} = \frac{\alpha I_E}{I_E} = \alpha$$

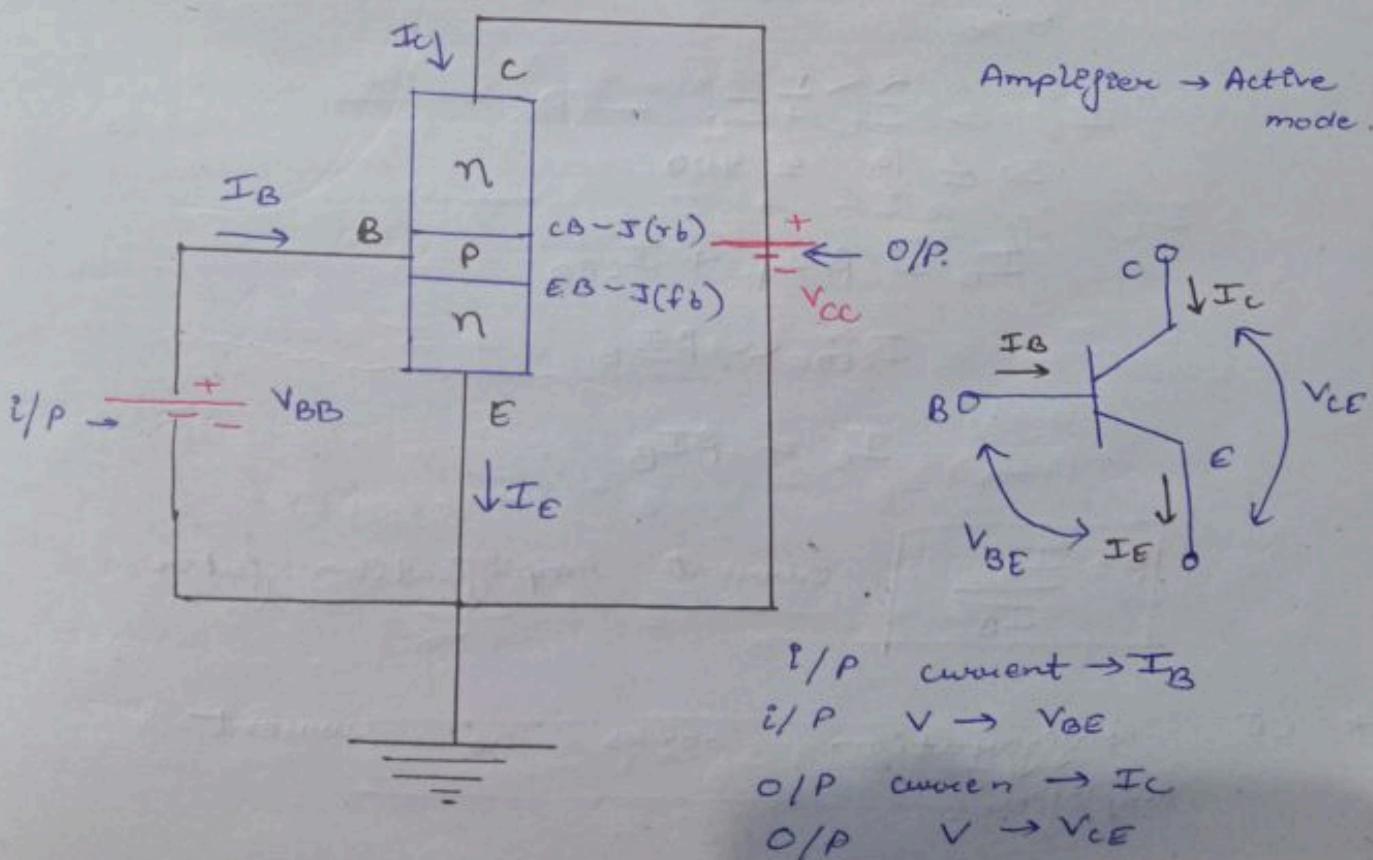0.95 to 0.99

Common Emitter Configuration Of Transistor



$$I_E = I_C + I_B \quad \text{--- (1)}$$

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (2)}$$

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$(1-\alpha) I_C = \alpha I_B + I_{CBO}$$

$$I_C = \left(\frac{\alpha}{1-\alpha} \right) I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\beta + 1 = \frac{1}{1-\alpha}$$

$$I_C = \beta I_B + \underbrace{(\beta + 1) I_{CBO}}_{I_{CEO}}$$

Case I: $\alpha = 0.98$ $\beta = \frac{0.98}{1-0.98} = 49$

Case II: $\alpha = 0.95$ $\beta = \frac{0.95}{1-0.95} = 19$

$$\ll 1$$

$$50 \leq \beta \leq 400$$

$$I_C = \beta I_B + I_{CEO}$$

$$I_{CEO} \ll \beta I_B$$


$$I_C = \beta I_B$$

$$\boxed{\beta = \frac{I_C}{I_B}}$$


current Amplification factor

* CE configuration works as current amplifier.


Input Characteristics

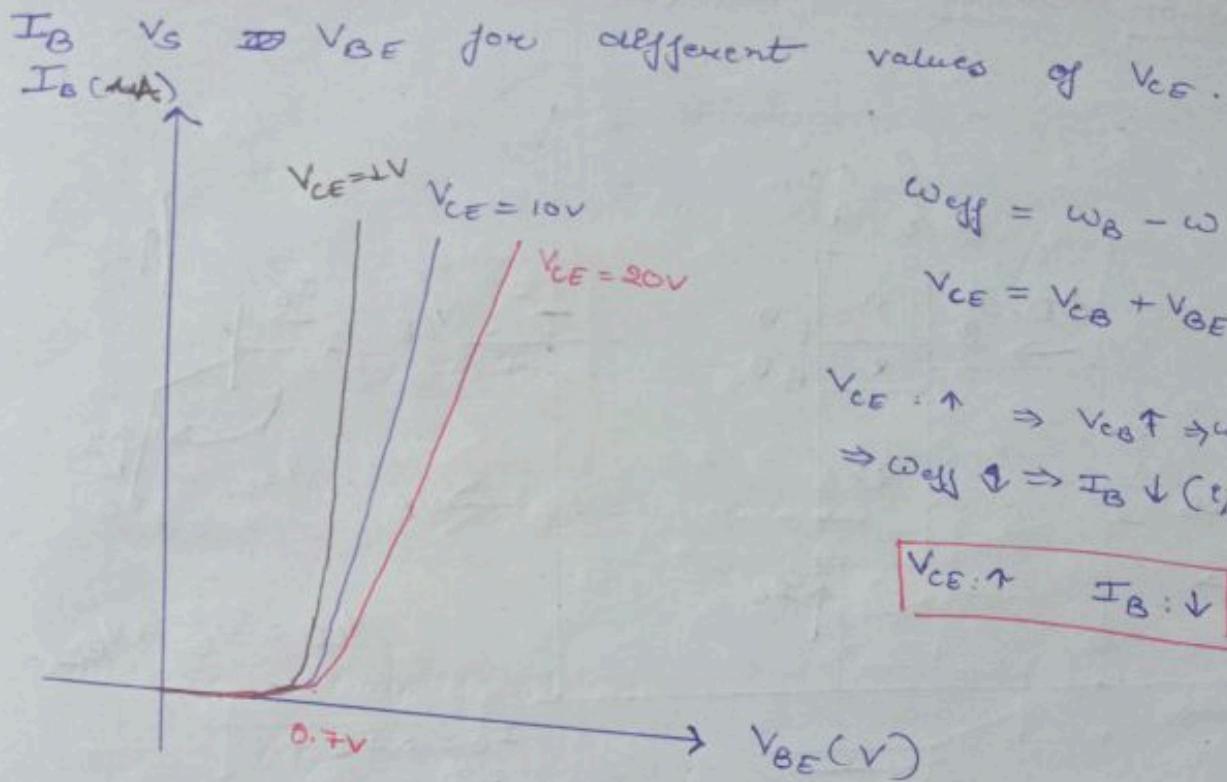

Output Characteristics.

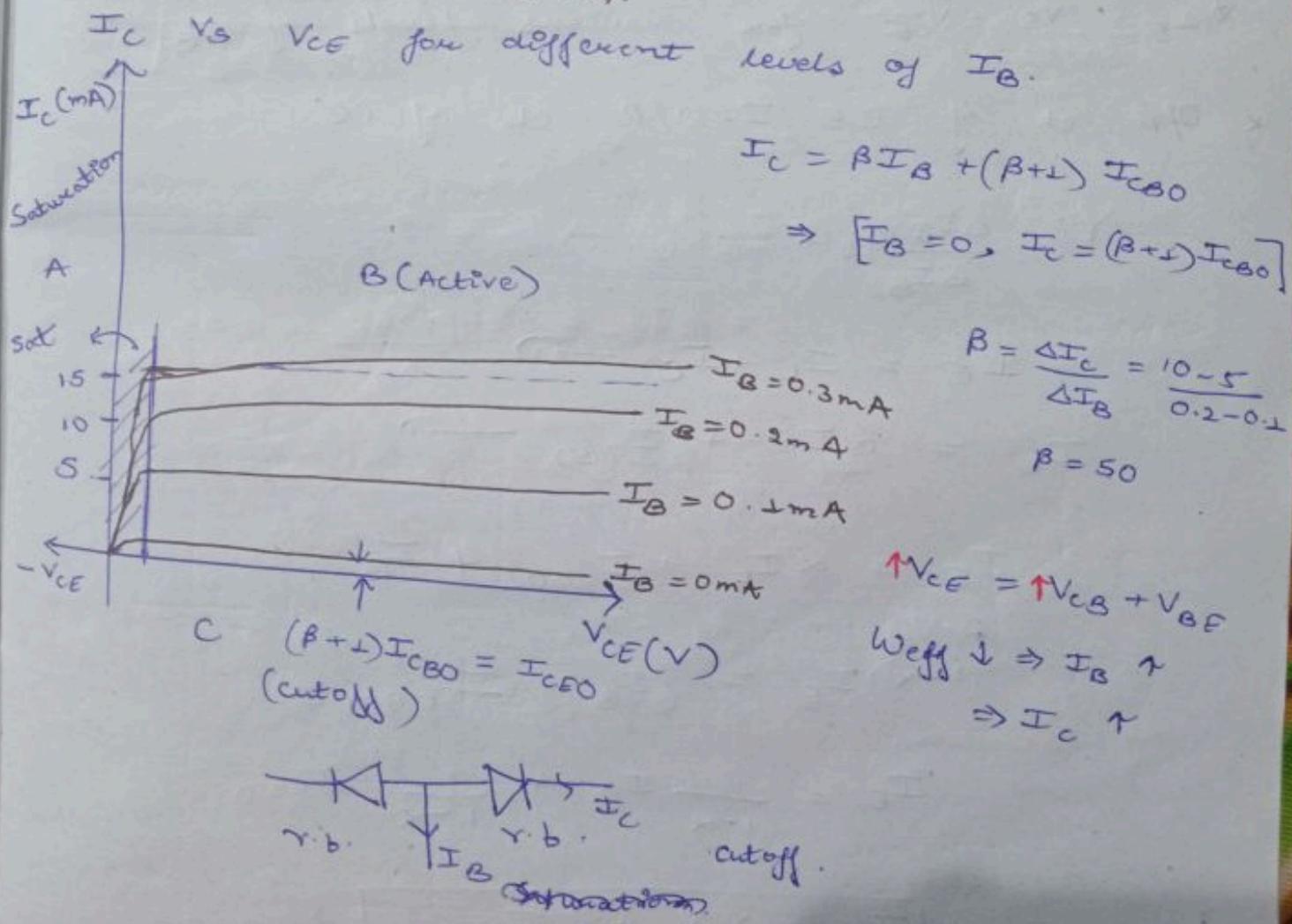

Common Collector Configuration

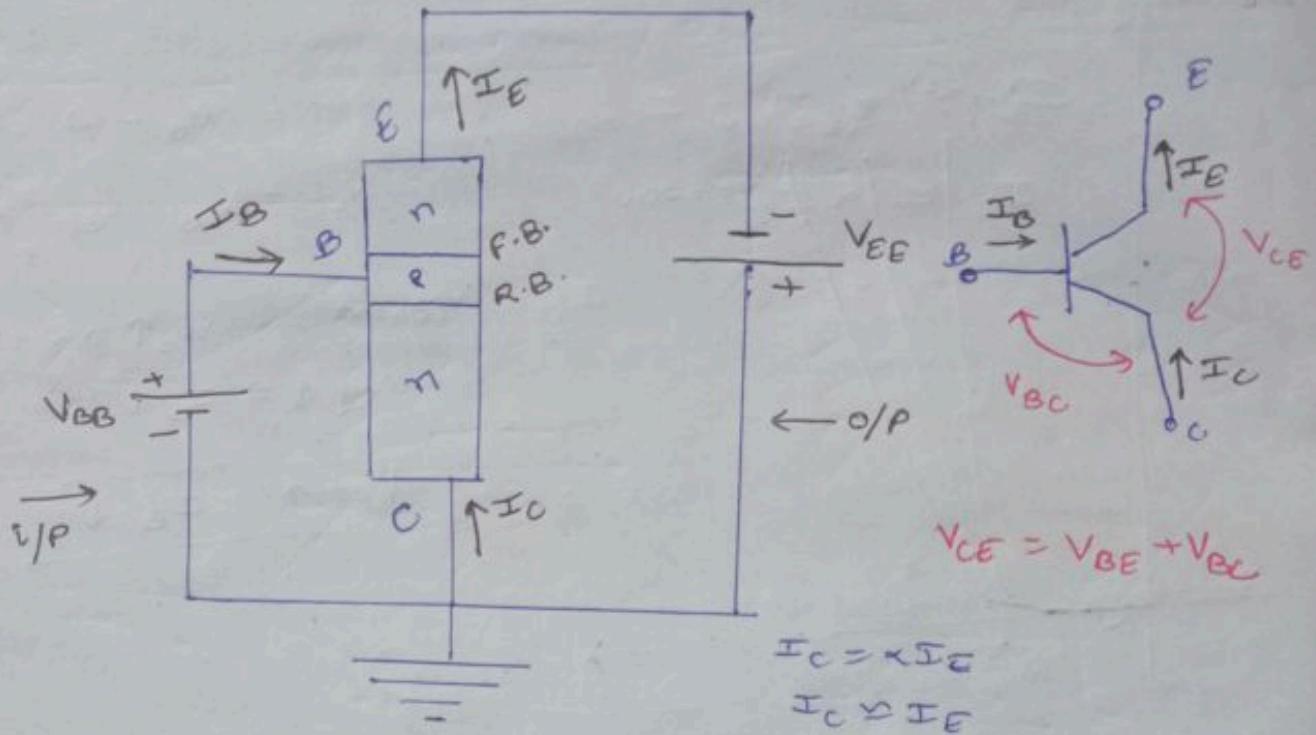

- * I_E vs V_{CE} for various levels of I_B .
- * O/P ch. of CE \equiv O/P ch. of CC

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$I_E = I_C + I_B \quad \text{--- (1)}$$

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (2)}$$

$$I_E = \alpha I_E + I_{CBO} + I_B.$$

$$(1-\alpha) I_E = I_B + I_{CBO}$$

$$I_E = \frac{1}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$I_E = \gamma I_B + \gamma I_{CBO}$

Relation between α, β, γ

$$\alpha \rightarrow \alpha_{dc} = \frac{I_C}{I_E}$$

$$\alpha \rightarrow \gamma_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CE} = \text{const}}$$

$$\beta \rightarrow \beta_{dc} = \frac{I_C}{I_B}$$

$$\beta \rightarrow \beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{const}}$$

$$\gamma \rightarrow \gamma_{dc} = \frac{I_E}{I_B}$$

$$\gamma \rightarrow \gamma_{ac} = \left. \frac{\Delta I_E}{\Delta I_B} \right|_{V_{CE} = \text{const}}$$

$$I_E = I_C + I_B$$

$$\frac{I_E}{I_B} = \frac{I_C}{I_B} + 1$$

$$\boxed{\gamma = \beta + 1}$$



$$\boxed{\beta = \frac{\alpha}{1-\alpha}}$$

$$\boxed{\gamma = \frac{1}{1-\alpha}}$$

$$\boxed{\gamma = \beta + 1 = \frac{1}{1-\alpha}}$$

DC Biasing of Transistors

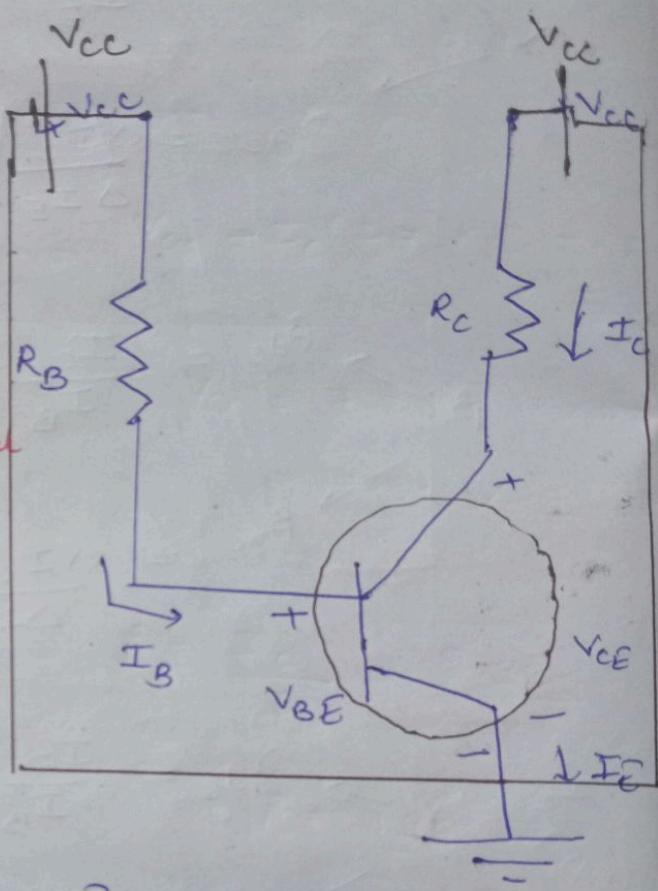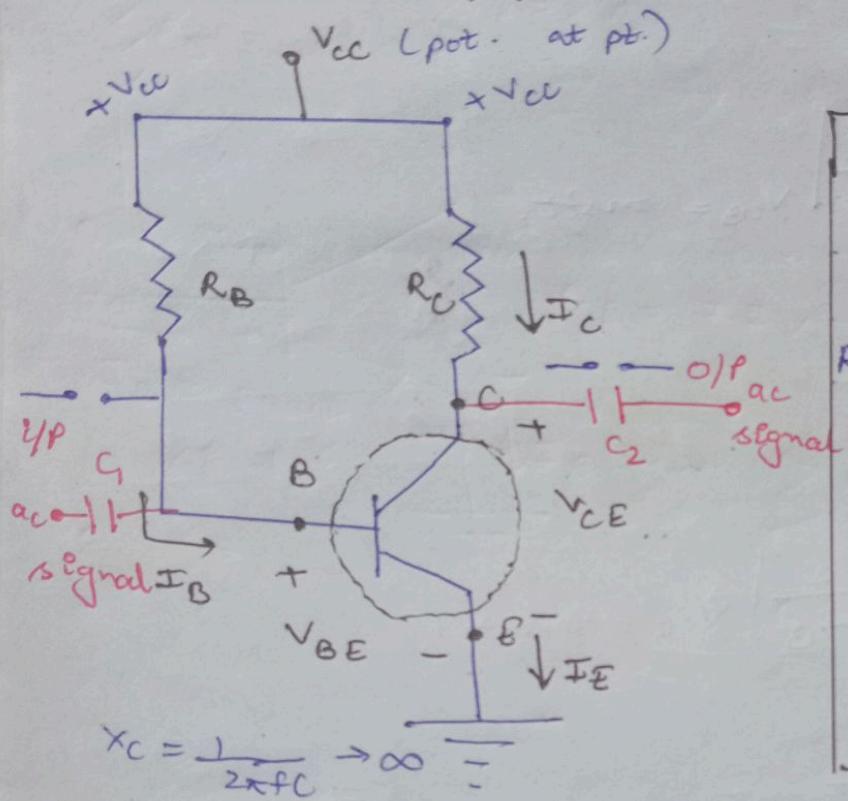Fined Bias Configuration / Base bias configuration



$$I_C = ? \quad V_{CE} = ?$$

$$+V_{CC} - I_B R_B - V_{BE} = 0.$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$


0.3V Ge
0.7V Si

$$I_C = \beta I_B = \frac{\beta (V_{CC} - V_{BE})}{R_B}$$

$$+V_{CC} - I_C R_C - V_{CE} = 0.$$

$$\therefore V_{CE} = V_{CC} - I_C R_C$$

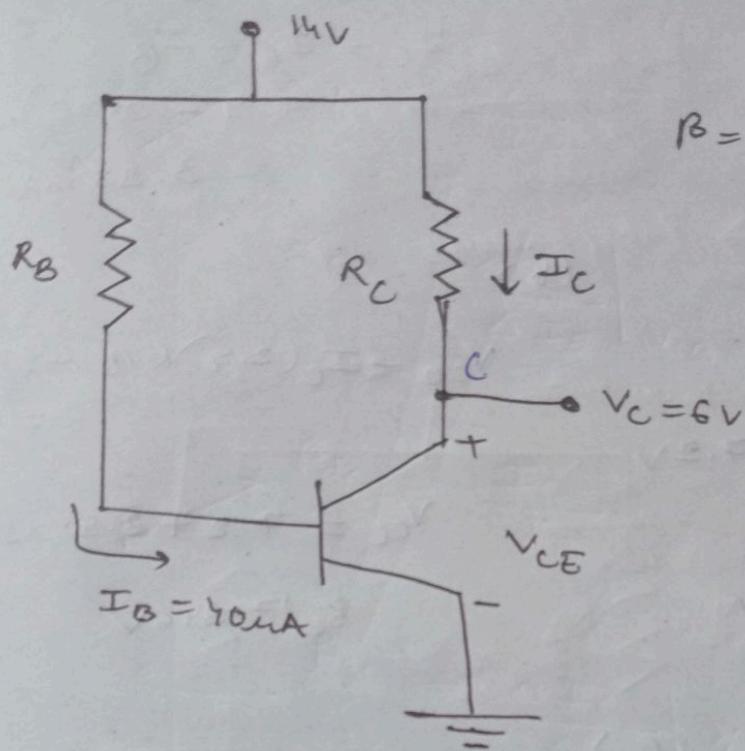Q \Rightarrow (a) I_C , (b) R_C (c) R_B (d) V_{CE} .



$$\beta = 80$$

$$V_{CC} = 14V$$

$$I_B = 40 \mu A$$

$$V_C = 6V$$

$$(a) I_C = \beta I_B$$

$$I_C = 80 \times 40 \times 10^{-6} A \\ = 3.2 mA$$

$$(b) 14V - I_C R_C = 6V$$

$$R_C I_C = 8V$$

$$R_C = \frac{8}{3.2 \times 10^{-3}} \\ = 2.5 k\Omega$$

$$(c) 14 - I_B R_B - V_{BE} = 0.$$

$$R_B = \frac{14V - V_{BE}}{I_B} \\ = \frac{14 - 0.7}{40 \mu A}$$

$$R_B = 332.5 k\Omega$$

$$(d) V_{CE} = V_C - V_E$$


$$= 6 - 0 = 6V$$

Q \Rightarrow (a) I_C

(b) V_{CC}

(c) β

(d) R_B .

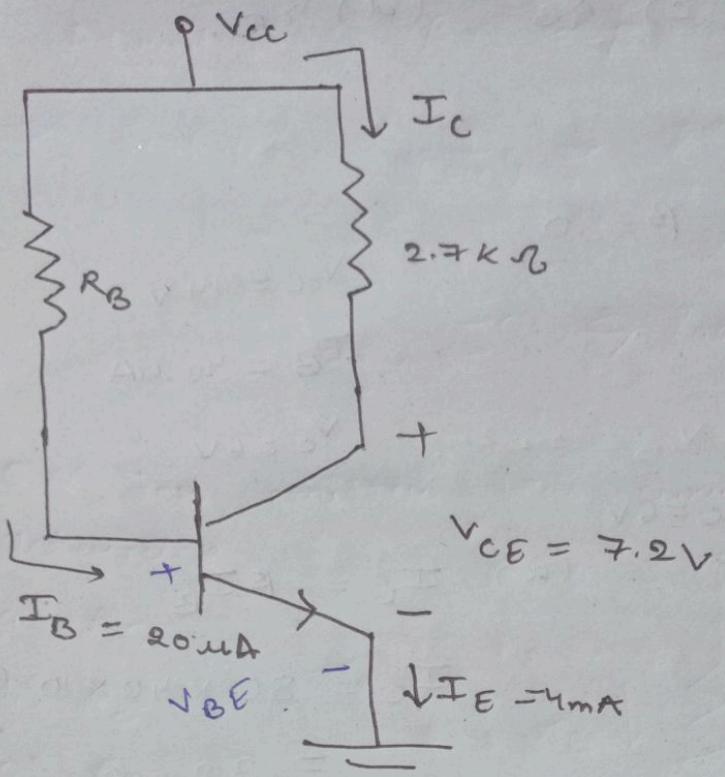

$$(a) I_E = I_C + I_B$$

$$I_C = I_E - I_B$$

$$= (4 - 0.02) \text{ mA} \\ = 3.98 \text{ mA}$$

(b)

$$V_{CC} - I_C(2.7) \text{ kΩ} - 7.2 \\ = 0$$

$$V_{CC} = 7.2 + 3.98 \times 2.7 \\ = 17.946 \text{ V}$$

(c)

$$\beta = \frac{I_C}{I_B} = \frac{3.98 \text{ mA}}{0.02 \text{ mA}}$$

$$\beta = 199$$

(d)

$$V_{CC} - I_B R_B - V_{BE}^{0.7} = 0.$$

$$17.94 \text{ V} - (20 \mu\text{A}) R_B - 0.7 \text{ V} = 0$$

$$R_B = 862.3 \text{ kΩ}$$

Emitter Bias Configuration

R_E is introduced to improve stability of operating point or Q-point (I_{CQ} , V_{CEQ})

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0 \text{ V}$$

$$I_E = I_C + I_B = \beta I_B + I_B$$


$$I_E = (\beta + 1) I_B$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$V_{CC} - I_B (R_B + (\beta + 1) R_E) - V_{BE} = 0$$

$$\left[I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} \right]$$

$$\left[I_C = \beta I_B \right]$$

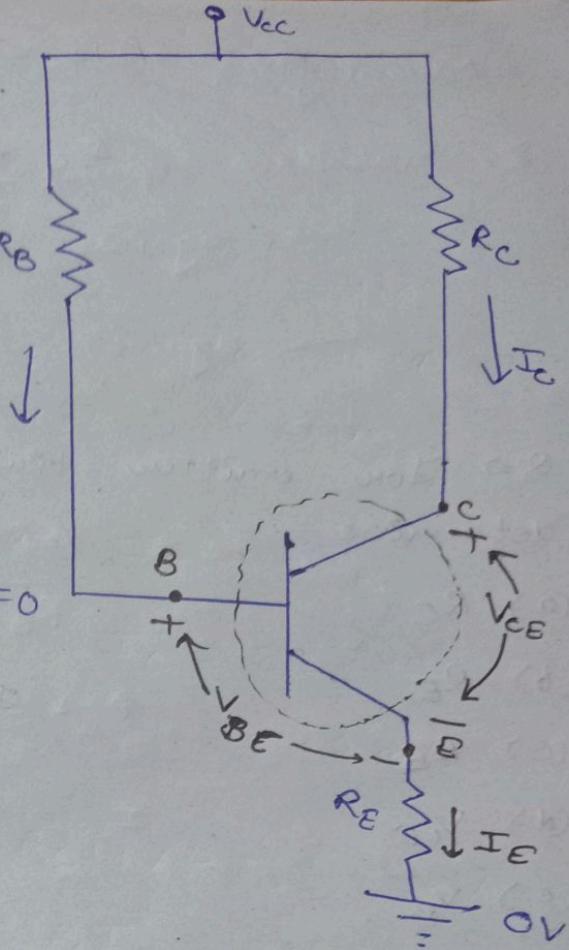

$$I_E \approx I_C$$

$$V_{CC} - R_C I_C - V_{CE} - I_E R_E = 0.$$

$$V_{CC} - I_C (R_C + R_E) - V_{CE} = 0.$$

$$\left[V_{CE} = V_{CC} - (R_C + R_E) I_C \right]$$

Advantages of using R_E .

$$I_C \Rightarrow Q-\text{pt}$$

(i) $T_e \uparrow \Rightarrow I_C: \uparrow \{ I_C = \beta I_B + (\beta + 1) I_{CBO} \uparrow \}$

$$\frac{I_E R_E}{\text{DROP}} \uparrow \Rightarrow I_B: \downarrow \Rightarrow I_C: \downarrow$$

Because of introduction of R_E temp^o will no longer effect on I_C .

$$(ii) \quad I_C = \beta I_B \quad \text{Ans}$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B + (\beta + 1) R_E}$$

$$\beta_{+1} \approx \beta \quad \beta R_E \gg R_B$$

$$I_C = \frac{\beta(V_{CC} - V_{BE})}{\beta R_E}$$

$I_C \Rightarrow$ independent of β .

Q \Rightarrow For emitter bias current, determine.

- (a) R_C
- (b) R_E
- (c) R_B
- (d) V_{CE}
- (e) V_B

$$V_C = 7.6V$$

$$V_E = 2.4V$$

$$(e) \quad V_{BE} = 0.7V$$

$$V_B - V_E = 0.7$$

$$V_B = 0.7 + 2.4 = 3.1V$$

$$(d) \quad V_{CE} = V_C - V_E = 7.6 - 2.4 \\ = 5.2V$$

$$(c) \quad 12V - I_B R_B = 3.1V$$

$$R_B = \frac{12 - 3.1}{I_B}$$

$$I_B$$

$$I_B = \frac{I_C}{\beta} \\ = \frac{3mA}{80} \\ I_B = 37.5 \mu A$$

$$R_B = 237.4 \text{ k}\Omega$$

(b) R_E

$$2.4 - I_E R_E = 0$$

$$R_E = \frac{2.4}{3 \text{ mA}} = 0.8 \text{ k}\Omega$$

(a) R_C

$$12 - R_C I_C = 7.6$$

$$R_C = \frac{4.4}{3 \text{ mA}} = 1.47 \text{ k}\Omega$$

Collector Feedback Biasing

$$I = I_C + I_B$$

$$\beta I_B$$


$$V_{CC} - (I_C + I_B) R_B - I_B R_B - V_{BE} = 0$$

$$I_C = \beta I_B$$

$$V_{CC} - [(\beta + 1) R_C + R_B] I_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + R_B}$$
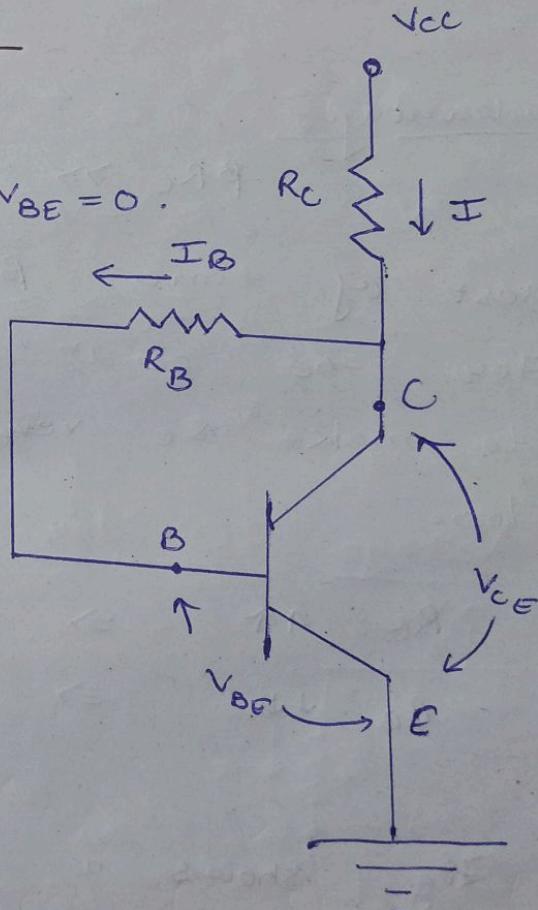
$$I_C = \beta I_B = \frac{\beta (V_{CC} - V_{BE})}{(\beta + 1) R_C + R_B}$$



$$V_{CC} - I_R C - V_{CE} = 0$$

$$V_{CC} - (I_C + I_B) R_C - V_{CE} = 0$$

$$[V_{CE} = V_{CC} - (I_C + I_B) R_C]$$

Advantages :

(D) Stabilizes operating point ($I_C - \rho t$)

↳ against the variation of temp.

↳ against the " " " V_{CC} (Biasing V_{cc})

↳ " " " " " β values.

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B + (\beta + 1) R_C}$$

$$\beta + 1 \approx \beta \quad \beta R_C \gg R_B$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C}$$

Disadvantages

$$\beta R_C \gg R_B$$

most of time β is unknown.

For the cond'n to satisfy, we have
to make R_C very large or R_B very
large.

$$R_C : \uparrow \uparrow \Rightarrow V_C : \uparrow \uparrow \text{ cost } \uparrow$$

$$R_B \downarrow \downarrow \Rightarrow R.B. \text{ of Collector Base } \downarrow \downarrow$$

\Rightarrow Fig shows a silicon transistor biased
by collector feedback method. Determine the
operating point. $\beta = 100$

$$V_{CC} = 20V$$

$$\beta = 100$$

$$R_C = 1k\Omega$$


$$R_B = 100k\Omega$$

$Q - pt \equiv (I_C, V_{CE})$

$$\beta I_B$$

$$V_{CC} - (I_C + I_B) (1k\Omega)$$

$$- I_B (100k\Omega) - 0.7V = 0$$

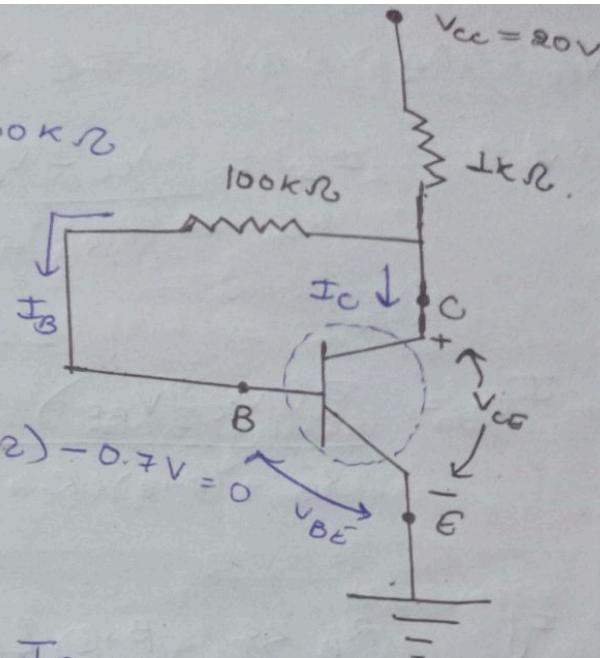

$$\frac{V_{CC} - 0.7}{(\beta + 1)(1k\Omega) + 100k\Omega} = I_B$$

$$I_B = \frac{20 - 0.7V}{201k\Omega} = 0.096mA$$

$$= 96mA$$

$$I_C = \beta I_B = 9.6mA$$

$$V_{CC} - (I_C + I_B) 2k\Omega - V_{CE} = 0$$

$$V_{CE} = 10.304V$$

$$Q - pt = (9.6mA, 10.304V)$$

Collector Feedback Biasing with Emitter Resistance


$$V_{CC} - I R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I = I_C + I_B$$

$$V_{CC} - (I_C + I_B) R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = I_C + I_B = \beta I_B + I_B$$

$$= (\beta + 1) I_B$$

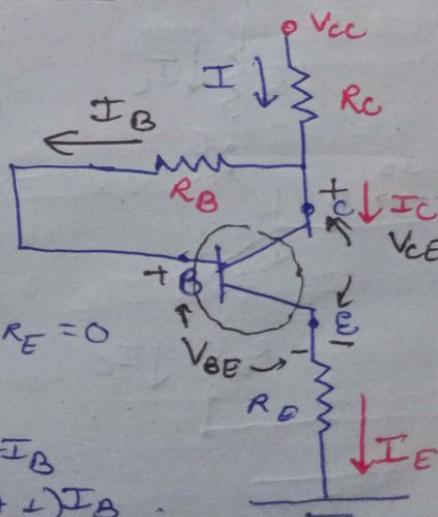

$$V_{CC} - (\beta + 1) I_B R_C - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(R_C + R_E)}$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B + (\beta + 1)(R_C + R_E)} = \beta I_B$$

If $R_B \ll (\beta + 1)(R_C + R_E)$

I_C will be independent of β .


KVL in O/P loop


$$V_{CC} - (I_C + I_B) R_C - V_{CE} - I_E R_E = 0$$

$$V_{CC} - I_E R_C - V_{CE} - I_E R_E = 0$$

$$I_E \approx I_C$$

$$[V_{CE} = V_{CC} - I_C (R_C + R_E)]$$

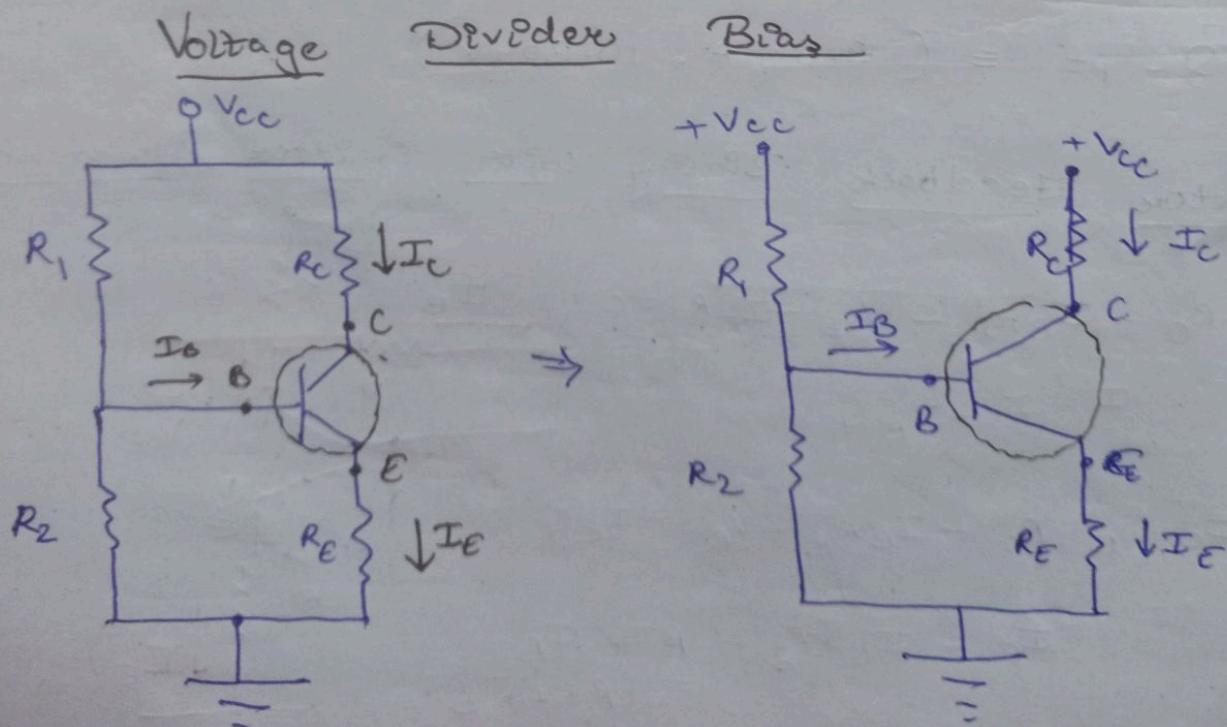

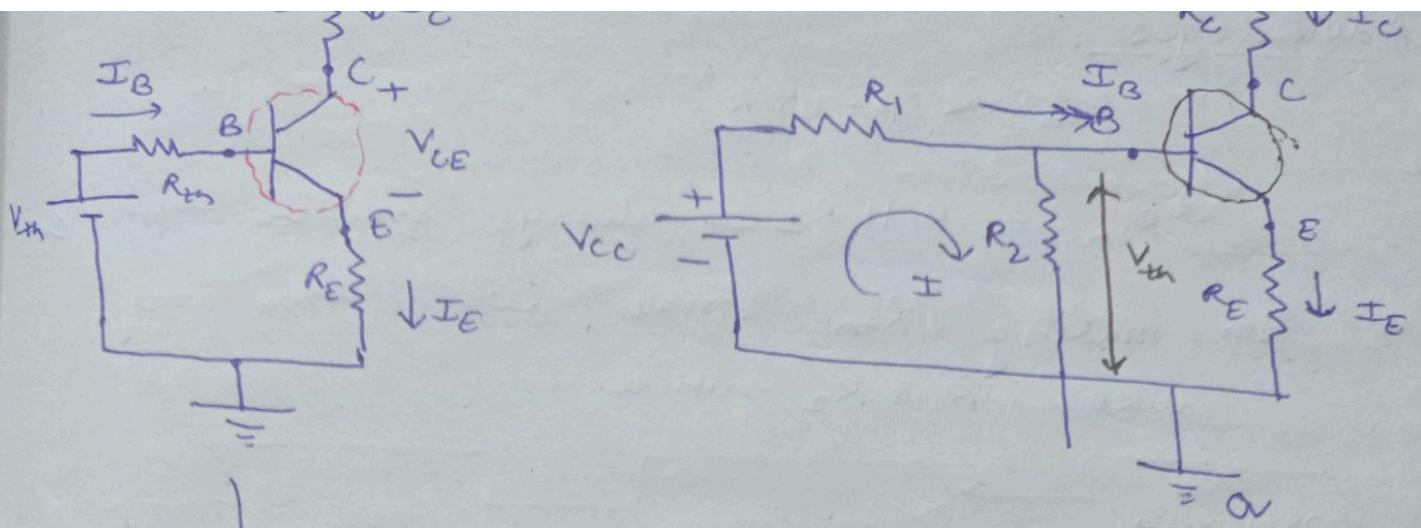


$$R_{th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{V_{cc}}{R_1 + R_2}$$

$$V_{th} = I R_2 = \frac{R_2 V_{cc}}{R_1 + R_2}$$

Emitter Bias

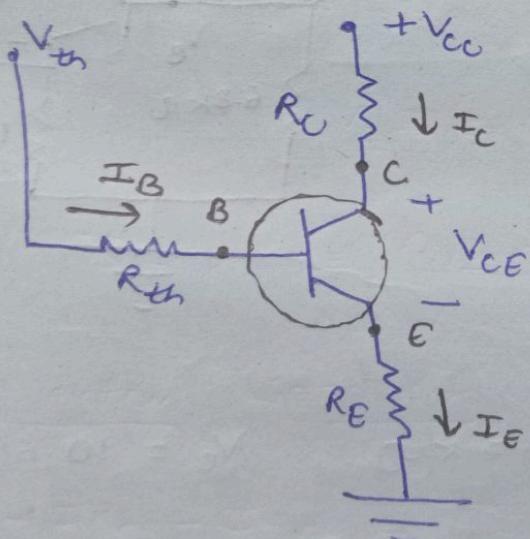

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

$$I_C = \beta I_B = \frac{\beta (V_{th} - V_{BE})}{R_{th} + (\beta + 1) R_E}$$

If $R_{th} \ll (\beta + 1) R_E \Rightarrow I_C$ independent of β .

$$V_{cc} - I_C R_L - V_{CE} - I_E R_E = 0$$

$$I_E \approx I_C$$

$$V_{CE} = V_{CC} - I_D (R_C + R_E)$$

Advantages :

$$R_{th} \ll (\beta + 1) R_E$$

$$R_{th} = R_1 \parallel R_2 \rightarrow \text{always smaller than } R_1 \text{ & } R_2$$

For making R_{th} small we have to take R_1 & R_2 small.

Whereas

$$R_B \ll (\beta + 1) R_E$$




It is single resistance.

$R_B \rightarrow$ very small.

Q → For the voltage divider bias configuration, determine

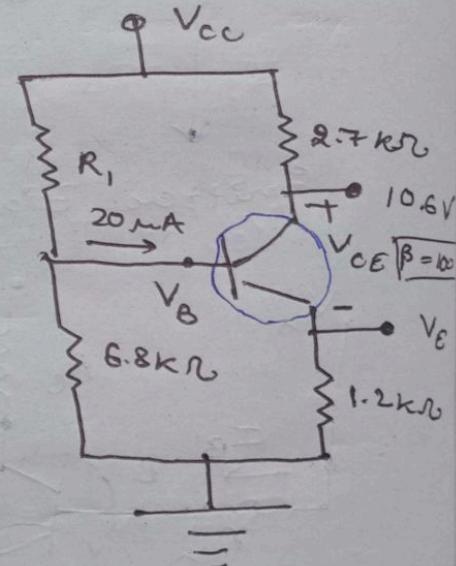- (a) I_C
- (b) V_E
- (c) V_{CC}
- (d) V_{CE}
- (e) V_B
- (f) R_1



$$I_B = 20 \mu A$$

$$R_C = 2.7 k\Omega \quad V_C = 10.6 V$$

$$\beta = 100$$

$$R_2 = 6.8 k\Omega$$

$$R_E = 1.2 k\Omega$$

$$(a) \quad I_C = \beta I_B = 100 \times 20 \times 10^{-6} A \\ = 2 mA$$


$$V_{CC} - I_C (2.7k\Omega) = 10.6V$$

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_m = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{CC} = (2mA)(2.7k\Omega) + 10.6V$$

$$V_{CC} = 16V$$

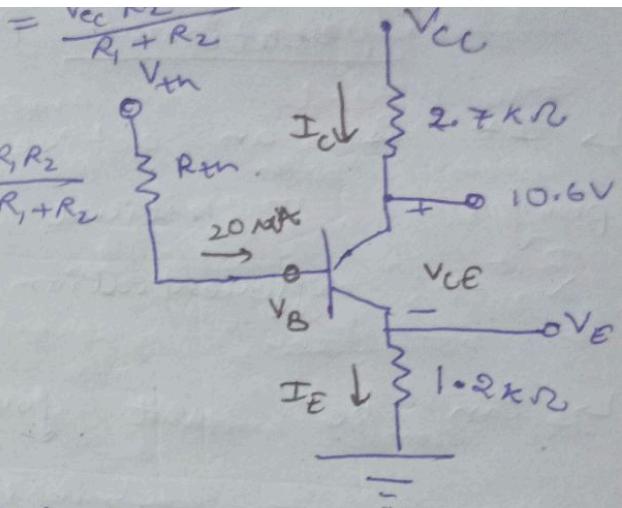

(b)

$$V_E$$

$$I_E = I_C + I_B = 2mA + 20\mu A$$

$$\checkmark I_E \approx I_C \quad \textcircled{1}$$

$$I_E \approx 2mA$$

$$d_{off} = 0.02 mA$$

$$V_E - (1.2k\Omega) I_E = 0.$$

$$\textcircled{1} \quad V_E = (2.02)mA (1.2k\Omega) = 2.424V$$

$$\textcircled{11} \quad V_E = 2.4V$$

$$d_{off} = 0.024V$$

$$(d) \quad V_{CE} = V_C - V_E = 10.6 - 2.424 \\ = 8.176V$$

(e) V_B

$$V_{BE} = V_B - V_E$$

$$0.7V = V_B - 2.424V$$

$$V_B = 3.124V$$

(f)


$$\stackrel{\rightarrow}{\text{pt. at point}} \\ V_{th} \approx V_B$$

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{16 \times 6.8k\Omega}{R_1 + 6.8k\Omega} = 3.124V$$


$$R_1 = 20k\Omega$$

Operational Amplifier (Op-Amp)

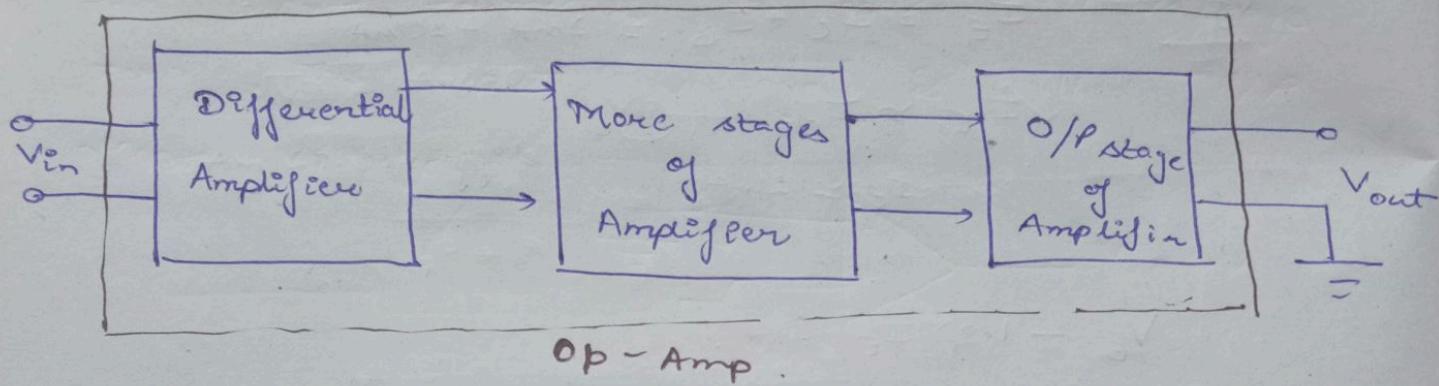
- It is an active element designed to perform mathematical operations like +, -, \times , \div , differentiation & integration.
- Can be used for AC as well as DC.



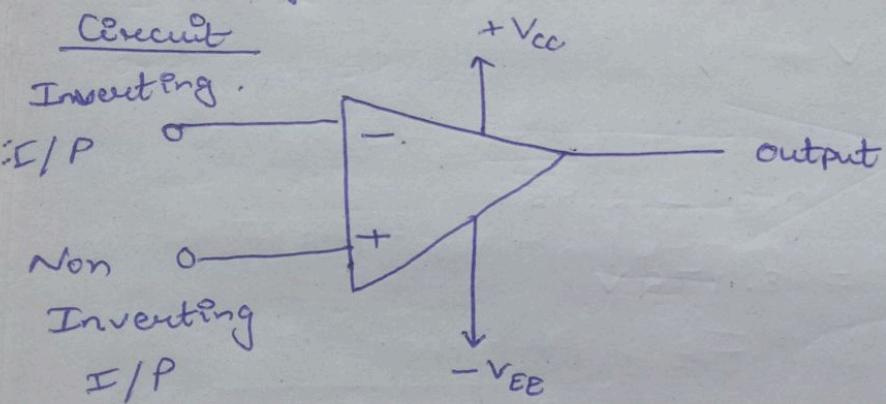- An op-Amp is a multi-stage, direct coupled amplifier.



Equivalent ckt

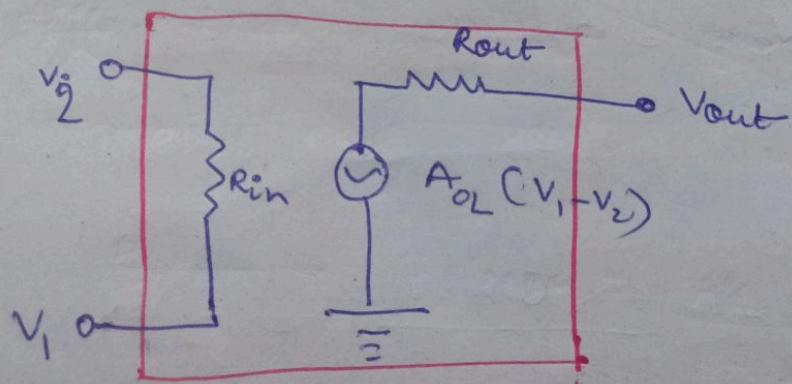


Op-Amp Characteristics

<u>Characteristics</u>	<u>Ideal Op-Amp</u>	<u>Practical OP-Amp (741)</u>
Open Loop Gain (A_{OL})	∞	10^6
Input Resistance (R_i)	∞	$1M\Omega$ to $2M\Omega$
O/P Resistance (R_o)	0	50 V_2 to 100 V_2 = 1MHz.
Open loop Bandwidth	∞	$< 10\text{ mV}$.
Offset voltage	0	
Offset current	0	10 nA
Common Mode Rejection Ratio (CMRR)	∞	90 dB
Slow Rate	∞	$1\text{ V}/\text{msec}$

Input Bias Current

$$[I_a = \frac{I_1 + I_2}{2}]$$

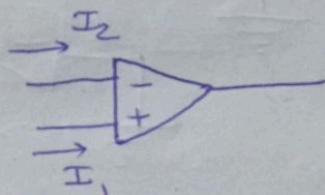

Ideally it is zero.

Practically is 100's of nA.

Input Offset current

Algebraic difference b/w the currents into inverting & non-inverting terminals.


$$I_{i_o} = |I_1 - I_2| \rightarrow \text{few nA}$$

Input offset voltage

For ideal op-amp output should be zero when both i/p are grounded.


But in practical op-amp the o/p voltage is not zero when both i/p are grounded.

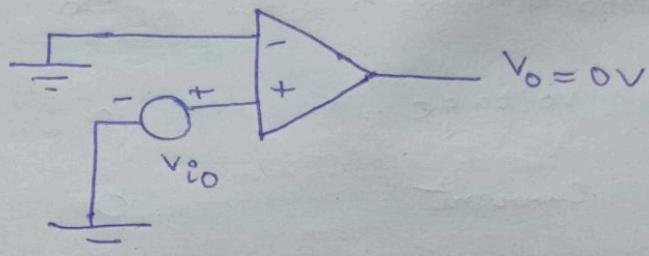A small amount of voltage is applied at the input terminals to make o/p voltage zero. This input voltage is called i/p offset voltage.



O/P offset Voltage

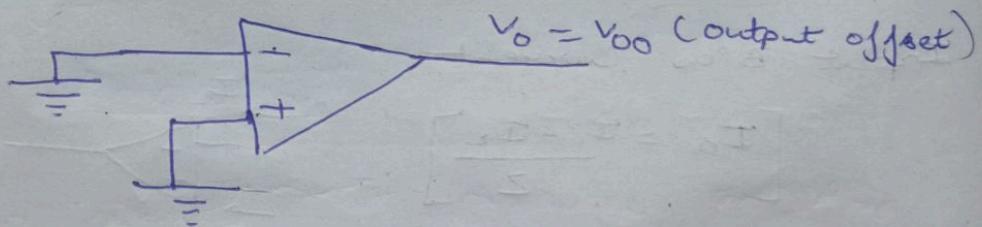It is o/p voltage of op-amp when $V_1 = 0$ and $V_2 = 0$.



Common Mode Rejection Ratio (CMRR)

It may be defined as the ratio of differential voltage gain (A_d) to the common mode gain (A_{CM}).

$$A_d = \frac{V_o}{V_1 - V_2} \Rightarrow V_d$$

$$CMRR = |A_d|$$

$$|A_{CM}| \quad CM = \frac{V_o}{V_{CM}}$$

$$V_{CM} = \frac{V_1 + V_2}{2}$$

Higher CMRR indicates better rejection of common input.

For ideal differential amplifier $A_{CM} = 0$.


Hence, $CMRR = \infty$

Slow Rate

It is the measure of how fast the output voltage of Op-Amp can change w.r.t. time.

$$\text{Slow Rate (SR)} = \frac{dV_o}{dt}_{\text{max}}$$

Unit $\rightarrow V/\mu s$

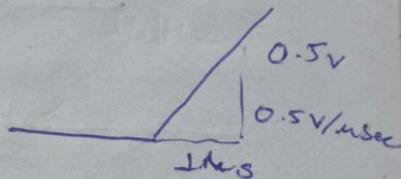


For ideal Op-Amp $SR \approx \infty$

Transfer Characteristics of op-Amp

Plot of O/P voltage (V_o) Vs difference i/p (V_d)

$$V_o = A_{OL}(V_1 - V_2)$$

$$V_o = A_{OL} V_d$$

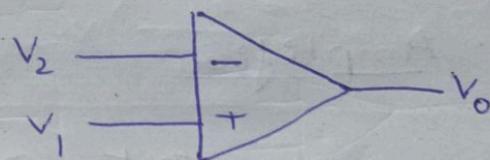


① Ideal Op-Amp

For ideal, $A_{OL} = \infty$.

If $V_d > 0 \Rightarrow V_o = +\infty = +V_{CC} = +V_{sat}$

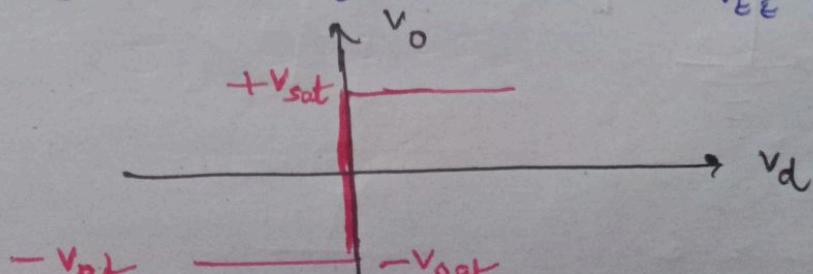If $V_d < 0 \Rightarrow V_o = -\infty = -V_{EE} = -V_{sat}$




(2) Non-Ideal op-Amp.

$A_{OL} = \text{large but finite}$

If V_d lies in the range $-\frac{V_{sat}}{A_{OL}}$ to $+\frac{V_{sat}}{A_{OL}}$

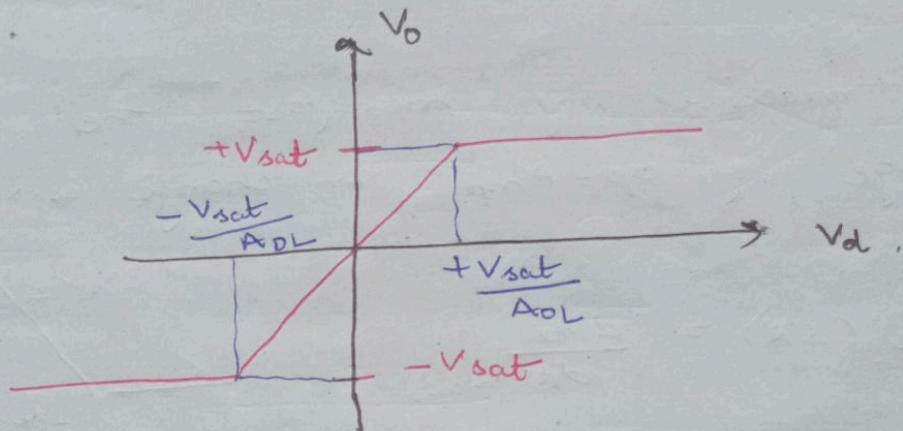
$\frac{+V_{sat}}{A_{OL}}$, O/P will vary linearly with V_d .



For very small values of V_d op-amp can be operated in linear region and for higher values of V_d op-amp will be in saturation region.

Inverting Amplifier

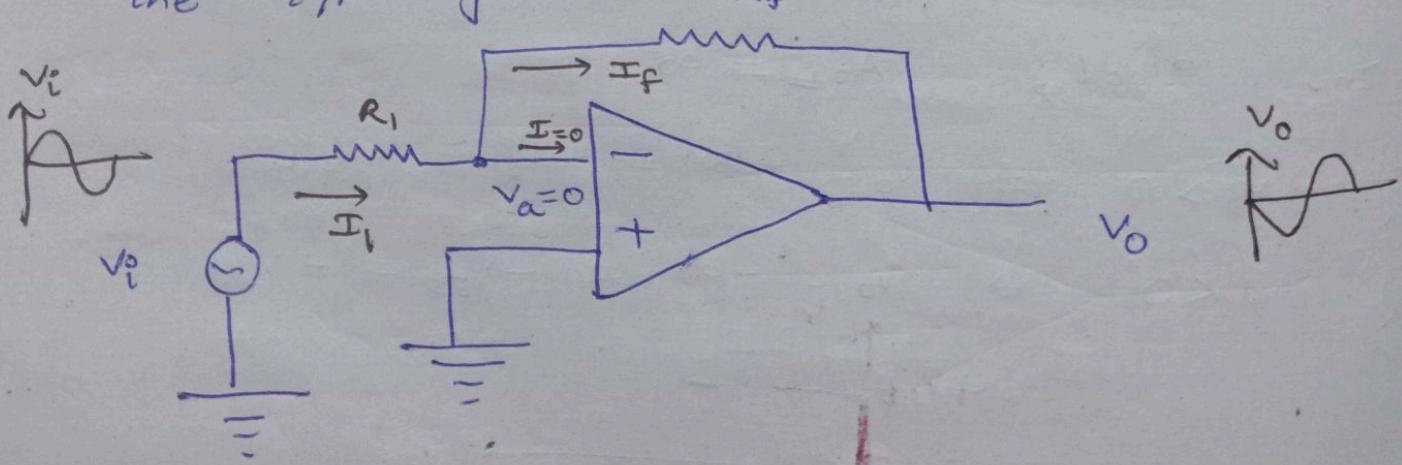An op-amp circuit that produces an Amplified O/P signal that is 180° out of phase with the I/P signal.



Applying KCL at node A,

$$I_1 = I_f$$

$$\frac{V_i - V_a}{R_1} = \frac{V_a - V_o}{R_f}$$

$$V_a = 0$$

$$\frac{V_i}{R_1} = -\frac{V_o}{R_f}$$

$$\boxed{V_o = -\frac{R_f}{R_1} \times V_i}$$

Gain ,

$$A = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

$$\boxed{A = -\frac{R_f}{R_1}} *$$

Concept of Virtual ground.


$$V_a = 0V$$

Q ⇒ For given op-amp config. determine the value of R_f required to produce a closed loop gain of -100.

For inverting Amplifier

$$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

$$\frac{-R_f}{2.2 \times 10^3} = -100$$

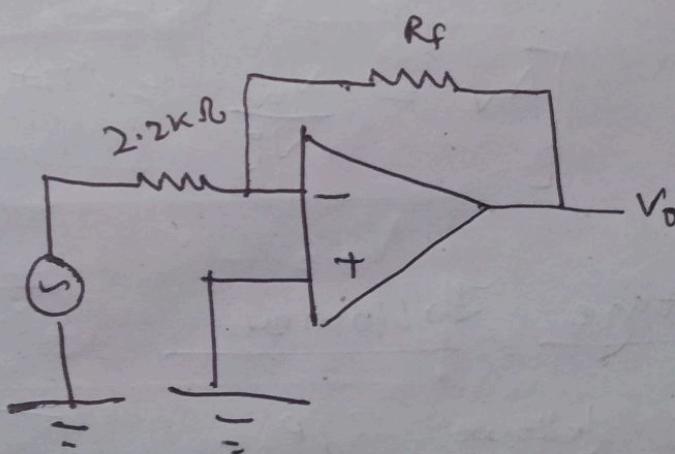


$$R_f = 2.2 \times 10^5 \Omega$$

Non Inverting Amplifier

A non-inverting amplifier is an op-amp circuit designed to provide voltage gain.

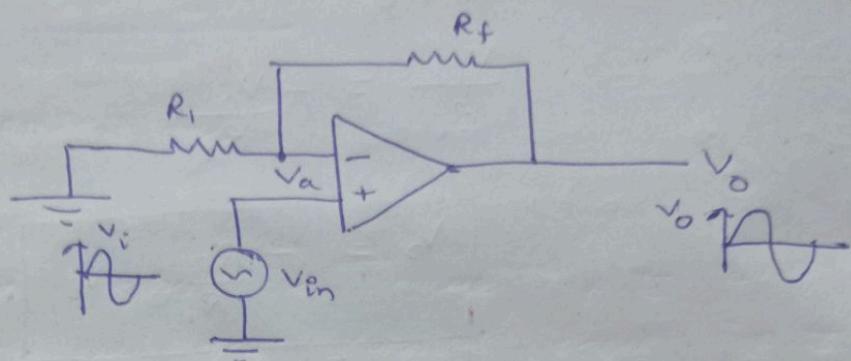The input is directly applied to non-inverting terminal.



$$V_a = \frac{V_o \times R_i}{R_i + R_f}$$

From concept of virtual ground $V_a = V_{in}$

$$V_{in} = \frac{V_o \times R_i}{R_i + R_f}$$

$$\boxed{V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}}$$

$$\boxed{A_v = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i}}$$

Voltage Follower


O/P follows I/P.

$$V_a = V_o$$

$$V_a = V_{in}$$


$$V_o = V_{in}$$

$$A_v = \frac{V_o}{V_{in}} = 1$$

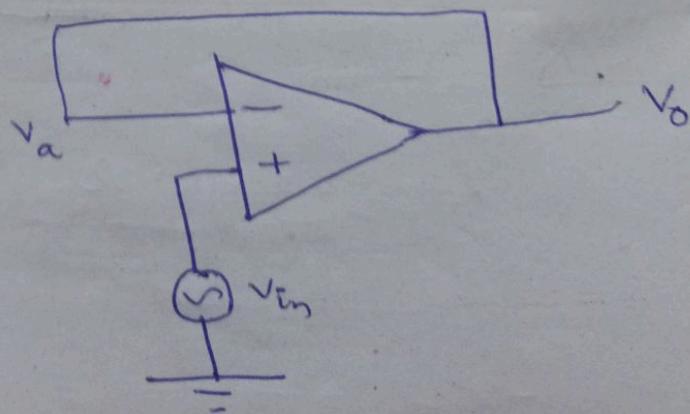

↳ It is used as Buffer
 ↳ It is used in instrumentation amplifier.

$$Q \Rightarrow V_o = ?$$

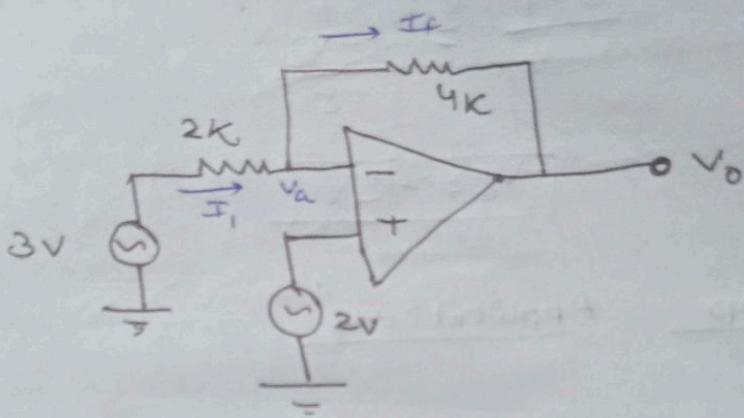

Sol:

$$V_a = 2V$$


$$I_i = I_f$$

$$\frac{3 - V_a}{2} = \frac{V_a - V_o}{4}$$

$$\frac{1}{2} = \frac{2 - V_o}{4}$$

$$2 - V_o = \frac{1}{2} \quad \rightarrow V_o = -\frac{1}{2}V$$

$$V_o = 0V.$$

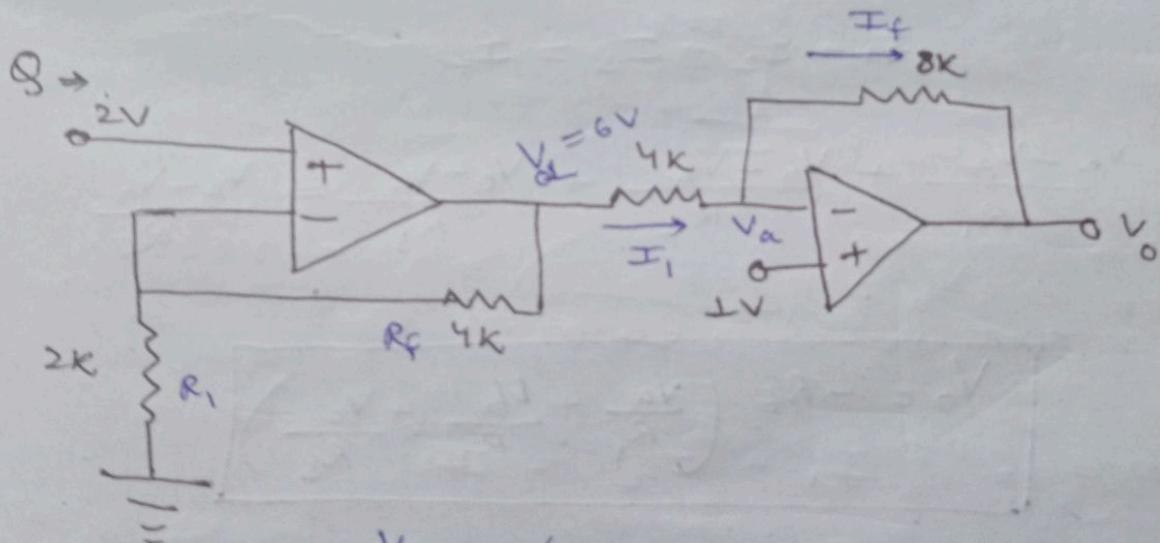

$$V_{o2} = \left(1 + \frac{R_F}{R_1}\right) V_i = \left(1 + \frac{4}{2}\right) \times 2 = 6V$$

By concept of virtual ground

$$V_a = 1V$$

KCL,

$$I_i = I_f$$

$$\frac{V_{O_L} - V_A}{4} = \frac{V_A - V_O}{8}$$


$$\frac{6-1}{4} = \frac{1-V_O}{8}$$

$$V_O = -9V$$

OP-Amp Applications

Adder:

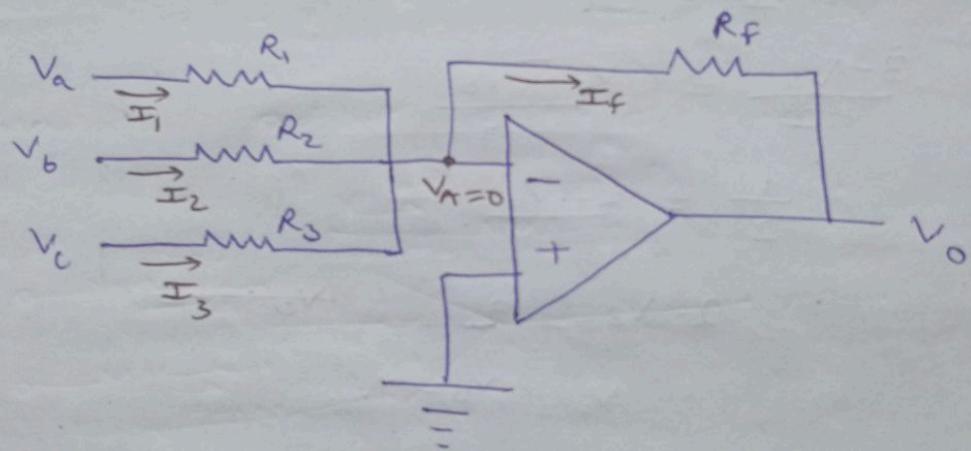It can accept two or more inputs and produces output as the sum of these inputs.



$$I_1 + I_2 + I_3 = I_f$$

$$\frac{V_a - V_A}{R_1} + \frac{V_b - V_A}{R_2} + \frac{V_c - V_A}{R_3} = \frac{V_A - V_O}{R_f}$$

$$V_O = -R_f \left(\frac{V_a}{R_1} + \frac{V_b}{R_2} + \frac{V_c}{R_3} \right)$$

If $R_1 = R_2 = R_3 = R$, then

$$V_O = -\frac{R_f}{R} (V_a + V_b + V_c)$$


$$+f \quad R_f = R_i$$

$$[V_o = R_f - (V_a + V_b + V_c)]$$

In this case, adder works with unity gain.

Averaging Amplifier

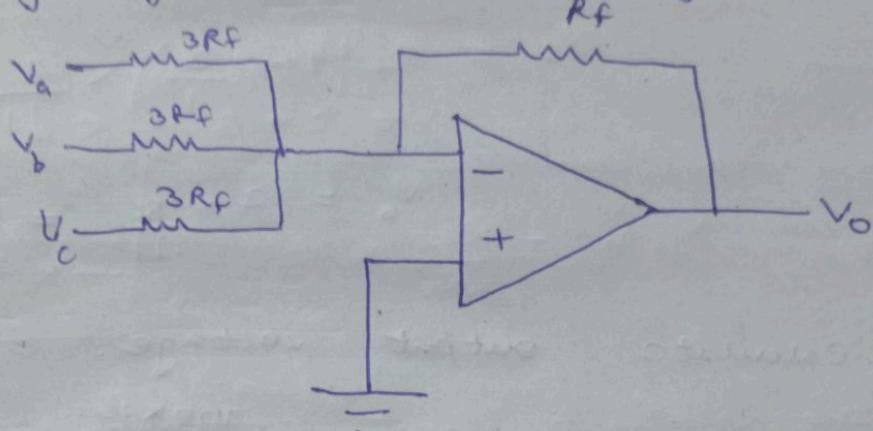It gives an O/P voltage proportional to average of all input voltages.




$$V_o = -\frac{R_f}{R_i} (V_a + V_b + V_c)$$

$$R_i = 3R_f$$

$$V_o = -\frac{(V_a + V_b + V_c)}{3}$$

- sign $\rightarrow 180^\circ$ out of phase.

Q → Calculate output voltage

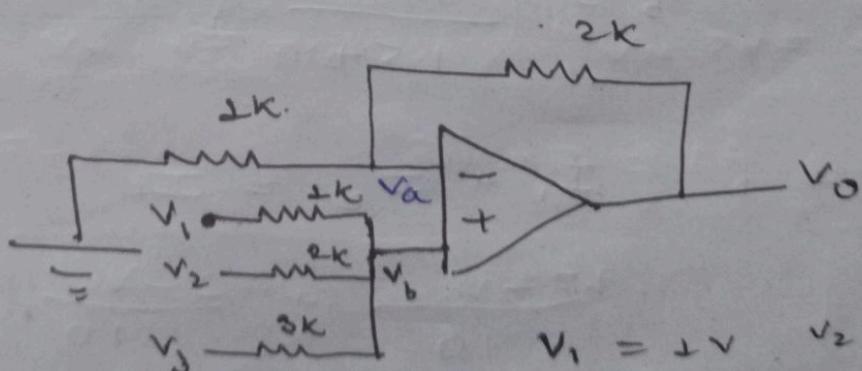

$$I_1 + I_2 + I_3 = 0 \rightarrow \text{Ideal OP-Amp}$$

No current flows inside.

$$\frac{V_1 - V_b}{1} + \frac{V_2 - V_b}{2} + \frac{V_3 - V_b}{3} = 0$$

$$V_b = \frac{18}{11} V$$


For non-inverting amplifier,

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

$$= \left(1 + \frac{2}{1}\right) \times \frac{18}{11}$$

$$V_o = 3 \times \frac{18}{11} = 4.9 V$$

Q ⇒ Calculate output voltage.

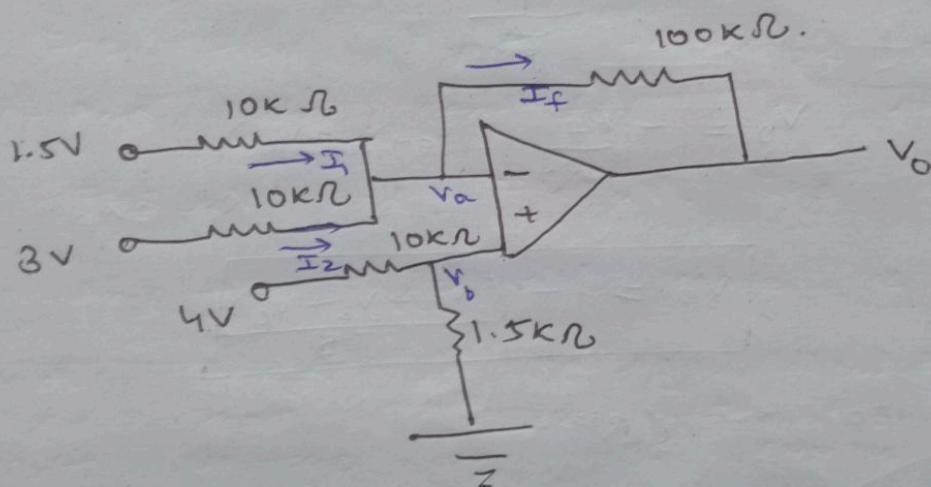


$$V_b = \left(\frac{1.5}{1.5+10}\right) \times 4 = 0.522 V$$

$$KCL \rightarrow I_1 + I_2 = I_f$$

$$\frac{1.5 - V_a}{10} + \frac{3 - V_a}{10} = \frac{V_a - V_o}{100}$$

concept of virtual short; $V_a = V_b = 0.522 V$


$$V_o = -34.56 V$$

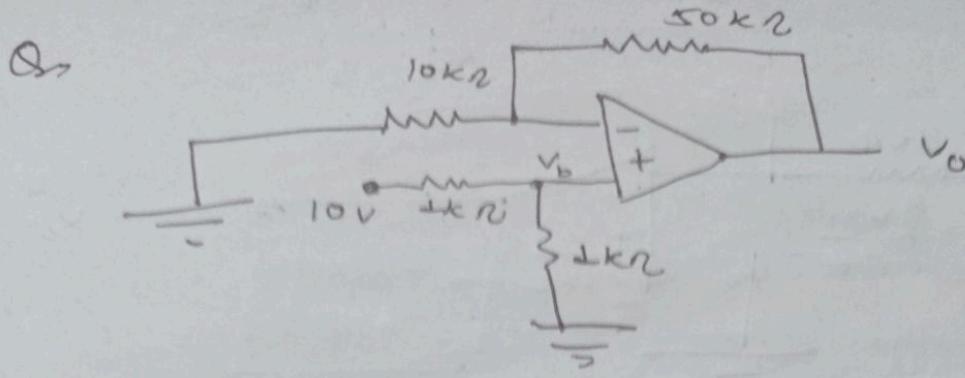

$$V_b = \frac{1}{1+1} \times 10 = 5 \text{ V}$$

For non-inverting amplifier,
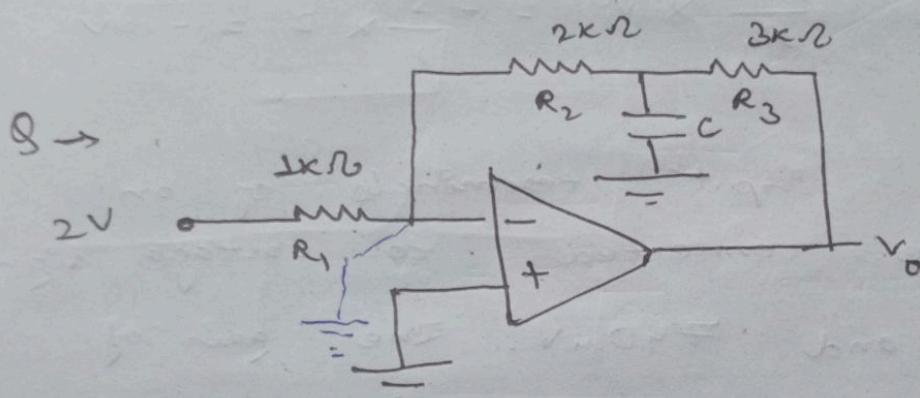
$$V_o = \left(1 + \frac{50}{10}\right) \times 5 = 30 \text{ V}$$



For DC C → open
 $R_f = R_2 + R_3 = 2 + 3 = 5 \text{ k}\Omega$


$$V_o = -\frac{R_f}{R_1} \times V_i = -\frac{5}{1} \times 2 = -10 \text{ V}$$

For AC C → closed short

$$R_f = R_3 \quad R_2 \rightarrow 0$$

$$V_o = -\frac{R_f}{R_1} \times V_i = -\frac{3}{1} \times 2 = -6 \text{ V}$$

Q → Determine

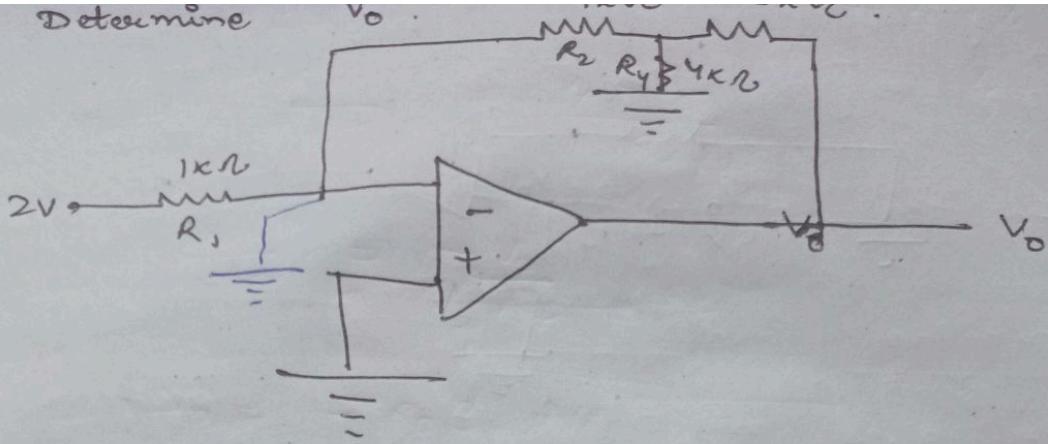

$$R_f = R_2 \parallel R_4 + R_3 \\ = 2 + 3 = 5 k\Omega$$

$$V_o = -\frac{R_f}{R_1} \times V_i = -\frac{5}{1} \times 2 = -10V$$

Q → The two input terminals of an op-Amp are connected to voltage signals of 745 mV and 740 mV. The gain of Op-Amp in differential mode is 5×10^5 and CMRR is 80 dB. calculate the output voltage and % error due to common mode.

$$V_1 = 745 \text{ mV} \quad V_2 = 740 \text{ mV}$$

$$A_d = 5 \times 10^5 \quad \text{CMRR} = 80 \text{ dB}$$

$$V_d = V_1 - V_2 \\ = 5 \text{ mV}$$

$$V_o = ? \quad \% \text{ error} = ?$$

$$V_o = A_d V_d + A_C V_c$$

$$V_c = \frac{V_1 + V_2}{2} \\ = \frac{745 + 740}{2}$$

$$\text{CMRR} = \frac{A_d}{A_C}$$

$$CMRR \text{ in } dB = 20 \log \frac{A_d}{A_c}$$

$$80 = 20 \log \frac{A_d}{A_c}$$

$$\frac{A_d}{A_c} = 10^4 \quad A_c = 50$$

$$V_o = 5 \times 10^5 \times 5 \times 10^{-6} + 50 \times \sqrt{\frac{745 + 740}{2}}$$

$$V_o = 2.537 V$$

~~for~~

ideal OP-Amp.

$$V_o = A_d V_d$$

$$= 5 \times 10^5 \times 5 \times 10^{-6}$$

$$= 2.5 V$$


$$\% \text{ error} = \frac{2.537 - 2.5}{2.5} \times 100\%$$

$$= 1.484 \%$$

Differentiator

It is that performs mathematical differentiation of I/P signal.

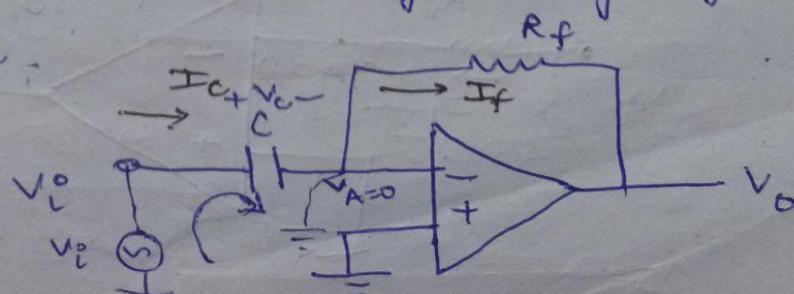The output of differentiator is proportional to rate of change of its I/P signal.



$$I_C = I_f$$


$$-V_i + V_c = 0$$

$$V_c = V_i$$

$$C \frac{dV_c}{dt} = \frac{V_A - V_o}{R_f}$$

$$C \frac{dV_o}{dt} = -\frac{V_o}{R_f}$$


$$\boxed{V_o = -R_f C \frac{dV_o}{dt}}$$

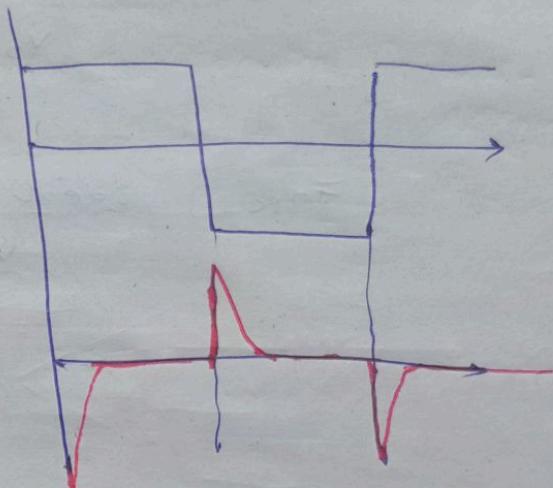

Integration

Ckt that performs integration of i/p signals.

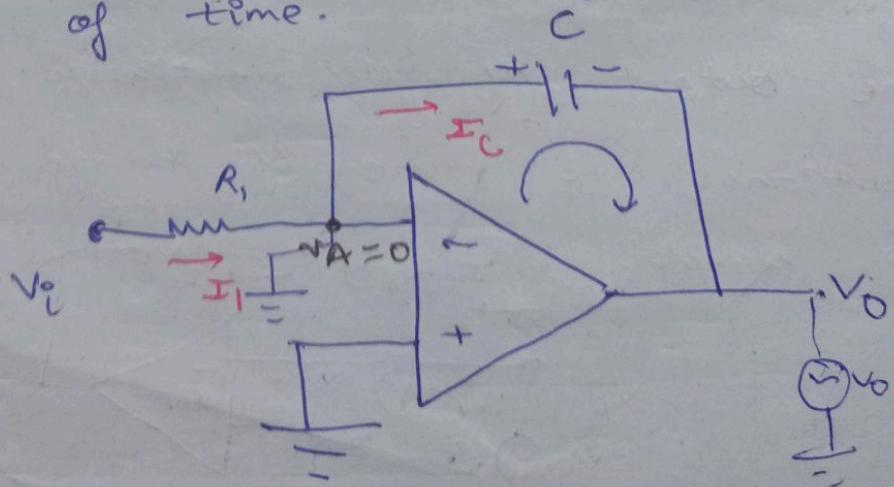The o/p of integrator is proportional to area of i/p waveform over a period of time.



$$v_c + v_o = 0$$

$$I_1 = I_C$$

$$\therefore v_c = -v_o$$

$$\frac{v_c - v_A}{R_1} = C \frac{dv_c}{dt}$$

$$I_C = C \frac{dv_c}{dt}$$

$$\frac{v_o}{R_1} = -C \frac{dv_o}{dt}$$

$$\int_0^t \frac{v_i}{R_1} dt = -C \int_0^t \frac{dv_o}{dt} dt$$

$$\frac{1}{R_1} \int_0^t v_i dt = -C v_o$$

$$v_o = -\frac{1}{R_1 C} \int_0^t v_i dt$$

