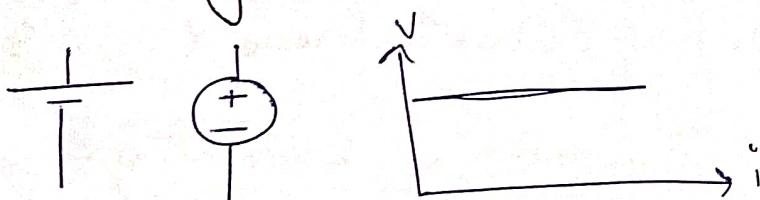


UNIT-1Circuit / Network


(VED PRAKASH TIWARI)

↳ interconnection of various elements.

Source → Voltage Source  
Source → current source.





Ideal voltage source

→ voltage across ideal voltage source remains constant irrespective of current.

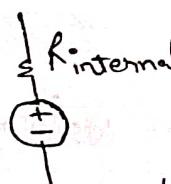Practical voltage source

→ when current increases through this, voltage across terminal decreases


$$I \uparrow V \downarrow$$

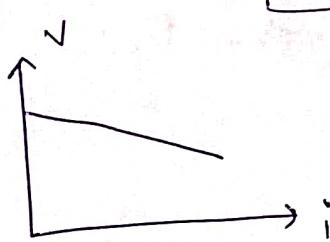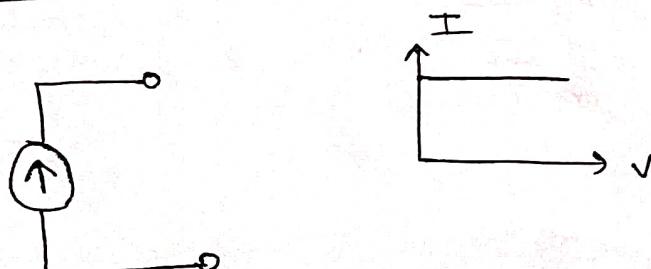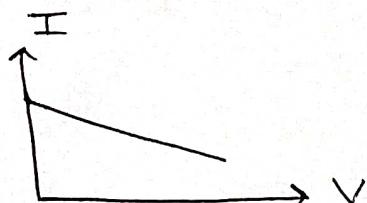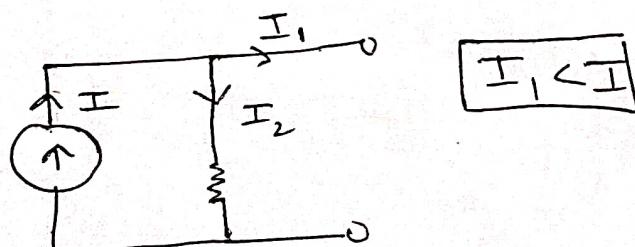Ideal current sourcepractical current source

→ these are independent source.

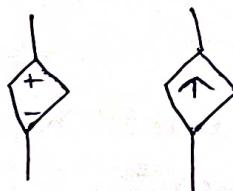
## DEPENDENT SOURCE

- also "Controlled Source"
- Voltage controlled voltage source (VCVS)
- ~~current controlled voltage source (CCVS)~~
- Current controlled current source (CCCS)
- Voltage controlled current source (VCCS)




Dependency:  $KV_o, KI_o$

## VCVS

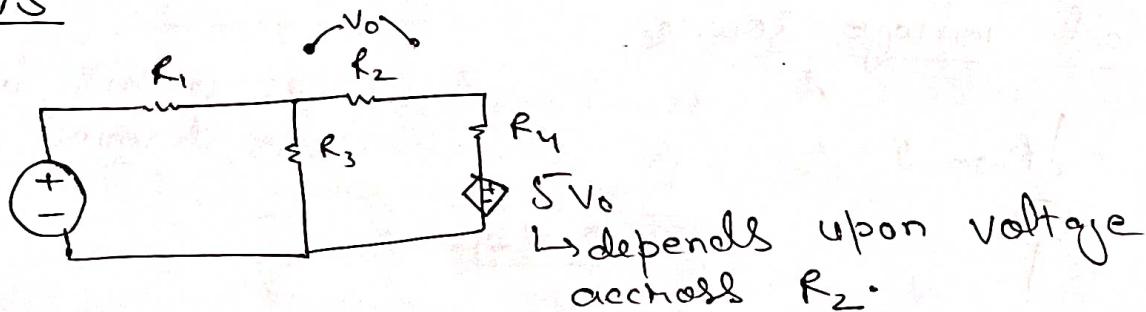

## CCVS

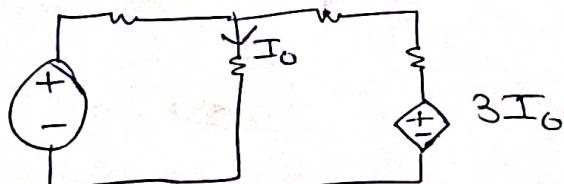

## Unilateral elements

- it allows current flowing through both direcns  
decentral without changing its characteristics.  
eg diode, BJT(bipolar junction Transistor)

## Bilateral elements

- it allows current flowing through both direcns.  
without changing its characteristics.

eg R, L, C

## Active elements

- if an element has an internal energy source  
that can drive the circuit is active element.  
eg voltage source, semiconductor devices.

## passive elements

- pass element which dissipates or stores  
energy.

eg . R, L, C



## LINEarity of Network

- ↳ compulsory ① Homogeneity  
② Superposition

- if any element follow these then it is be follows  
linearity.

(Scaling property)

→ HOMOGENEITY for  $y \rightarrow$  function

$$\boxed{y(ax) = a y(x)} \quad (\text{homogeneity only})$$

Scaling property

e.g.

$$f(n) = y = 7n \quad \hookrightarrow \text{yes, follows homogeneity}$$

$$f(an) = 7(an) = a \cdot 7n = af(n)$$

$$\boxed{y(an) = a y(n)}$$

②)  $f(n) = 3n^2 \rightarrow$  does not follow, homogeneity

$$f(an) = 3a^2n^2 \neq a f(n)$$

→ SUPER POSITION (additive property)

$$\boxed{y(x_1+x_2) = y(x_1) + y(x_2)}$$

→ if we are applying 2 signal simultaneously, then effect must be sum of signal when applied solo.

e.g.

$$f(n) = 7n$$

$$f(n_1+n_2) = 7n_1 + 7n_2 \\ \Rightarrow f(n_1) + f(n_2)$$

↳ Shows additive property

$$y(n) = 3n^2$$

$$f(n_1+n_2) = 3(n_1+n_2)^2 \neq f(n_1) + f(n_2)$$

↳ does not show additive prop.


→ if an element follow both if it follows both.

$\rightarrow$   $R, L \& C$  as linear

$R:$

$$V = IR$$

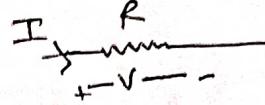
$\rightarrow$  this is linear eqn. & shows linearity of  $R$



$L:$

$$V = L \frac{dI}{dt}$$

$\hookrightarrow$  this eqn.

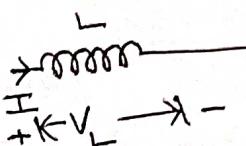


$\rightarrow$  is non linear eqn.

$\hookrightarrow$  by this we cannot show  $L$  as linear

So, we apply another eqn,

$$\Phi = LI \rightarrow$$
 it is a linear eqn.

$C:$

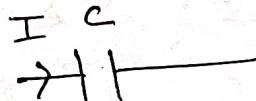

$+V_C \rightarrow -$

$$I = C \frac{dV_C}{dt}$$



$$\Rightarrow V_C = \frac{1}{C} \int I \cdot dt \quad \hookrightarrow \text{non linear eqn.}$$

$$\Phi = CV \rightarrow$$
 it is a linear eqn.

Source Transformation

$\rightarrow$  we can replace these connections


if required. (R same in both case)

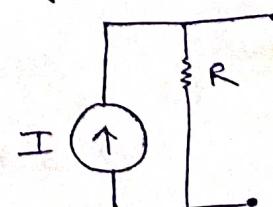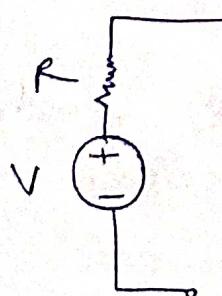

$$V = IR \rightarrow$$
 use this to find value.


## Series & || connection
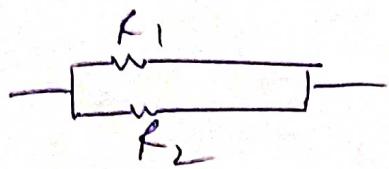
$$\text{In } R_1 \text{ and } R_2 \quad R_{eq} = R_1 + R_2$$




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$
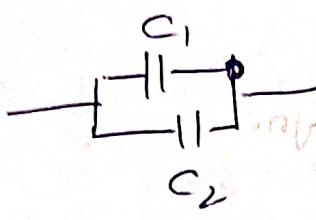
$$\text{In } C_1 \text{ and } C_2 \quad \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$




$$C_{eq} = C_1 + C_2$$
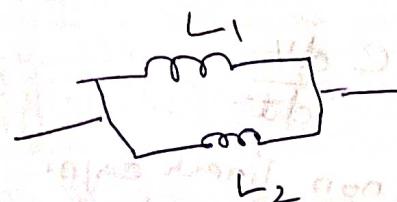
$$\text{In } L_1 \text{ and } L_2 \quad L_{eq} = L_1 + L_2$$



$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

## Loop analysis

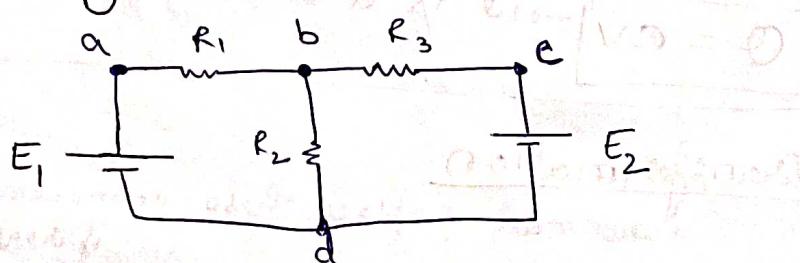

### node

↳ if equipotential point ~~exists~~ at which 2 or more elements are connected.

e.g.: (a,b,c,d)

### Junction

↳ is equipotential point where 3 or more than 3 elements are connected. (b,d) e.g.

Branch:- is that part of network which lies b/w 2 junctions.

e.g.: dab, ab, dcba

Loop:- any closed path in a circuit is a loop.

e.g. abda, bedb, acda

↳ elementary loops


Mesh:

↳ elementary loops are called mesh.

e.g. abda, bedb

Mesh analysis:-

Q).

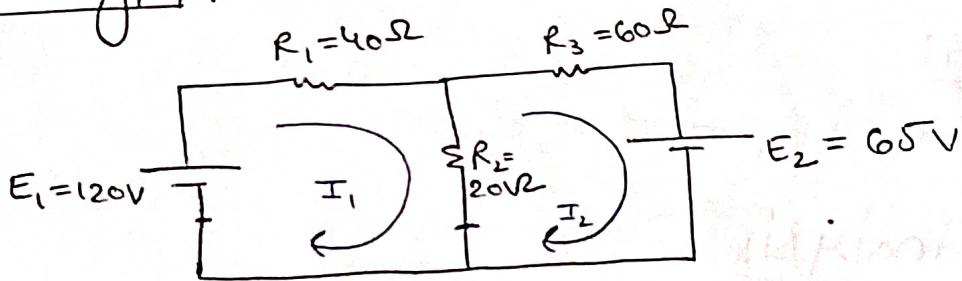

~~Wavy line~~

by KVL Loop 1:

$$-120 + 40I_1 + (I_1 - I_2)20 = 0 \quad \text{--- (1)}$$

$$24I_1 + 2I_1 - 2I_2 = 120$$

$$3I_1 - I_2 = 6$$

$$I_2 = 3I_1 - 6$$

by KVL Loop 2:

$$(I_2 - I_1)20 + 60I_2 + 65 = 0 \quad \text{--- (2)}$$


$$80I_2 - 20I_1 + 65 = 0$$

$$16I_2 - 4I_1 + 13 = 0$$

$$I_1 = 4.38$$

$$I_2 = 7.14$$

#

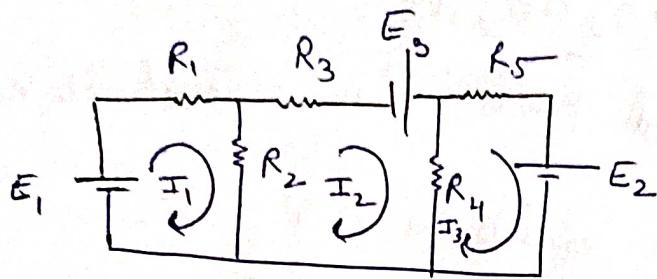loop 01:

$$-E_1 + I_1 R_1 + (I_1 - I_2) R_2 = 0$$


loop 02:

$$I_2 R_3 - E_3 + (I_2 - I_3) R_4 + (I_2 - I_1) R_2 = 0$$

loop 03:

$$I_3 R_5 + E_2 + (I_3 - I_2) R_4 = 0$$

## Nodal Analysis

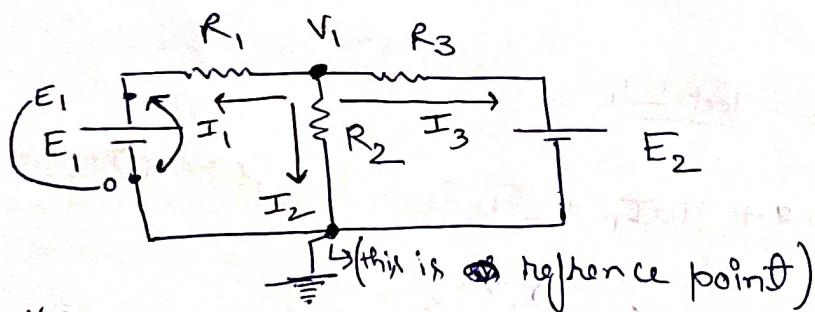KCL

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - E_1}{R_1} + \frac{V_1 - 0}{R_2} + \frac{V_1 - E_2}{R_3} = 0$$


$$V_1 = \frac{H90}{11}$$

$$I_1 = \frac{44.5 - 120}{40} \Rightarrow -1.088$$

$$I_2 = 2.27$$


$$I_3 = -0.39$$

Q2

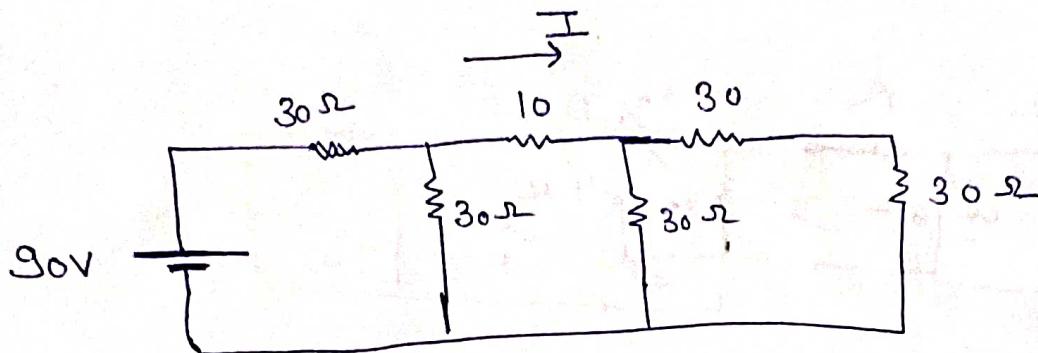

Find  $I$  using ~~Mesh analysis~~


Soln

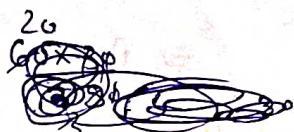

$$i_{\text{net}} = \frac{90}{45} \Rightarrow 2$$

$$I = \frac{i_{\text{net}}}{2} = 1A$$

## # STAR-DELTA Transformation

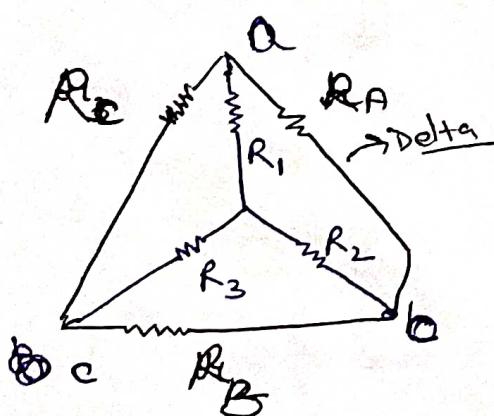

$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

## Network theorems




→ Superposition theorem

→ Thevenin's theorem → Norton's theorem → Maximum power transfer theorem.

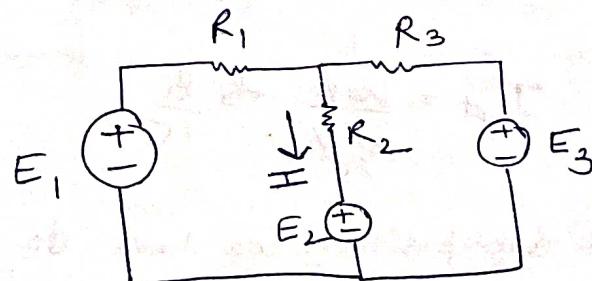1. Superposition theorem: - active linear bilateral network containing 2 or more sources, then combined effect of all source is always equal to summation of the individual sources on (all other off).






→

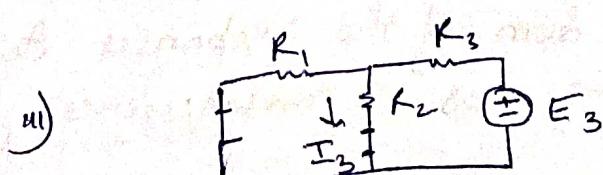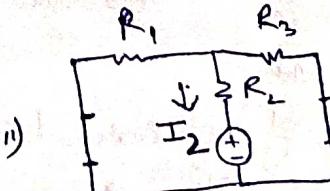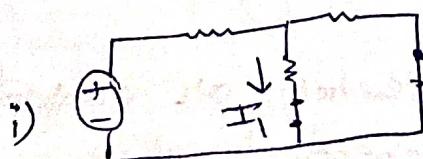


$$I = I_1 + I_2 + I_3$$

→ Current source → replace with open circuit  
 Voltage source → short circuit



eg

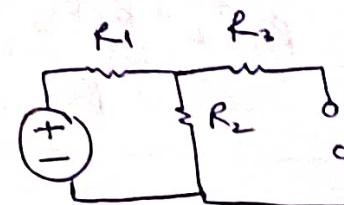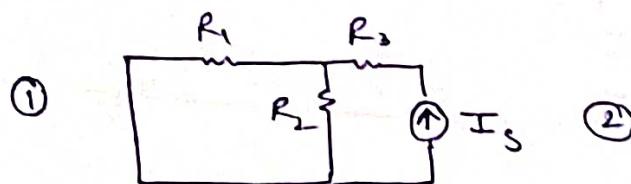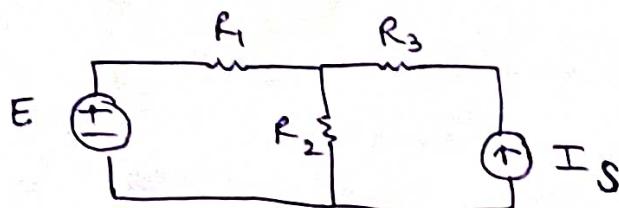

(a)

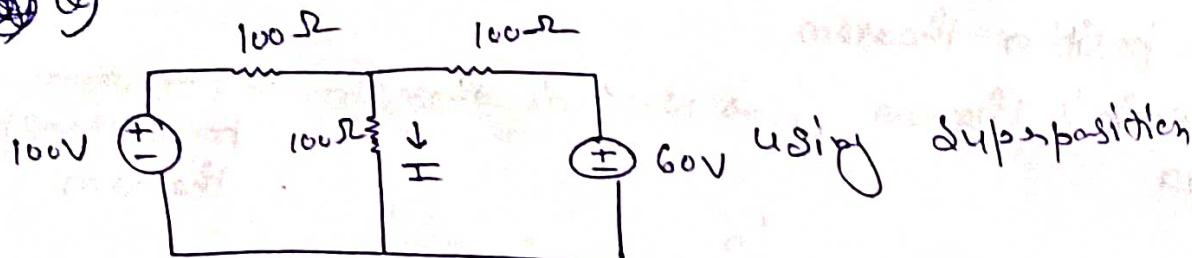

using superposition

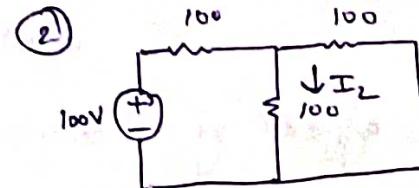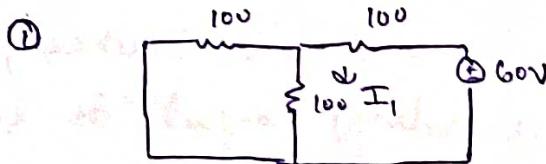

$$I_1 = \frac{60}{150}$$


$$I_2 = \frac{100}{300}$$

$$I_{\text{net}} = \frac{60}{300} \Rightarrow \frac{2}{15}$$

→ To verify the superposition, we have to show it by superposition & by one another method.


→ The response of network (Voltage across or current through an element) with several independent sources can be obtained as the sum of the responses to sources taken one at a time as a consequence of circuit linearity.

→ Current division rule :-

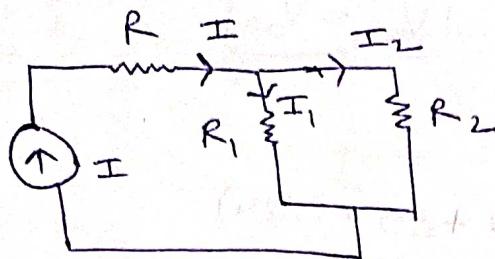

$$I_1 = \left( \frac{R_1}{R_1 + R_2} \right) I$$
$$I_2 = \left( \frac{R_2}{R_1 + R_2} \right) I$$


→ Voltage division rule :-

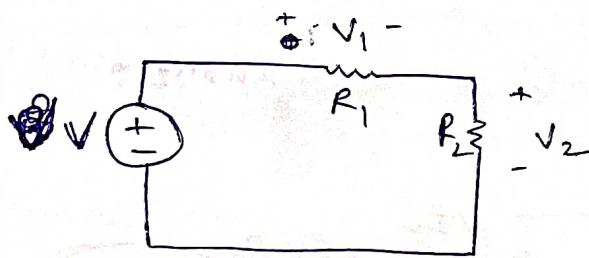

$$V_1 = \left( \frac{R_1}{R_1 + R_2} \right) V$$

$$V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V$$


② Thevenin's theorem :-

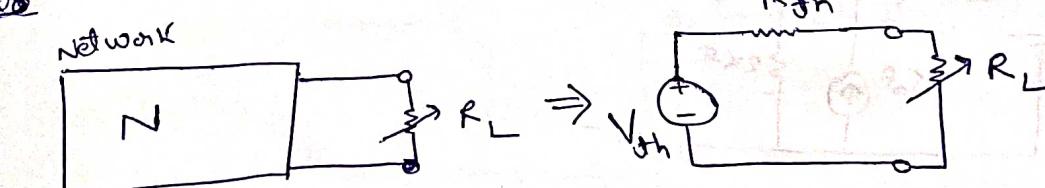



Complex  
network

#


(current, voltage & power of  $R_L$ )

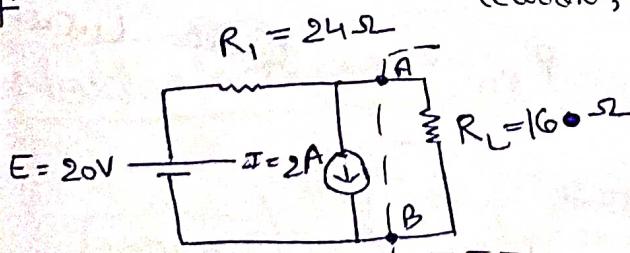

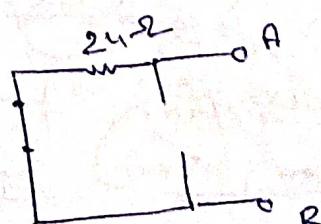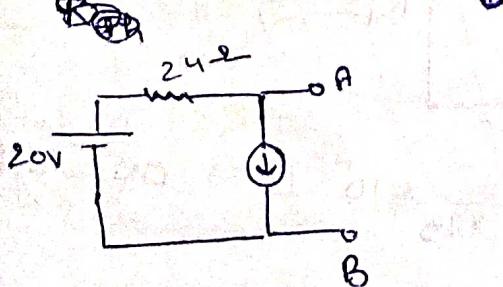①  $R_{th}$   
→ ~~inactive~~ inactive all the sources  
 $\rightarrow R_{AB} = R_{th}$


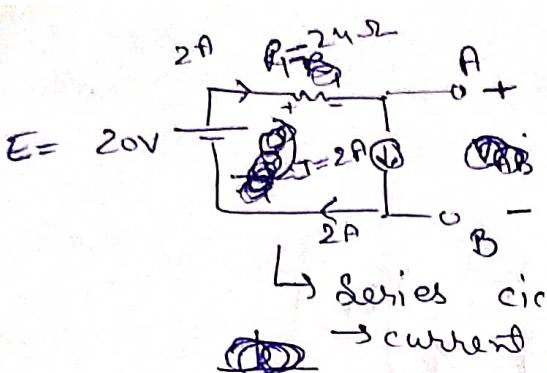
$$R_{AB} = 24\Omega \Rightarrow R_{th} = 24\Omega$$




$\frac{V_{th}}{R_{th}}$  ~~is open~~  $\rightarrow V_{AB}$  across A B

$$\boxed{V_{AB} = V_{th}}$$

$$V_{AB} = +20 - 2(2)$$


$$\Rightarrow 28 \text{ Volt.}$$

$$\boxed{V_{th} = 28V}$$

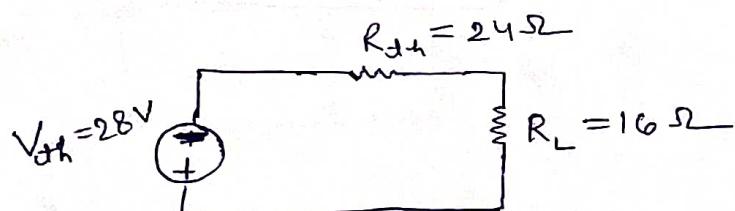

KNDMS


### ③ Norton's theorem

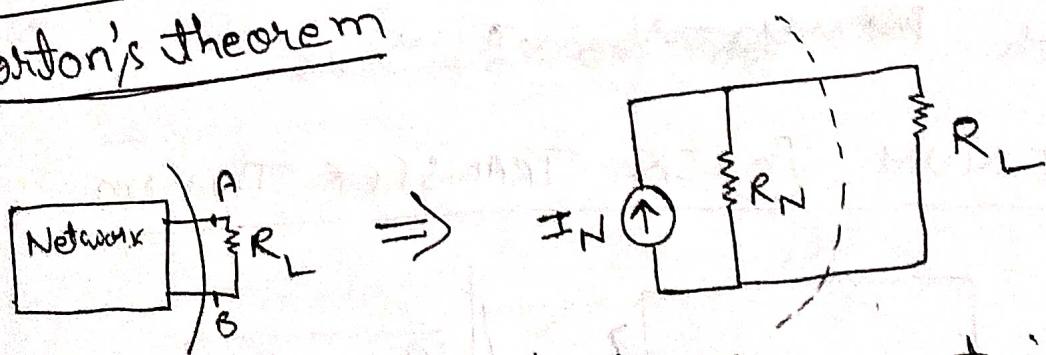



i)  $R_N$  ii)  $I_N$  (short circuit AB, current in AB =  $I_N$ )

↳ Same as  $R_{th}$

Q7

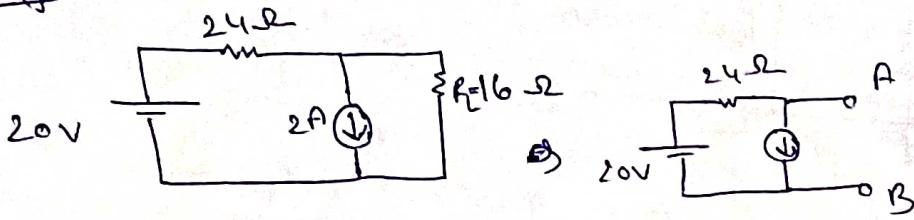


$$R_N = R_{th} = 24\Omega$$

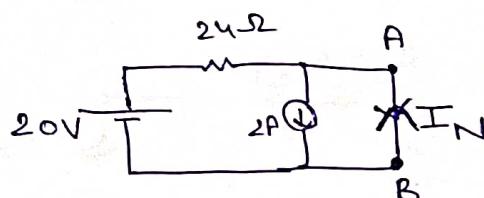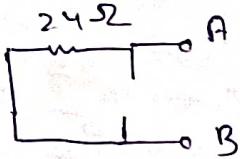


by superposition,

~~$$I_N = \frac{20}{24} \Rightarrow \frac{5}{6} A \Rightarrow 1.67 A$$~~

Norton equivalent

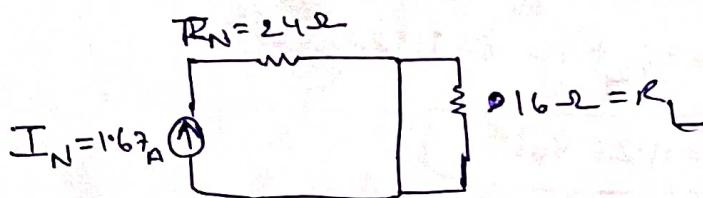

$$R_{th} = 24\Omega$$

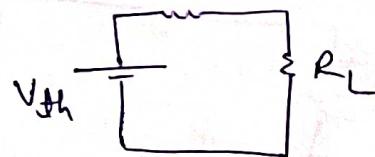

~~$$V_{th} = I_N R_{th}$$~~

$$= I_N R_N = \frac{5}{6} \times 24 \Rightarrow 20V$$

→ Thevenin & Norton circuit are dual circuit

→  $R_N = R_{th}$  ~~mutually conservative~~

#### ④ MAXIMUM POWER TRANSFER Theorem



Power delivered to  $R_L$  will be Maximum.

Proof:

$$V_s = I^2 R$$



$$P_{RL} = I^2 R_L$$

$$\Rightarrow \frac{V_s^2}{(R_L + R_S)^2 R_L}$$

$$\frac{dP_L}{dR_L} = V_s^2 \left( \frac{(R_L + R_S)^2 - R_L^2(R_L + R_S)}{(R_L + R_S)^4} \right)$$

$$\Rightarrow \frac{V_s^2}{(R_L + R_S)^4} \times (R_L + R_S) \left( R_L + R_S - 2R_L \right)$$

$$\Rightarrow \frac{V_s^2}{(R_L + R_S)^3} (R_S - R_L)$$

for maxima,

$$R_L = R_S$$


$$\frac{V_s^2}{(R_L + R_S)^3} (2R_S - 2R_L) = 0$$

$$\boxed{(P_L)_{\text{max}} = \frac{V_s^2}{4 R_S}}$$

5 Jan 2021

SUPER node

→ [Ignore]

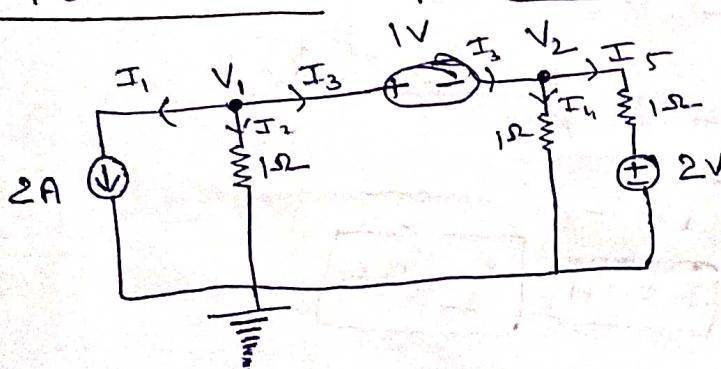

$$I_1 + I_2 + I_3 = 0 \quad -I_3 + I_4 + I_5 = 0$$

$$\therefore I_3 = I_4 + I_5$$

$$I_1 + I_2 + I_4 + I_5 = 0$$

$$\rightarrow 2 + \frac{V_1 - 0}{1} + \frac{V_2 - 0}{1} + \frac{V_2 - 2}{1} = 0$$

$$2V_2 + V_1 = 0 \quad \& \quad V_1 - V_2 = 1$$

$$2V_2 + 1 = 0$$


$$V_2 = -\frac{1}{2} \quad V_1 = \frac{2}{3}$$

$$I_4 = -\frac{1}{3}, \quad I_5 = -\frac{2}{3}$$

$$I_3 = -\frac{8}{3} \text{ A}$$

$$P_{(1v)} = (1) \frac{8}{3} \Rightarrow \frac{8}{3} \text{ W}$$

## Super Mesh

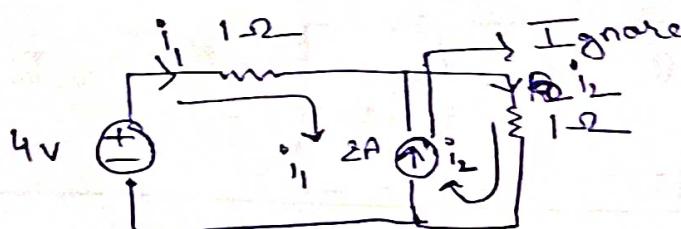

$$-4 + i_1 + i_2 = 0$$

$$i_1 + i_2 = 4 \quad \& \quad i_1 + 2 = i_2$$

$$2i_1 = 2$$


$$i_1 = 1 \text{ A}$$

$$i_2 = 3 \text{ A}$$

$$\eta = \frac{P_{RL}}{P_{RL} + P_{R_{DS}}} \times 100 \Rightarrow 50\% \quad (\text{in Maximum power Transfer theorem})$$


efficiency of system

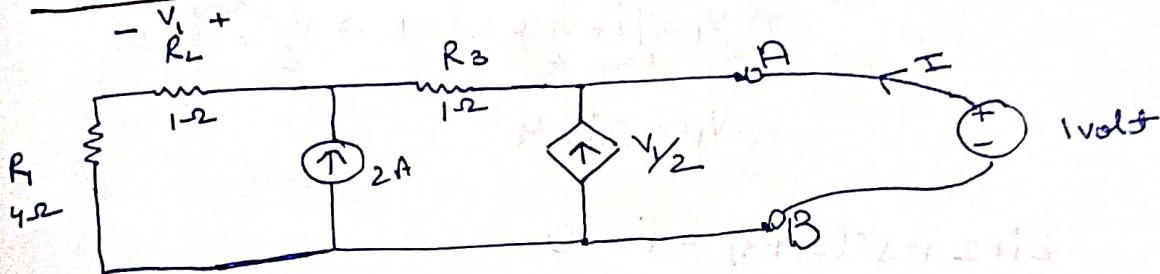Thevenin's / Norton's (with Dependent Source)



#  $R_{th}$

$$R_{AB} = \frac{1}{I} = R_{th}$$

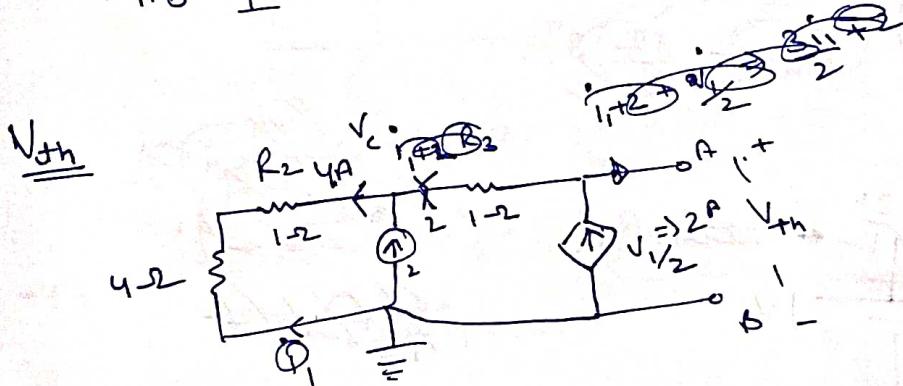

~~$$V_1 = R_2 i_1$$~~

~~$$V_1 = -6V$$~~

~~$$V_{th} = -6V$$~~

$$\frac{V_c}{10} + 2 - \frac{V_1}{2} = 0$$


$$V_1 = \frac{1}{5} \times V_c \Rightarrow \frac{V_c}{5}$$

$$\frac{V_c}{10} = 2 \Rightarrow V_c = 20$$

$$V_{th} = 2 + 4 + 4(4) = 22$$

$$V_{th} = 22 \text{ Volt}$$

$R_{th}$

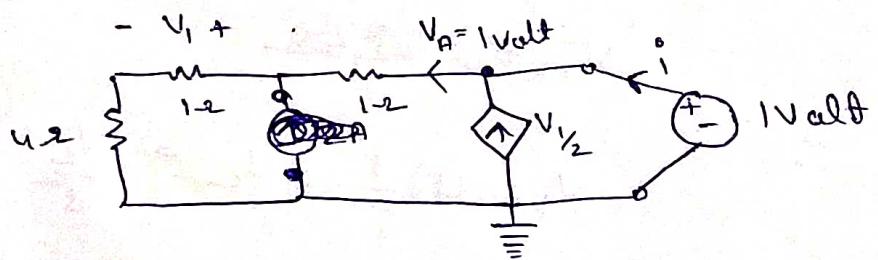

$$R_{AB} = \frac{1}{\frac{1}{12} + \frac{1}{12}}$$

$$V_1 = V_p \left( \frac{1}{6} \right) \Rightarrow \frac{V_A}{6} \Rightarrow \frac{1}{6}$$

$$\frac{V_A - 0}{6} - \frac{V_1}{2} - i = 0$$

$$\frac{1}{6} - \frac{1}{12} - i = 0 \Rightarrow i = \frac{1}{12}$$

$$R_{AB} = \frac{1}{i} \Rightarrow \frac{1}{Y_{12}} \Rightarrow 12 \text{ A}$$