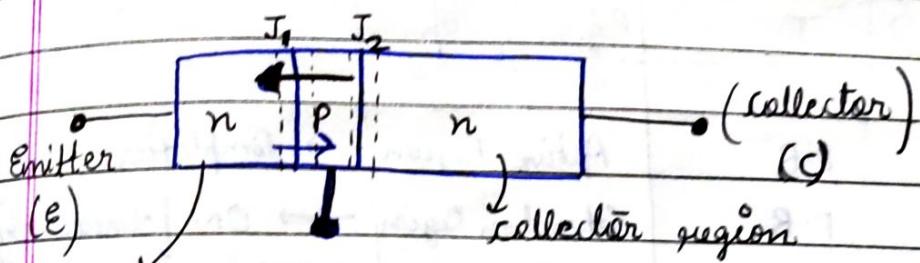


BJT [Bipolar Junction Transistor]

Date _____
Page _____


Physical Structure :-



Emitter region

J₁ → emitter-base


J₂ → collector-base

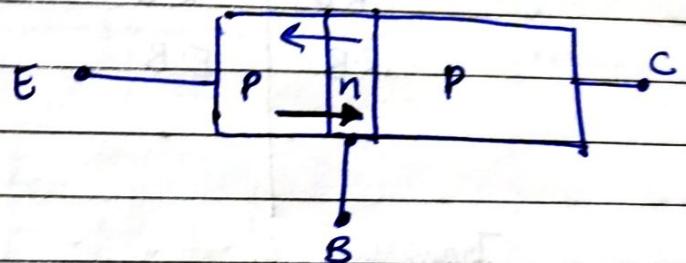

* Width :- C > E > B

* Doping :- E > C > B

Symbol :-

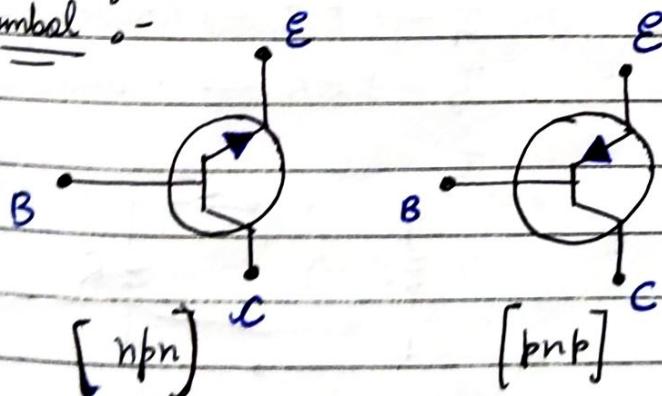

Bipolar Junction Transistor :-

- ① e⁻
- ② hole

Transistor \Rightarrow Transfer + Resistor


J₁ → Forward biased

J₂ → Reverse biased

Regions of operation :-

J ₁	J ₂	Region of Operation
F-B	R-B	Active Region → Amplifier
F-B	F-B	Saturation Region → ON [closed switch]
R-B	R-B	cutoff Region → OFF [open switch]
R-B	F-B	Inverted → Rarely used


Transistor Operation :-

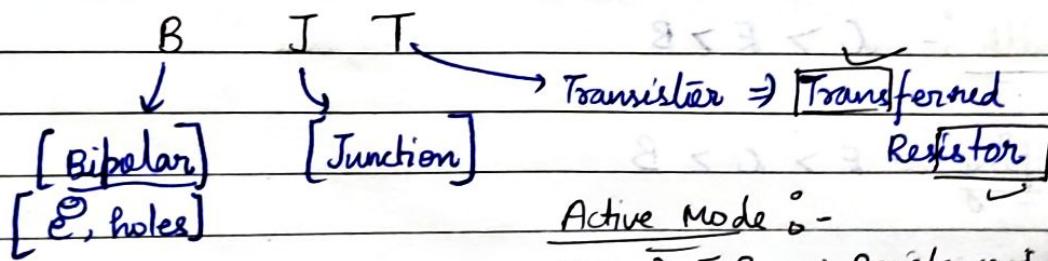

Active Mode :-

J₁ → F-B → Resistance ≈ 0

J₂ → R-B → Resistance $\approx \infty$

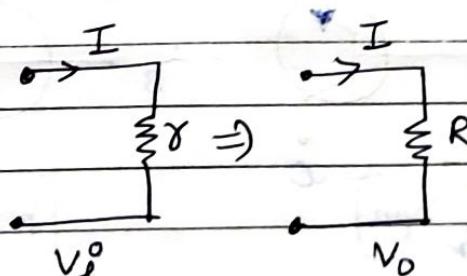

$$V_i^o = I \times \gamma$$

$$- R > \gamma$$

$$V_o = I \times R$$

$$V_i^o < V_o$$


[Amplification]

$V_{bt} + V_{CB}$

Base \rightarrow very small + lightly doped

Date _____
Page _____

Active mode :-

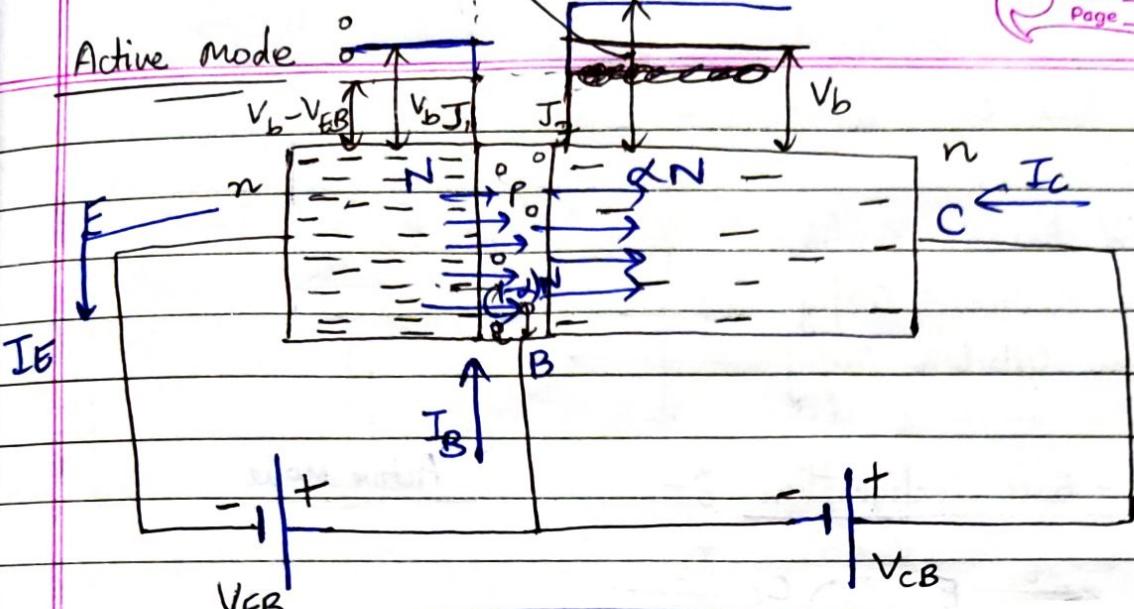

Reverse sat-current
or leakage current

$$I_c = \alpha I_b + I_{co}$$

KCL :-

$$I_e = I_b + I_c$$


Active mode :- Emitter-Base Junction (J_1) is F.B
Collector-Base Junction (J_2) is R.B

- B, E and C

- Common Base Config.
- Common Emitter Config
- Common Collector Config

→ Common - Base Configuration

Active mode

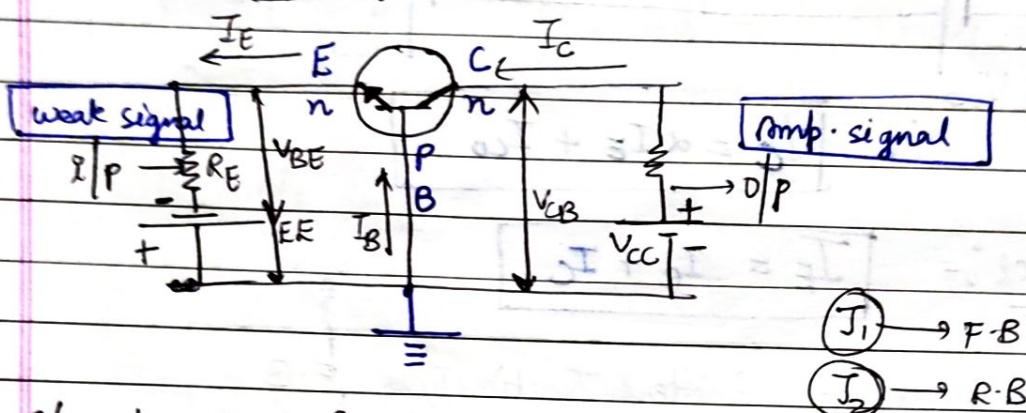

i/p characteristic

I_E Vs V_{BE}

$J_1 \rightarrow EB$ Diode
 $J_2 \rightarrow BC$ Diode

O/p characteristic

I_C Vs V_{CB}

Active mode

$$KCL \quad I_E = I_B + I_C \quad \rightarrow ①$$

$$I_C = \alpha I_E + I_{C0} \quad \begin{matrix} \text{Reverse} \\ \text{saturation} \end{matrix} \quad \begin{matrix} \text{current} \\ \text{when emitter} \\ \text{terminal is open} \end{matrix}$$

or

$$I_C = \alpha I_E + I_{CBO} \quad \begin{matrix} \text{Reverse saturation} \\ \text{current when emitter} \\ \text{terminal is open} \end{matrix}$$

$$I_E \gg I_{CBO}$$

$$I_B = (1-\alpha) I_E$$

$$I_C = \alpha I_E$$

$$\alpha = \frac{I_C}{I_E}$$


$$\text{gain} = \frac{\text{o/p}}{\text{i/p}}$$

Common
base current gain/amp factor

$$\alpha = 0.95 - 0.98 \Rightarrow 95\% - 98\%$$

Common Base Transistor [Input Characteristics]

Date _____
Page _____

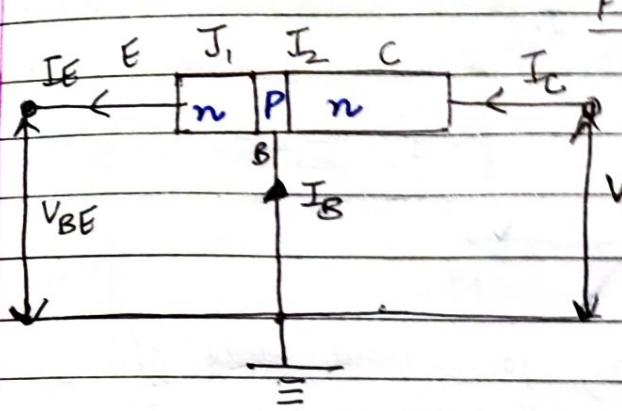

F.B Diode

Early Effect

$i/p \text{ I vs } i/p \text{ V}$ for different
 $o/p \text{ V}$.


$$i/p \text{ I} = I_E$$

$$i/p \text{ V} = V_{BE}$$


$$o/p \text{ V} = V_{CB}$$

$$o/p \text{ I} = I_C$$
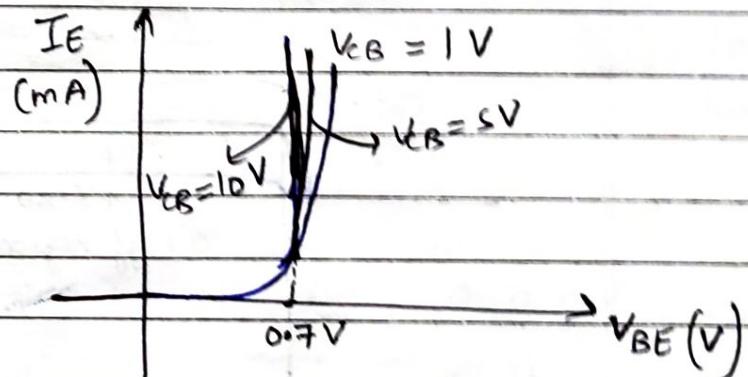
$$V_{CB} \uparrow \rightarrow I_E \uparrow$$



Early Effect :- [Base width modulation]

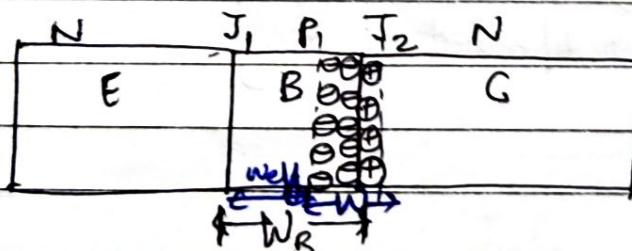

$J_1 \Rightarrow F.B \quad J_2 \Rightarrow R.B$

$V_{CB} \uparrow \rightarrow R.B \uparrow$

$W_B \Rightarrow$ width of the Base / Metallurgical base width Doping :-

$$E > C > B$$

$$V_{CB} \uparrow \quad R.B \uparrow \quad W \uparrow$$

R.B increase \Rightarrow Depletion layer will increase

$$w_{eff} = W_B - W \uparrow$$

$$w_{eff} \Rightarrow \downarrow$$

★ $R.B \uparrow \downarrow \Rightarrow W.B \uparrow \downarrow$

① $w_{eff} \Rightarrow \downarrow$

② Conc. gradient \uparrow

$I_E \uparrow$

Less Recombination $\Rightarrow \alpha \uparrow$


$$I_C = \alpha I_E + I_{CBO}$$

$\alpha \uparrow \quad I_C \uparrow$


Reverse Biased Diode

Date _____
Page _____

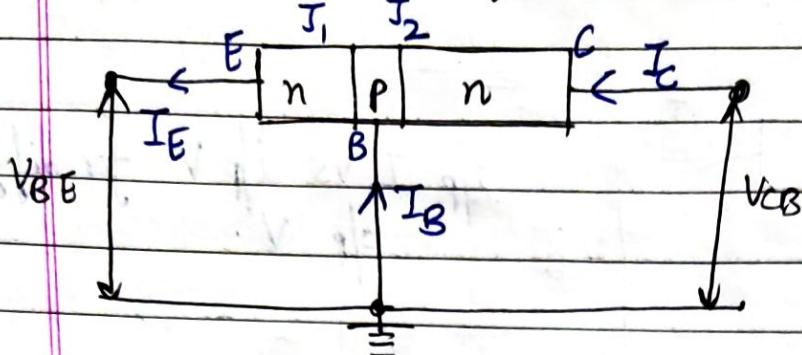Common Base Transistor [Output Characteristics]



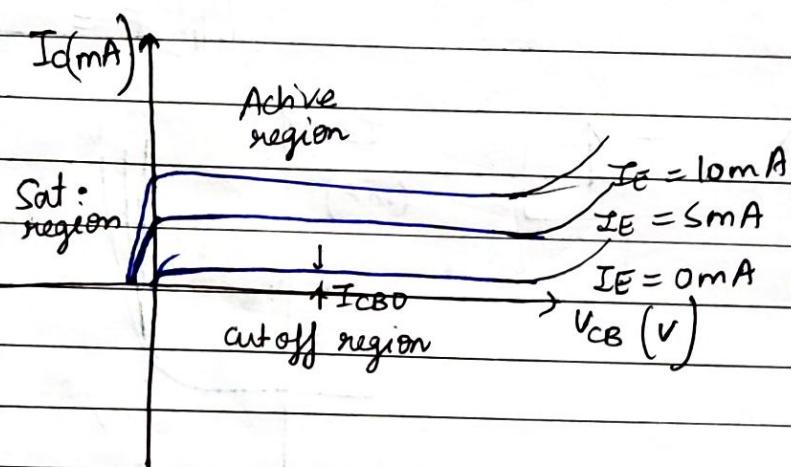O/p I (I_C) Vs O/p V (V_{CB}) for various levels of i/p I (I_E).



$$I_C = \alpha I_E + I_{CBO} \quad [\text{independent of } V_{CB}]$$

$$I_C \approx \alpha I_E$$



$I_C \approx I_E$

$$(\alpha = 0.95 - 0.98)$$

\downarrow \downarrow

O/p i/p

Transistor Amplifying Action :-

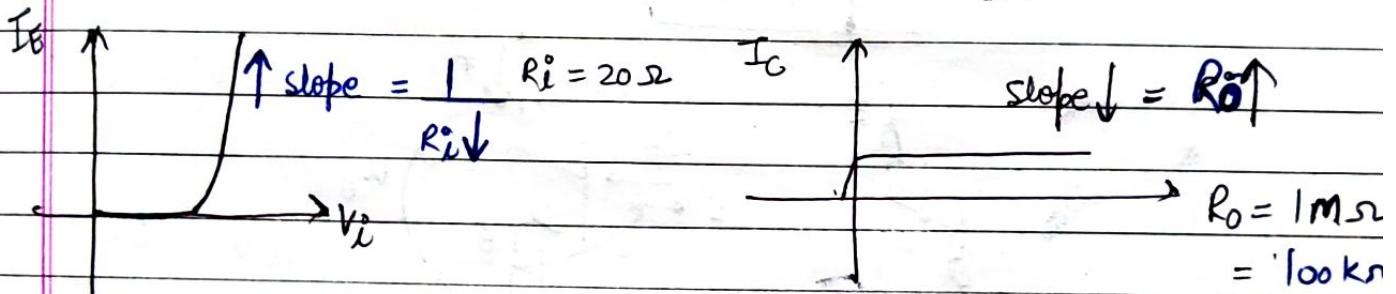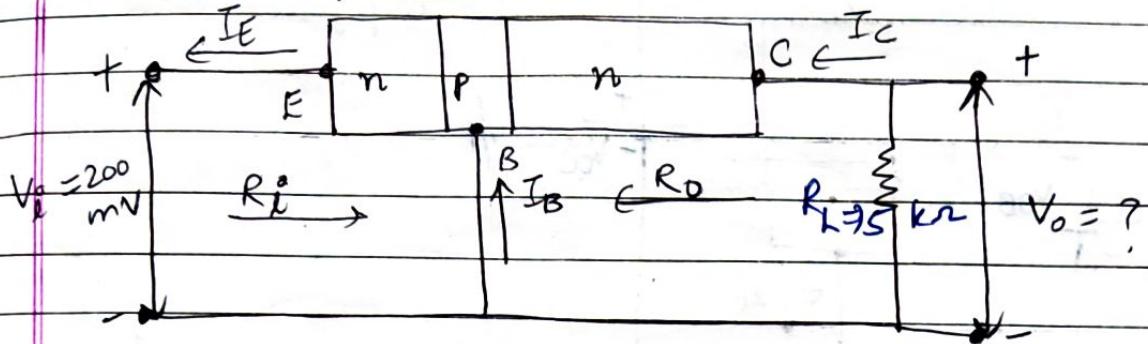

$$V_i = I_E R_i$$

$$V_i = I_E R_i \Rightarrow I_E = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} \Rightarrow 10 \text{ mA}$$

$$I_c = \alpha I_E + I_{cBO}$$

$$I_c \approx \alpha I_E$$

$$I_e = I_E$$

$$I_c = 10 \text{ mA}$$

$$V_o = I_c R_L$$


$$= 10 \text{ mA} \times 5 \text{ k}\Omega$$

$$V_o \Rightarrow 50 \text{ V}$$


$$\text{Voltage Amplification : } A_v = \frac{V_o}{V_i} = \frac{50 \text{ V}}{200 \text{ mV}} \Rightarrow 50$$

Common-Emitter Configuration of Transistor :-

Data
Page

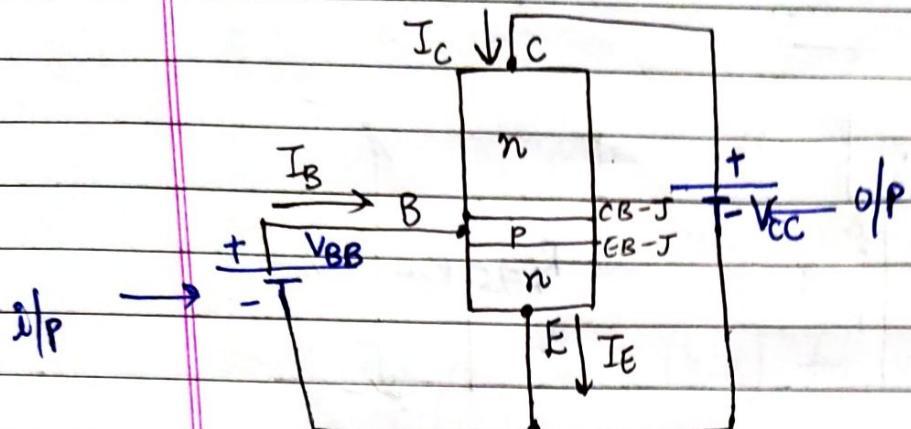

Amplifier \Rightarrow Active Mode

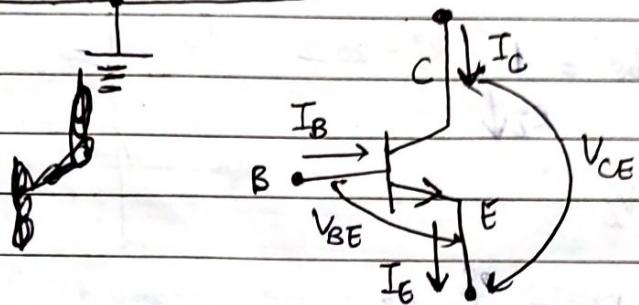

i/p current $\rightarrow I_B$

i/p voltage $\rightarrow V_{BE}$

o/p current $\rightarrow I_C$

o/p voltage $\rightarrow V_{CE}$

$$I_E = I_C + I_B \quad \text{---} \textcircled{1}$$

$$I_C = \alpha I_E + I_{CBO} \quad \text{---} \textcircled{11}$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$I_C = \alpha I_C + \alpha I_B + I_{CBO}$$

$$1-\alpha$$

$$(1-\alpha)I_C = \alpha I_B + I_{CBO}$$

$$\beta + 1 = \frac{\alpha}{1-\alpha} + 1 \neq 1$$

$$I_C = \left(\frac{\alpha}{1-\alpha} \right) I_B + I_{CBO}$$

$$\frac{1}{\beta+1}$$

$$I_C = \beta I_B + (1+\beta) I_{CBO}$$

$$I_{CEO}$$

Case (I) :-

$$\alpha = 0.98$$

$$\rightarrow \alpha < 1$$

$$\beta = \frac{0.98}{1-0.98} \Rightarrow 49$$

$$\rightarrow 50 < \beta \leq 400$$

Case (II) :-

$$\alpha = 0.95$$

$$\beta = \frac{0.95}{1-0.95} \Rightarrow \frac{0.95}{0.05} \Rightarrow 19$$

$$I_c = \beta I_B + \underbrace{(\beta+1) I_{CEO}}_{I_{CEO}}$$

$$I_c = \beta I_B + I_{CEO}$$

$$I_{CEO} \ll \beta I_B$$

$$I_c = \beta I_B$$

$$\boxed{\beta = \frac{I_c}{I_B}}$$

Current Amplification factor

$$I_B = 1 \text{ mA}$$

$$\beta = 100$$

$$I_c = \beta I_B$$

$$I_c = 100 \text{ mA}$$

- Common Emitter config. works as Current Amplifier.

Note :- $I_c = \alpha I_E + I_{CEO}$

$$I_c = \beta I_B + (\beta+1) I_{CEO}$$

Let $\beta = 99$ $(\beta+1) \Rightarrow 100$

Common Base


Common

- Contribution of leakage current to the output current is more in case of Common emitter config. and contribution of leakage current to the output current is less in case of common base configuration.

Forward Biased
↑ Diode

Common Emitter Transistor [Input characteristic]


Date _____
Page _____

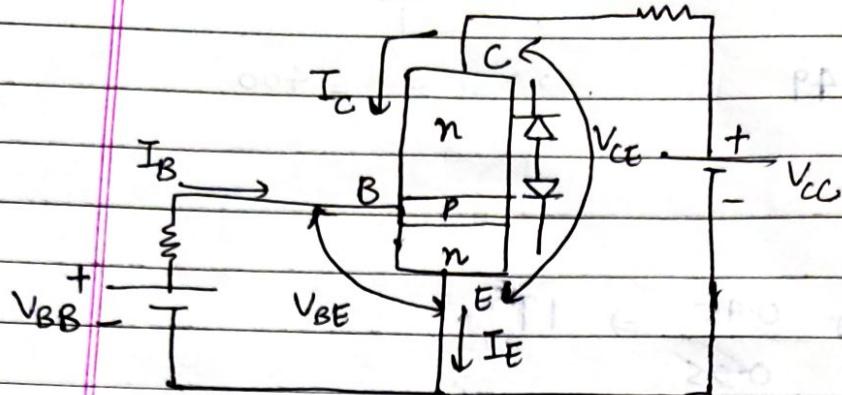

i/p voltage =

→ I_B vs V_{BE} for diff. values of V_{CE}

i/p current $I_B(\text{diff})$

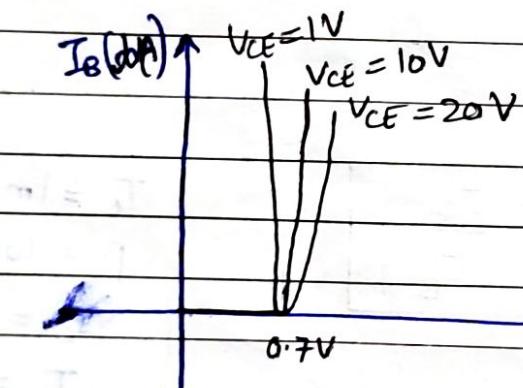

$$V_{CE} = V_{CB} + V_{BE}$$


$V_{CE} \uparrow \Rightarrow V_{CB} \uparrow \Rightarrow I_B \downarrow$ (Less Recombination
(By Early effect)

$V_{CE} \downarrow \Rightarrow I_B \uparrow$
 $V_{CE} \uparrow \Rightarrow I_B \downarrow$

Common Emitter Transistor [Output characteristic]

Date _____
Page _____

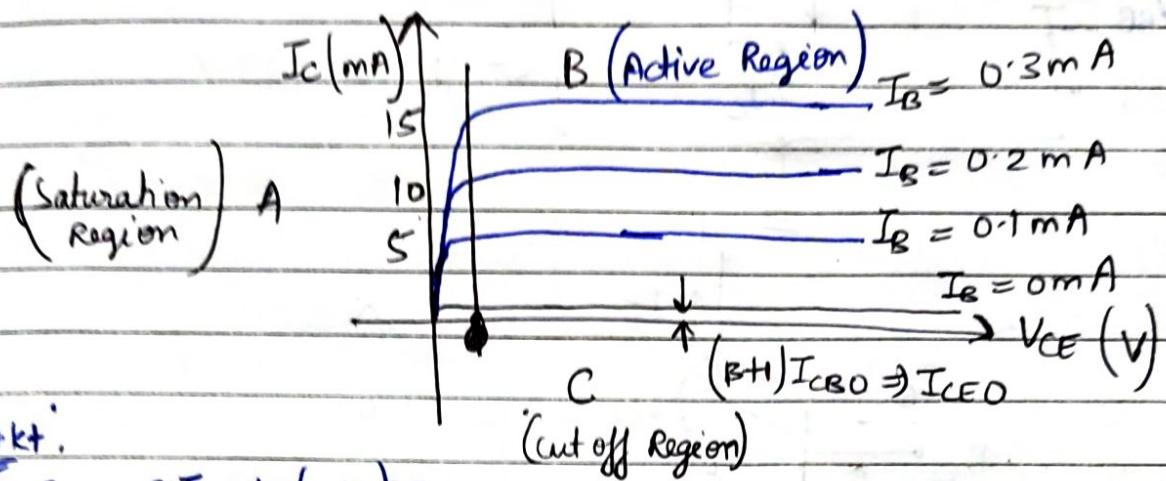I_c vs V_{CE} for different levels of I_B
 (output current) (Input current)
 ↓
 (output voltage)



$$I_c = \beta I_B + (\beta+1)I_{cBO}$$

$$I_B = 0$$

$$I_c = (\beta+1)I_{cBO}$$



$$\beta = \frac{\Delta I_c}{\Delta I_B} \Rightarrow \frac{10 - 5}{0.2 - 0.1} = 50$$

$$\beta \Rightarrow 50$$

- | |
|--|
| $\left\{ \begin{array}{l} A \rightarrow \text{Saturation Region} \\ B \rightarrow \text{Active Region} \\ C \rightarrow \text{Cut off Region} \end{array} \right.$ |
|--|

Common-Collector Configuration of Transistor

Date _____
Page _____

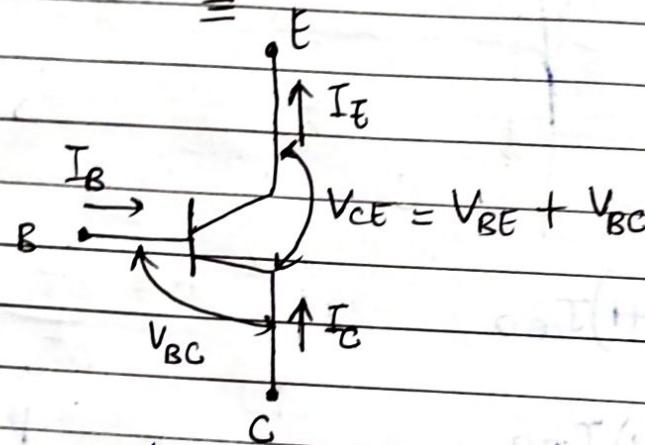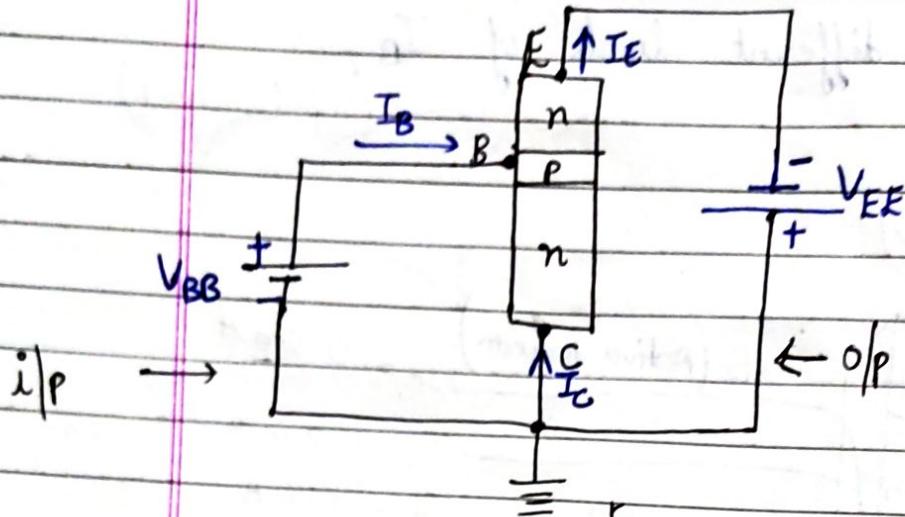

I_E vs V_{CB} for various levels of I_B

$$I_c = \alpha I_E$$

$$\alpha = 0.95 - 0.98 \approx 1$$

$$I_c \approx I_E$$

~~JMP~~ o/p char. of CE \Rightarrow o/p char. of CC

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$I_E = I_c + I_B \rightarrow \textcircled{I}$$

$$I_c = \alpha I_E + I_{CBO} \rightarrow \textcircled{II}$$

Current
Amplification factor

$$I_E = \alpha I_E + I_{CBO} + I_B$$

$$(1-\alpha) I_E = I_B + I_{CBO}$$

$$I_E = \frac{1}{(1-\alpha)} I_B + \frac{1}{(1-\alpha)} I_{CBO}$$

$$I_E \approx \gamma I_B + \gamma I_{CBO}$$

RELATION B/W α , β and V^o

1.00

9

0

1

Date _____
Page _____

$$\alpha_{dc} \Rightarrow \frac{I_C}{I_E}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\alpha \Rightarrow \alpha_{ac} \Rightarrow \frac{\Delta I_C}{\Delta I_E} \quad | \quad V_{CB} = \text{const.}$$

$$\beta \Rightarrow \frac{0.99}{1-0.99}$$

$$\beta = \frac{0.99}{0.01}$$

$$\beta \Rightarrow \beta_{dc} \Rightarrow \frac{I_C}{I_B}$$

$$\alpha \Rightarrow \frac{I_C}{I_E}$$

$$\beta \Rightarrow \beta_{ac} \Rightarrow \frac{\Delta I_C}{\Delta I_B} \quad | \quad V_{CE} = \text{const.}$$

$$\beta = \frac{I_C}{I_B}$$

$$\gamma \Rightarrow V_{dc} \Rightarrow \frac{I_E}{I_B}$$

$$0.99 = \frac{I_C}{I_E}$$

$$\gamma \Rightarrow V_{ac} \Rightarrow \frac{\Delta I_E}{\Delta I_B} \quad | \quad V_{CE} = \text{const.}$$

$$\beta = \frac{I_C}{I_B}$$

$$I_E = I_B + I_C$$

$$\frac{I_E}{I_B} = 1 + \frac{I_C}{I_B}$$

$$V = 1 + \beta$$

$$V = \frac{\alpha}{1-\alpha} + 1$$


$$\beta = \frac{\alpha}{1-\alpha}$$

$$V = \frac{\alpha + 1 - \alpha}{1-\alpha} \Rightarrow \frac{1}{1-\alpha}$$

$$V = \beta + 1 = \frac{1}{1-\alpha}$$

DC Biasing, Load Line & Operating point / Q-Point of Transistors :-

Common Emitter

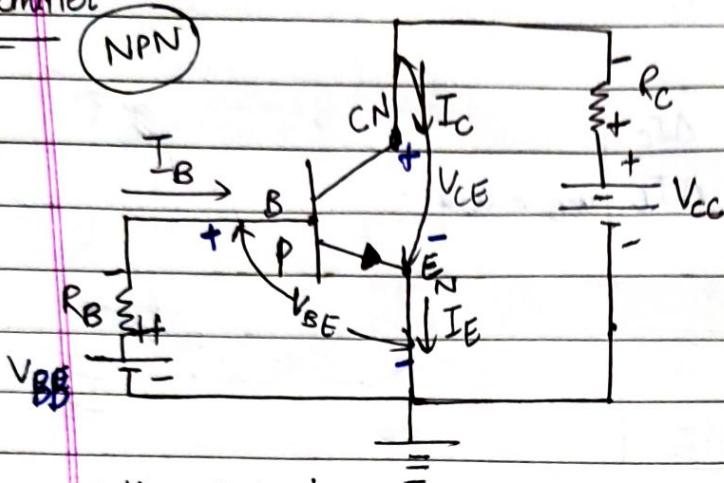


Q point :- Quiescent Point
when no ac signal applied on the base junction, condⁿ called as Q-point.

Active Region:

$$\begin{aligned} EB &\rightarrow F.B \\ CB &\rightarrow R.B \end{aligned}$$

$$I_F = I_B + I_C$$

Output Characteristics:

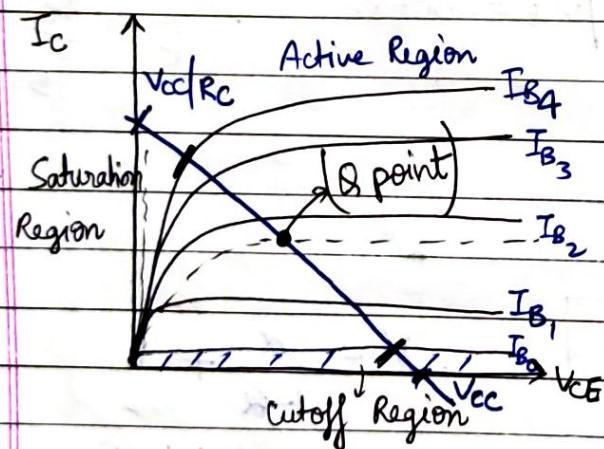

i/p section :

$$+V_{BB} - I_B R_B - V_{BE} = 0$$

$$+I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

0.7V
(si)

$$I_B \approx \frac{V_{BB}}{R_B}$$

On y-axis :

$$V_{CE} = 0$$

$$V_{CC} - I_C R_C - 0 = 0$$

$$I_C = \frac{V_{CC}}{R_C}$$

$$+V_{CC} - I_C R_C - V_{CE} = 0$$

eqⁿ of st. line

$$y = mx + c$$

On x-axis :

$$I_C = 0$$

$$V_{CC} = V_{CE}$$

$$\frac{V_{CC} - V_{CE}}{R_C} = I_C$$

$$C = \frac{V_{CC}}{R_C}$$

$$I_C = \frac{V_{CC}}{R_C} - \frac{V_{CE}}{R_C}$$


$$m = -\frac{1}{R_C}$$

$$y = C + mx$$


\therefore Thevenin's Theorem :- "A linear and bidirectional two-terminal network can be replaced by an equivalent network consisting of a voltage source V_{th} connected in series with R_{th} ".

- Thevenin resistance - R_{th} equivalent network consisting of a voltage source V_{th} connected in series with R_{th} .
- Thevenin Voltage - V_{th} - All the voltage source are short circuited and current source are open circuited.
- V_{th} - Open circuit voltage across the terminal.

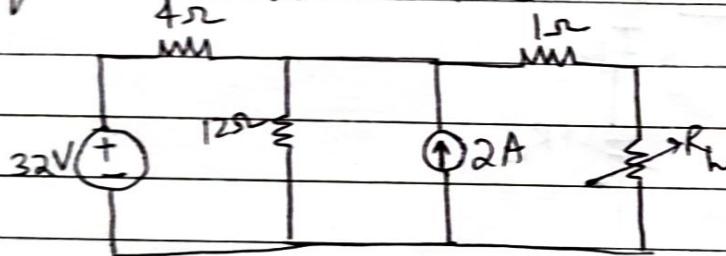Q:- find current flowing through the load resistance when it is equal to 6Ω and 16Ω .



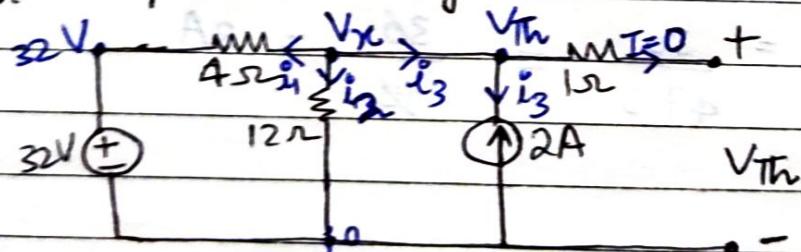Sol:- 1. V_{th} :- Open circuit voltage across the terminal.



$$\text{from KCL} \rightarrow i_1 + i_2 + i_3 = 0$$

$$\frac{V_x - 32}{4} + \frac{V_x - 0}{12} + (-2) = 0$$

$$3V_x - 96 + V_x = 24$$

$$\Delta V_x = 126 \text{ V}$$


$$\boxed{V_x = 30 \text{ V}}$$

$$\text{W.K.T} \therefore V_{th} = V_x$$

$$\boxed{V_{th} = 30 \text{ V}}$$

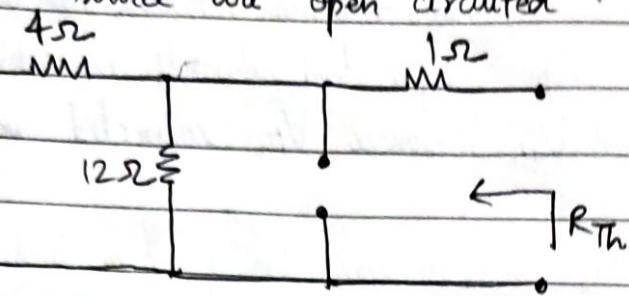2.


R_{Th} :- All the voltage source are short circuited and current source are open circuited.



$$R_{Th} = 4 \parallel 12 + 1$$

$$R_{Th} = \frac{4 \times 12}{4 + 12} + 1 \Rightarrow 4\Omega$$

Thevenin's Eq. circuit :-

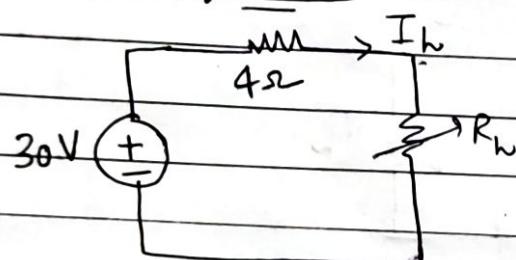


i) $R_L = 6\Omega$

$$I_L = \frac{30}{4+6} = \frac{30}{10} = 3A$$

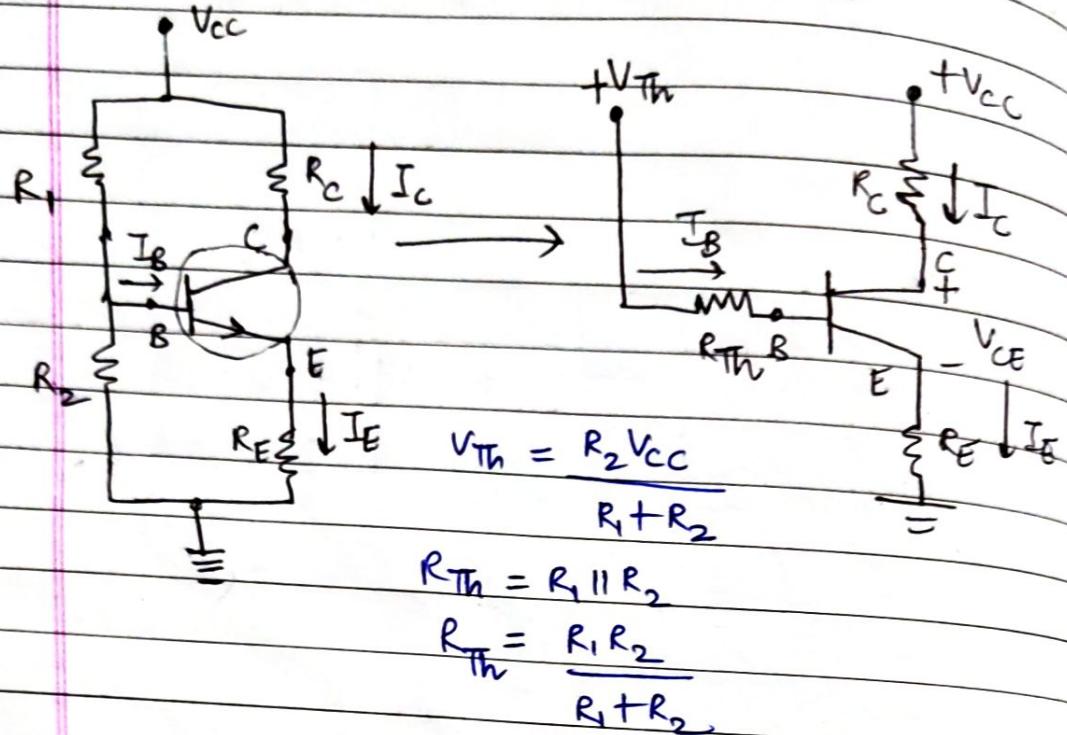ii) $R_L = 16\Omega$

$$I_L = \frac{30}{4+16} \Rightarrow \frac{30}{20} \Rightarrow 1.5A$$

Stability factor for Voltage Divider Biasing



Step ① $I_B = ?$

Step ② $I_c = \beta I_B + (\beta + 1) I_{EBQ}$

Step ③ Diff. wrt to I_c keeping β & V_{BE} const.

→ Stability factor does not depend on V_{cc} . So replacing V_{cc} with V_{Th} will have no effect.

$$S = \frac{(\beta + 1) \left(\frac{R_{Th}}{R_B + R_E} \right)}{\frac{R_B}{R_{Th}} + (\beta + 1) R_E}$$

$$S = \frac{(\beta + 1) (R_{Th} + R_E)}{R_{Th} + (\beta + 1) R_E}$$

S.F for V.D.B

$$S' = -\beta$$


$$R_{Th} \leftarrow \frac{(\beta + (\beta+1)R_E)}{R_E}$$

$$\boxed{S' = \frac{-\beta}{R_{Th} + (\beta+1)R_E}}$$

V.D.B


Voltage-Divider Bias Configuration :-

Accurate Analysis

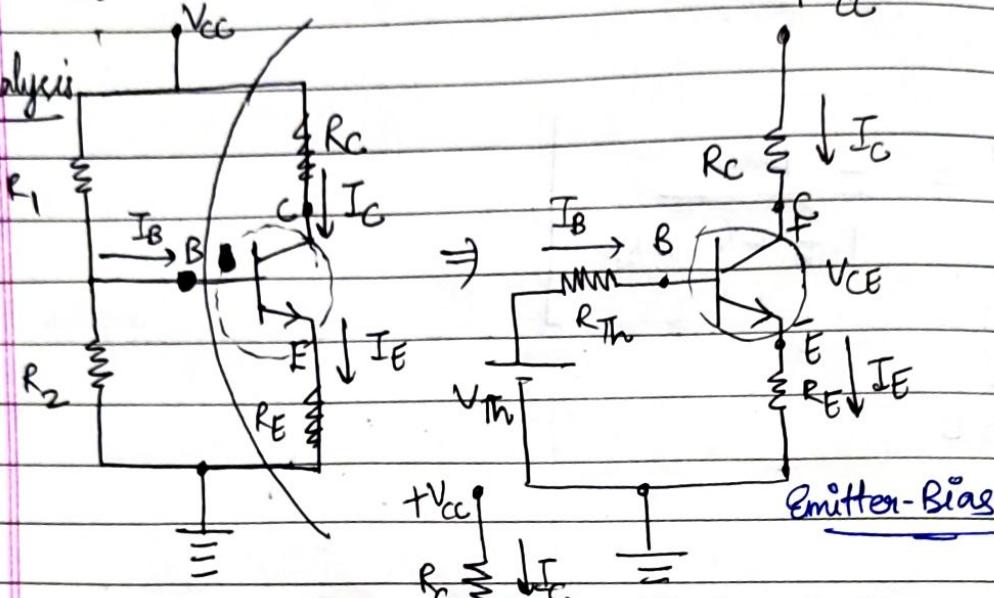

Emitter-Bias

R_{Th} , V_{Th}

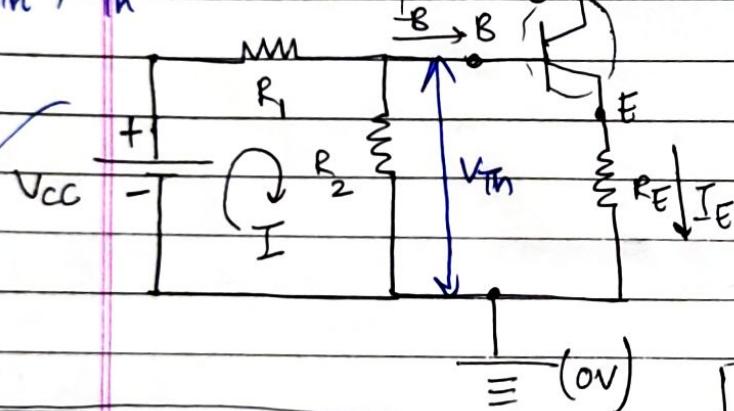

Eqn for input :-

$$V_{Th} - I_B R_{Th} - V_{BE} - I_E R_E = 0$$

$$V_{Th} - I_B R_{Th} - V_{BE} - (\beta + 1) I_E R_E = 0$$

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}$$

$$I_C = \beta I_B = \beta \left(V_{Th} - V_{RE} \right)$$

$$R_{Th} + (\beta + 1) R_E$$

$$I_E \quad [R_{Th} \ll (\beta + 1) R_E]$$

then I_C is independent
of β .

Eqn for output :-


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$I_E \approx I_C$$

$$V_{CC} - I_C (R_C + R_E) - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

R_{Th}

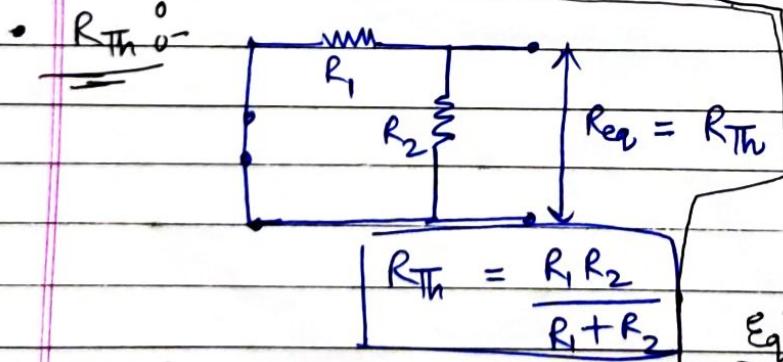


$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$


V_{Th}

$$I = \frac{V_{CC}}{R_1 + R_2}$$
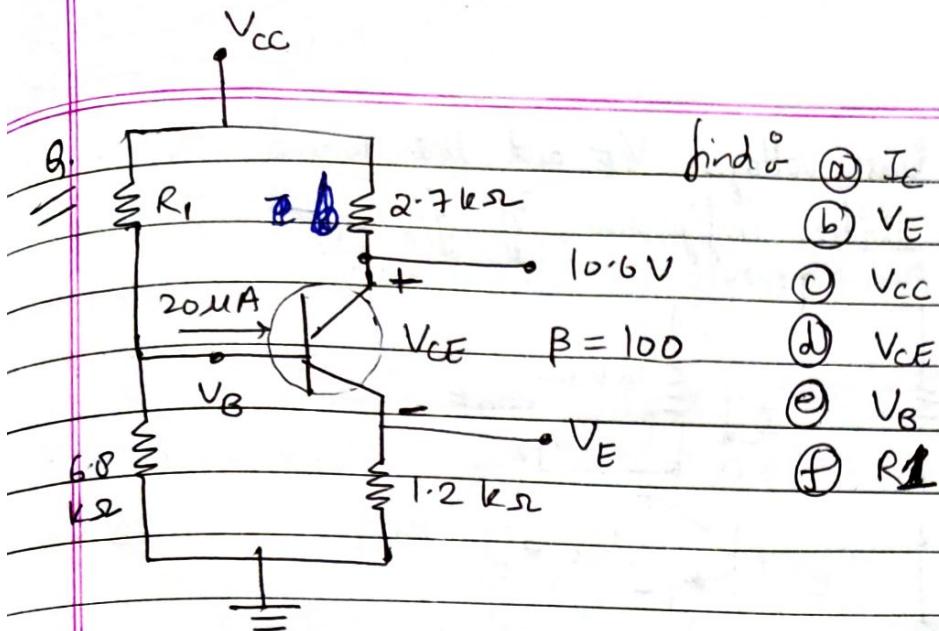
$$V_{Th} = IR_2 = \frac{R_2 V_{CC}}{R_1 + R_2}$$



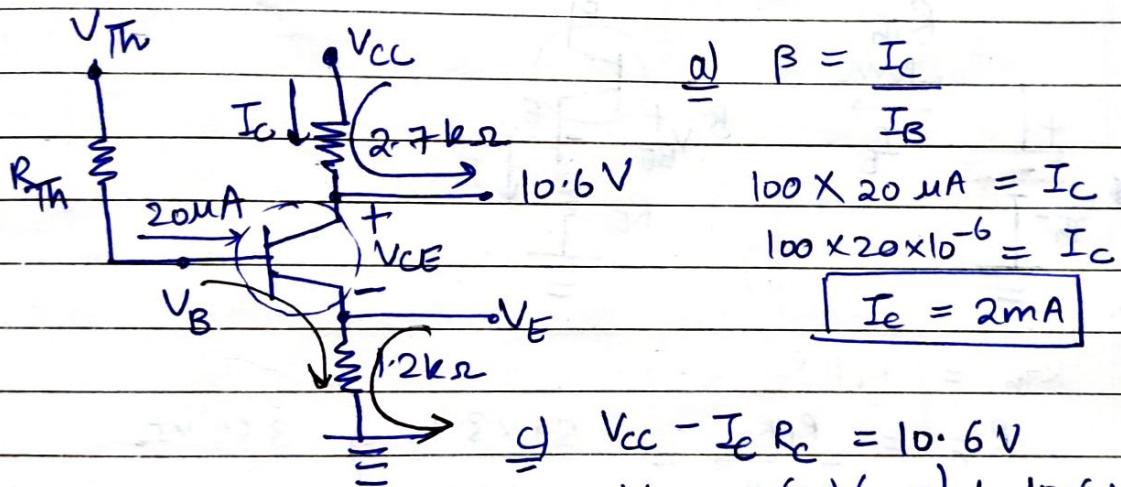Sol: Given: $I_B = 20 \mu A$, $V_C = 10.6 V$, $R_c = 1.2 k\Omega$
 $\beta = 100$, $R_E = 2.7 k\Omega$, $R_B = 6.8 k\Omega$



b) $I_E = I_B + I_C$
 $I_E \approx I_C$
 $I_E = 2 mA$

$I_E = 2 mA + 20 \mu A$

$I_E = 2 mA + 0.02 mA = 2.02 mA$

diff. $\Rightarrow 0.02 mA$

(f) $V_{TH} = V_B$

$V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2}$



$8.124 \Rightarrow \frac{16 \times 6.8}{R_1 + 6.8 k\Omega}$

(d) $V_{CE} = V_C - V_E$
 $= 10.6 V - 2.424 V$
 $V_{CE} = 8.176 V$

(e) $V_{BE} = V_B - V_E$
 $0.7 V = V_B - 2.424 V$

$V_B = 3.124 V$

Q. Determine the dc bias voltage V_{CE} and the current I_C for the voltage divider configuration of figure (4.35).

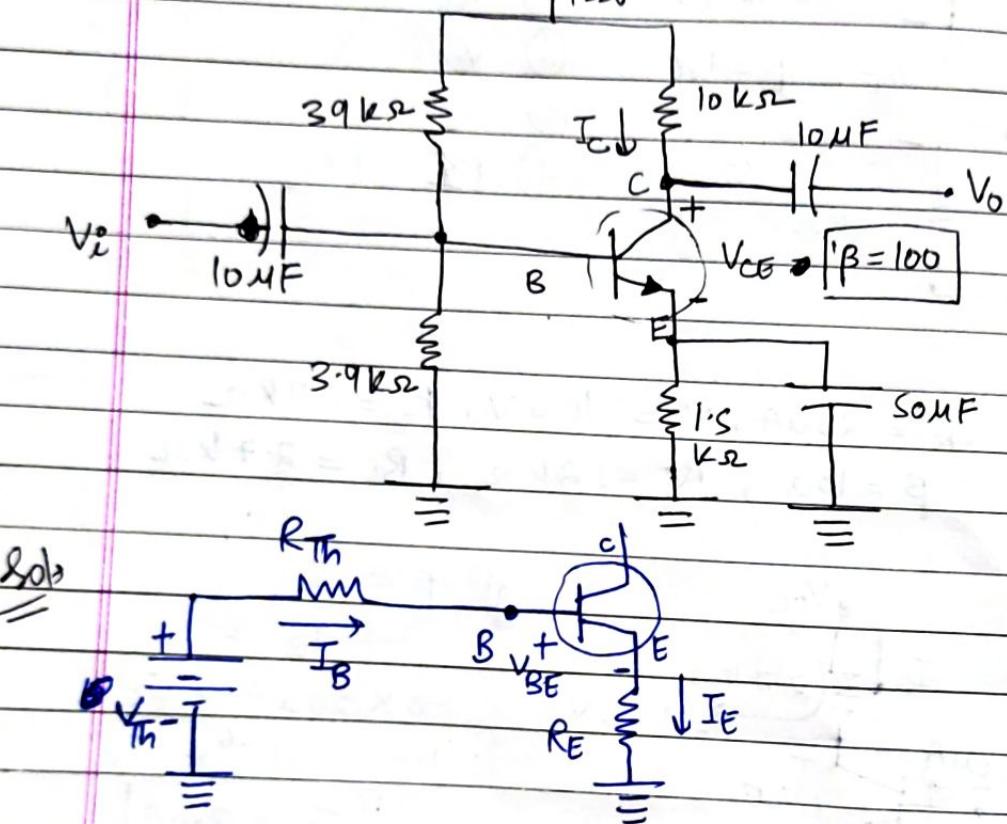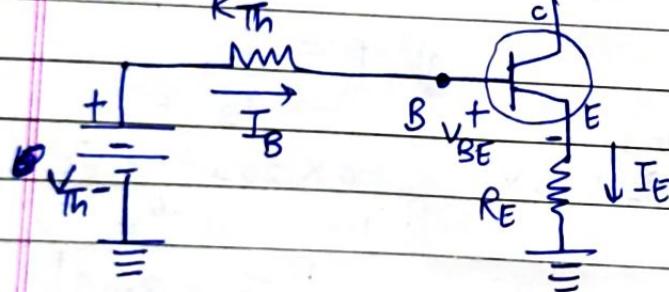
Sols

$$R_{Th} = R_1 \parallel R_2$$

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{3.9 \times 3.9}{3.9 + 3.9} \Rightarrow 3.45 \text{ k}\Omega$$

$$V_{Th} = \frac{R_2 \cdot V_{CC}}{R_1 + R_2}$$

$$I = \frac{V_{CC}}{R_1 + R_2}$$

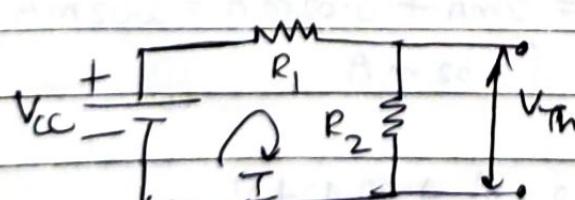

$$V_{Th} = \frac{3.9 \times 22}{3.9 + 3.9}$$

$$\boxed{V_{Th} = 2\text{V}}$$

$$V_{Th} - I_B \times R_{Th} - V_{BE} - I_E R_E = 0$$

$$2 - I_B \times 3.45 - 0.7 - (\beta + 1) 1.5 = 0$$

$$2 - I_B \times 3.45 - 0.7 - (101) 1.5 = 0$$

$$\boxed{I_B = 8.38\text{ mA}}$$

$$\beta = \frac{I_C}{I_B}$$

$$I_C = 100 \times 0.38 \Rightarrow 0.84 \text{ mA}$$

$$I_E = I_B + I_C$$

$$|I_E \approx I_C|$$


~~I_{EBO}~~

$$V_{CC} - I_C R_E - V_{CE} - I_E \times 1.5 = 0$$

$$22 - 0.84 \times 10 - V_{CE} - 0.84 \times 1.5 = 0$$

$$V_{CE} = 12.34 \text{ V}$$

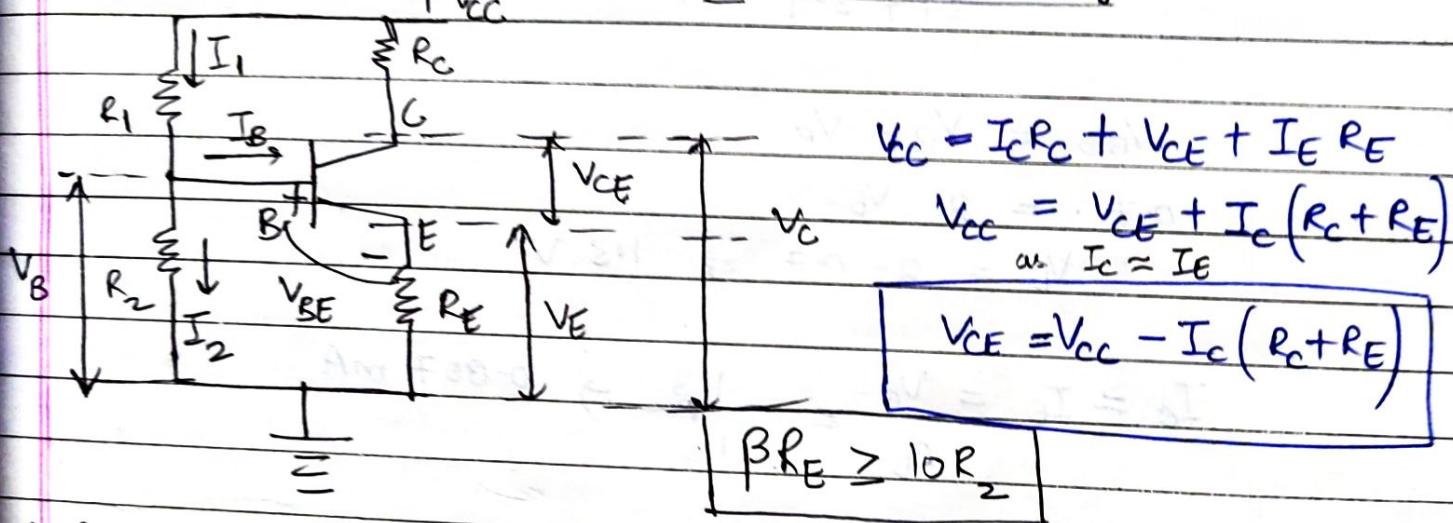Approximate Analysis of Voltage-Divider Biasing :-



* Approximate Analysis :-

$$I_1 = I_2 + I_B$$

$$I_1 \approx I_2$$

$$I_B \approx 0$$

$$V_{BE} = V_B - V_E$$

$$I_E = I_B + I_C$$

$$I_E \approx I_C$$

$$V_{BE} = V_B - I_E R_E$$

$$V_{BE} = V_B - I_C R_E$$

$$I_E = \frac{V_B - V_{BE}}{R_E}$$

$$V_{CC} = I_1 R_1 + I_2 R_2$$

$$V_{CC} = I_1 (R_1 + R_2) \text{ or } I_2 (R_1 + R_2)$$

$$I_1 = I_2 = \frac{V_{CC}}{R_1 + R_2}$$

$$V_B = R_2 I_2$$

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$


Field-Effect Transistors (FETs)

FETs & BJTs

→ FETs are smaller than BJTs

→ BJT → 3 terminal

← FET • Application of FET ≈ App. of BJT

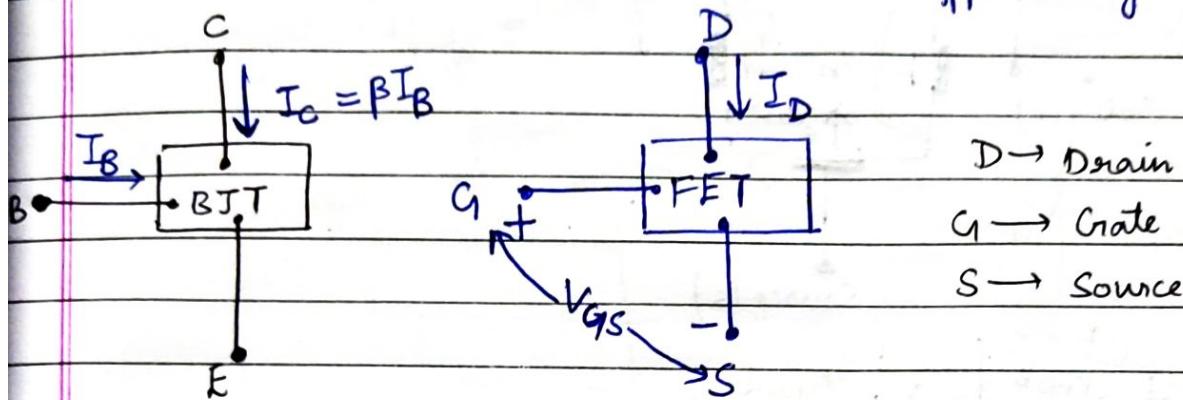

→ BJT is current

→ I_D depends on V_{GS} .

controlled device.

→ FET is voltage controlled device

$$\rightarrow I_C = f(I_B)$$

$$\rightarrow I_D = f(V_{GS})$$

→ BJT → Bipolar

→ FET → Unipolar (e^- or holes)

(e^- & holes both)


→ n-channel & p-channel

→ npn & pnp

e^- holes

→ BJT is used for
amplification & switching

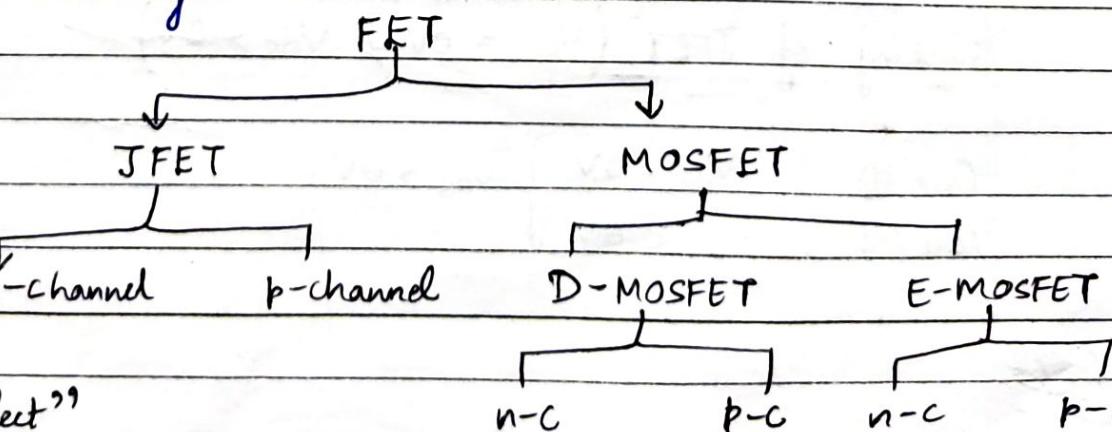→ FET is used for amplification & switching



→ "Field - Effect"

(E-F) developed by the charges present


→ This E-F controls the conduction path of o/p

→ FETs has high input impedance & more temp. stable.

n-channel p-channel

Date _____
Page _____

Construction and Working of JFET :-

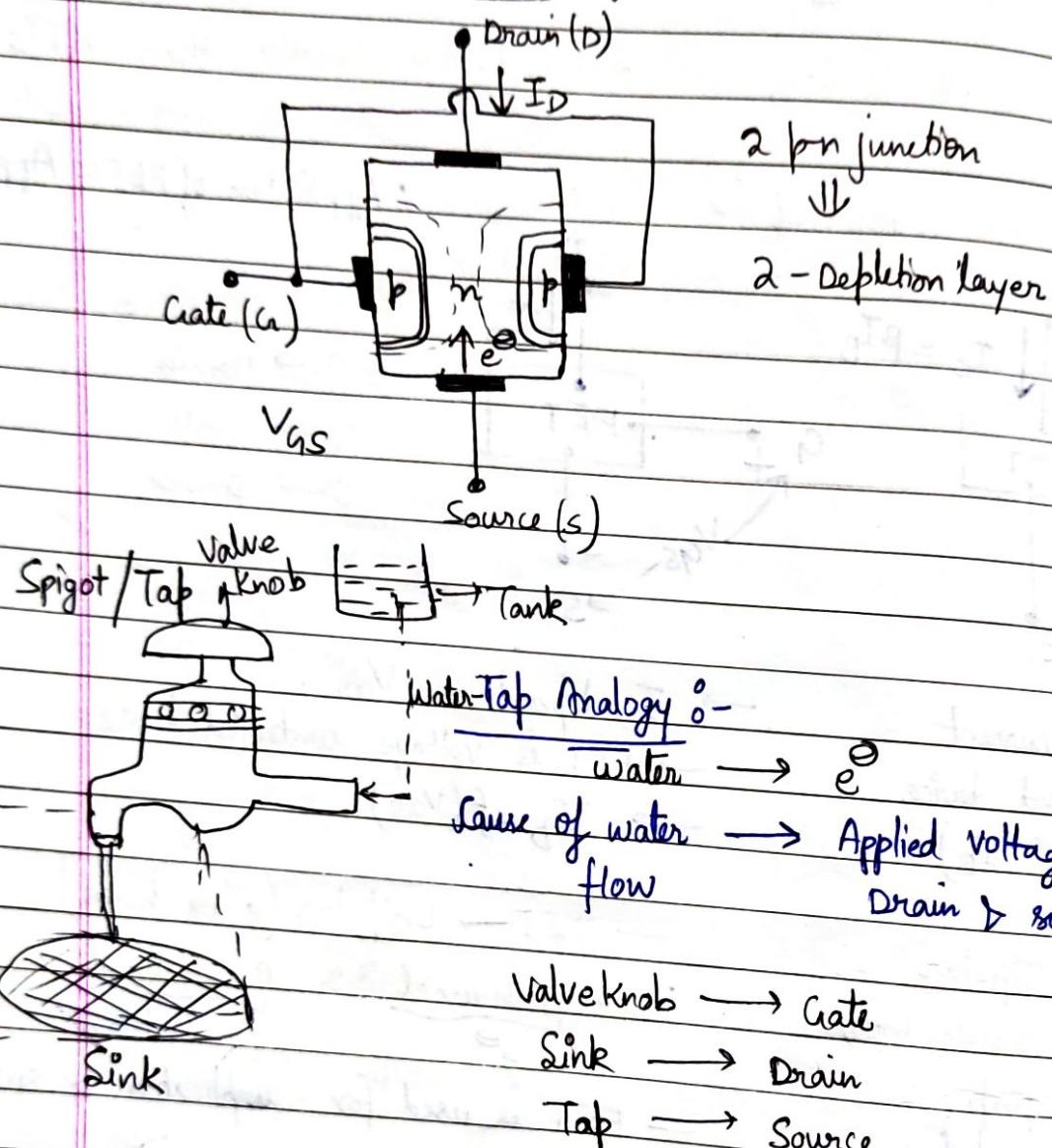


Working of JFET ($V_{GS} = 0V$ & $V_{DS} > 0V$)

Case ① : $V_{GS} = 0V$ } $V_{DS} > 0V$
 Case ② : $V_{GS} < 0V$ }



(Scribble)

Case ① $V_{GS} = 0V$, $V_{DS} > 0V$

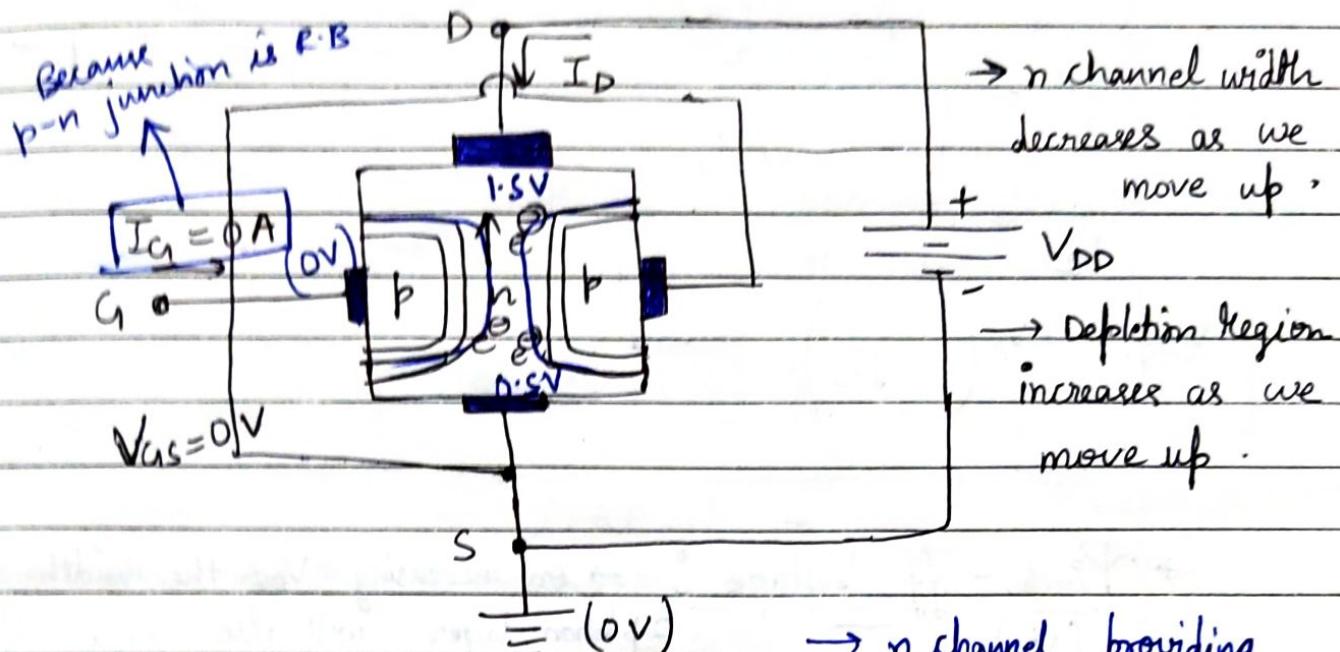

$$V_{DS} = V_{DD} > 0$$

\rightarrow Symbol

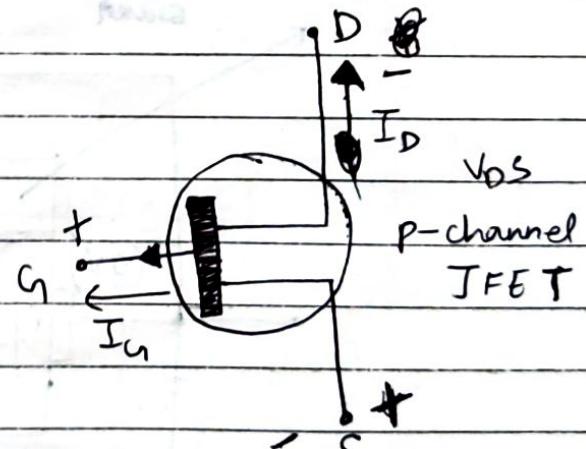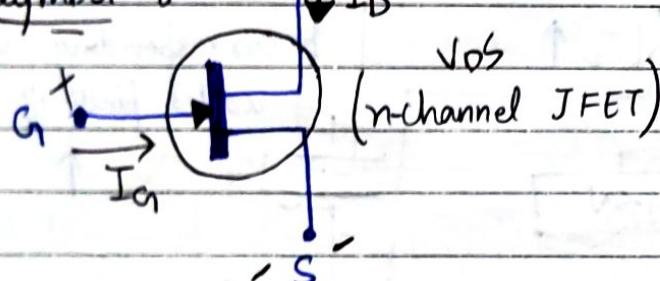

Rough work:

$$\gamma_d = \frac{\gamma_0}{\left(1 - \frac{V_{GS}}{V_p}\right)^2}$$

$$2\gamma_0 = \gamma_0$$

$$\left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$\gamma_d = \frac{\gamma_0}{\left(1 - \frac{1}{2}\right)^2}$$

$$\boxed{\gamma_d = 4\gamma_0}$$

$$\left(1 - \frac{V_{GS}}{V_p}\right)^2 = \frac{1}{4}$$

$$1 - \frac{V_{GS}}{V_p} = \frac{1}{2}$$

$$I_d \Rightarrow \left(1 - \frac{2}{-8}\right)^2 \\ \Rightarrow \left(1 - \frac{-1}{4}\right)^2$$

Date _____
Page _____

$$I_D = I_{DSS} \left(1 - \frac{V_{DS}}{V_p}\right)^2 \Rightarrow \left(1 + \frac{1}{4}\right) \Rightarrow \left(\frac{5}{4}\right)^2$$

$$\Rightarrow \frac{25}{16} \Rightarrow 1.5$$


$$\frac{1}{2} = \left(1 - \frac{V_{DS}}{V_p}\right)^2$$

$$\frac{1}{2} = 1 - \frac{V_{DS}}{V_p}$$

$$V_{DS} = V_p \left(1 - \frac{1}{2}\right)$$

→ Pinch-off Voltage $\stackrel{\circ}{\rightarrow}$ → on increasing V_{DS} the width of depletion layer will also increase if V_{DS} increases upto the level when two depletion layers touching each other.

p-n junction is reverse biased

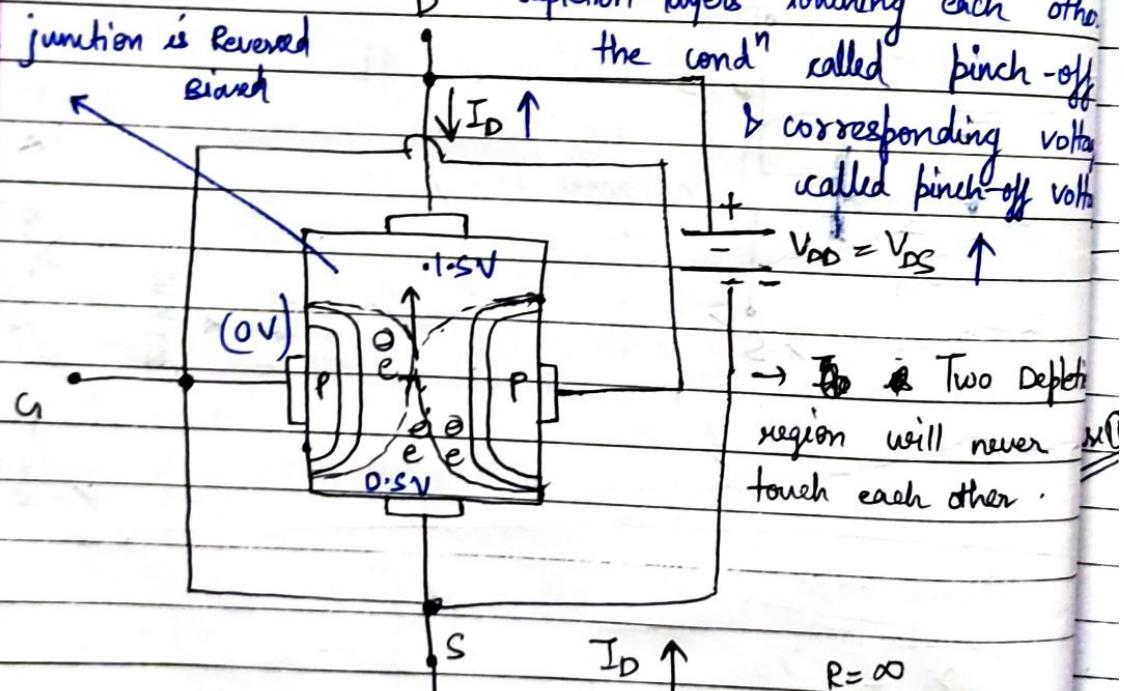


→ for explanation purpose only

$$2V \\ 1.5V \\ 1V \\ 0.5V \\ 0V$$

$$R_{eq} = 4\gamma$$

$$\text{let } V_{DD} = 2V$$
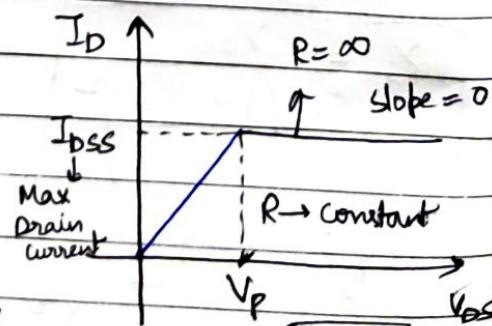
$$2V \rightarrow 4\gamma \text{ or } \gamma = 0.5V$$



$I_{DSS} \rightarrow$ defined for $V_{DS} = 0V$


& $|V_{DS}| > |V_p|$

JFET as a Current source

- Effect on Depletion Region } when $V_{DS} > V_p$
- Effect on I_D }

→ When $V_{DS} > V_p$, the width of D-R increases along the length of the n-channel.

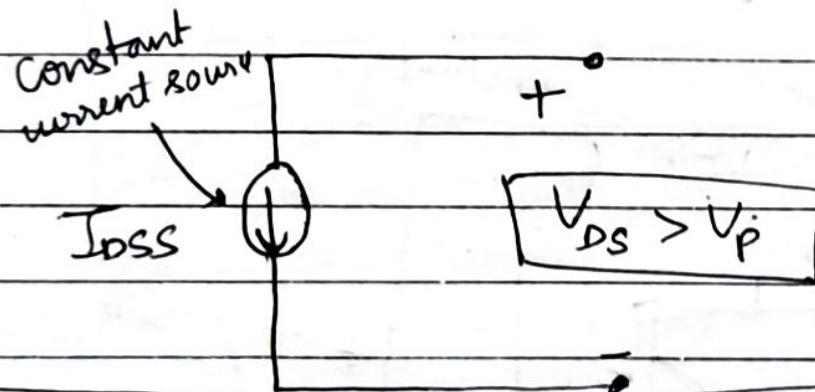- $I_D = I_{DSS}$ when $V_{DS} > V_p$ & $V_{DS} < V_{DS\ max}$
- ↓
- JFET act as a constant current source.
- Breakdown word^n
- When ~~V_{DS}~~



Date _____ Page _____

Working of JFET [Negative Voltage at GATE]

Case(I)

$$V_{GS} = 0V$$

$$V_{DS} > |V_p| \text{ then}$$

$$I_D = I_{DSS}$$

$$\text{and } V_{DS} = V_{DD} > DV$$

Max. Drain current

Case(II)

$$V_{GS} < 0V$$

$$\& V_{DS} = V_{DD} < V_{DD}$$

Obtain the Saturation at lower value of V_{DS}


$$I_{DSS} \times$$

$I_D \rightarrow$ constant with change in V_{DS}

$$I_D \neq I_{DSS}$$

$$V_{DS} \downarrow$$

V_{GS} more (-ve)

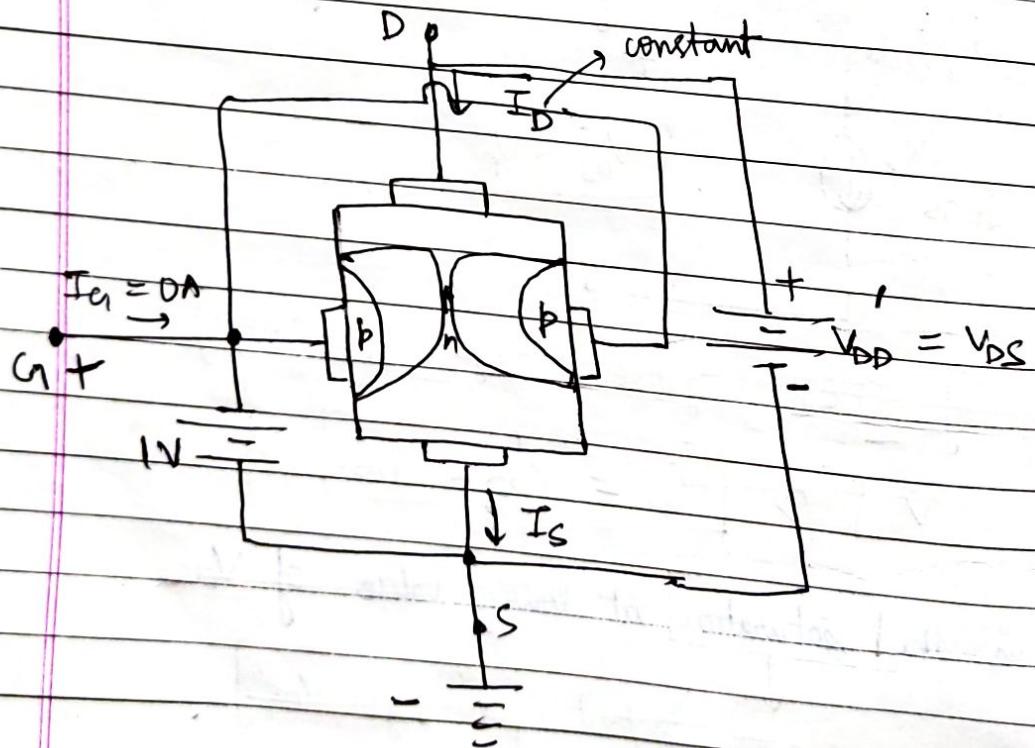

n-channel Output or Drain characteristic of JFET :-

Date _____
Page _____

CE Transistor:

I_C vs V_{CE}
dc current output voltage

for different I_D (drain current)

(controlling current)

active region | Pinch off

| saturation region

Pinch off voltage

(controlling) voltage

JFET :-


I_D vs V_{DS}

output

of p voltage

current for different

levels of V_{GS} (p voltage)

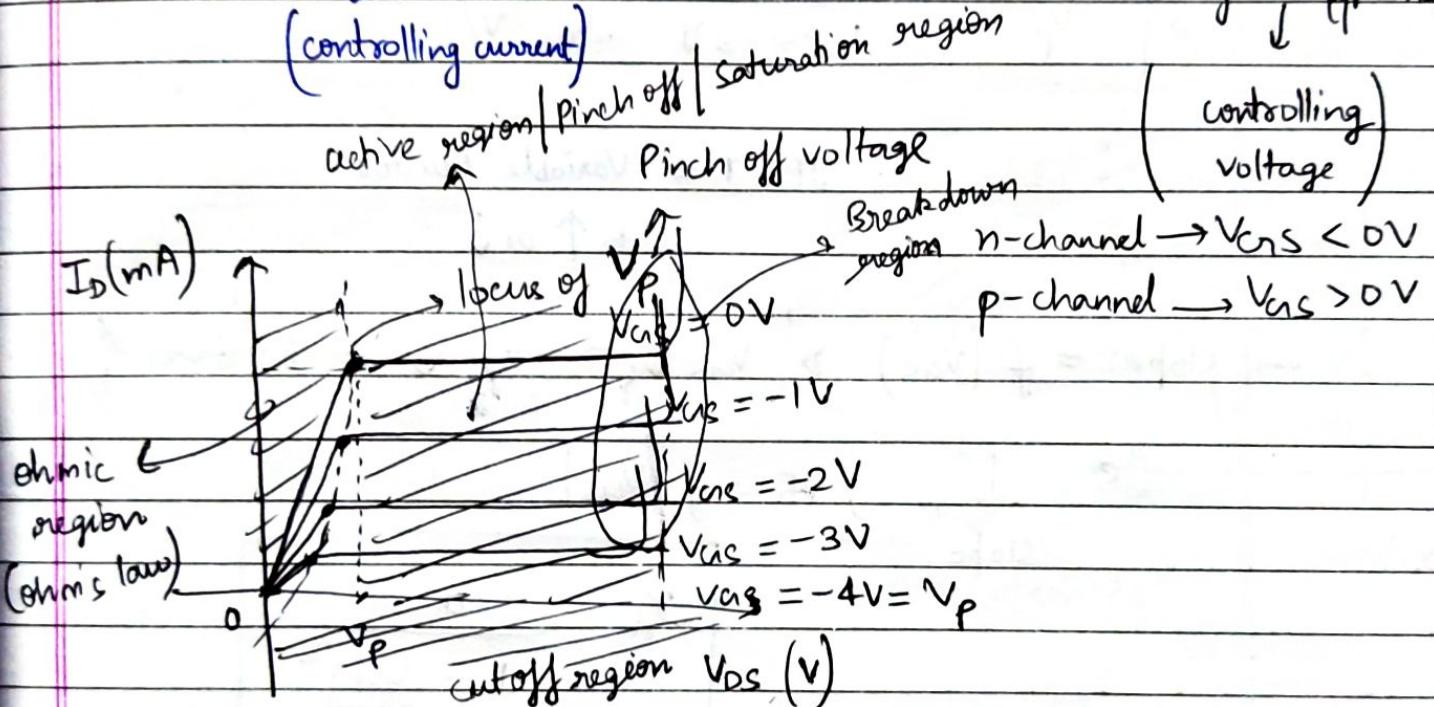

Case ① $I_{DSS} = 8 \text{ mA}$

$V_p = -4 \text{ V}$

$V_{GS} = 0 \text{ V}$

$V_{DS} > |V_p|$

Case ② $V_{GS} = -1 \text{ V}$

Case ③ $V_{GS} = -2 \text{ V}$

Case ④ $V_{GS} = -3 \text{ V}$

Case ⑤ $V_{GS} = -4 \text{ V}$

n-channel $\rightarrow +ve$
p-channel $\rightarrow -ve$ } $\nabla B \uparrow = D.L \uparrow$


Pinch off - voltage obtained
early

JFET as Voltage-Controlled Resistor

Date _____
Page _____

Rec.

Resist.

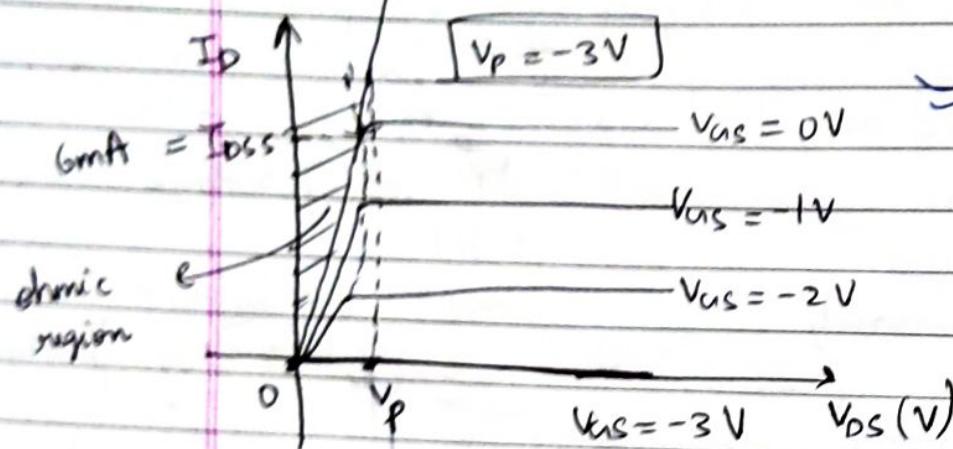

- ① Ohmic \Rightarrow Voltage control
- ② Sat.
- ③ cut-off
- ④ Breakdown

JFET \Rightarrow Variable Resistor

$R \uparrow \text{ or } \downarrow$

$\rightarrow \text{slope} = f(V_{GS}) \Rightarrow V_{GS} \downarrow \Rightarrow \text{slope} \downarrow \Rightarrow R \uparrow$

$$R = \frac{1}{\text{slope}} \Rightarrow R = f(V_{GS})$$

$$\boxed{\gamma_d = \gamma_0 \left(1 - \frac{V_{GS}}{V_p}\right)^2}$$

* $\left\{ \begin{array}{l} V_{GS} \ll 0V \\ R \text{ of JFET} \uparrow \end{array} \right\}$

Ex: $\gamma_0 = 10 \text{ k}\Omega \rightarrow \text{when } V_{GS} = 0V$

$$V_p = -6V$$

$$V_{GS} = -3V$$

$$\gamma_d = \frac{10}{\left(1 - \frac{(-3)}{(-6)}\right)^2} \Rightarrow 40 \text{ k}\Omega$$

$$\begin{aligned} I_D &\Rightarrow I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 \\ I_D &\Rightarrow 2 \left(1 - \frac{f^2}{f_0^2}\right)^2 \Rightarrow 2 \left(1 - \frac{1}{2}\right)^2 \\ &\Rightarrow 2 \times \frac{1}{4} \end{aligned}$$


Transfer characteristics of JFET :-

Date _____
Page _____

Q: what is Transfer characteristic ?

~~Op I~~ → ~~Op V~~

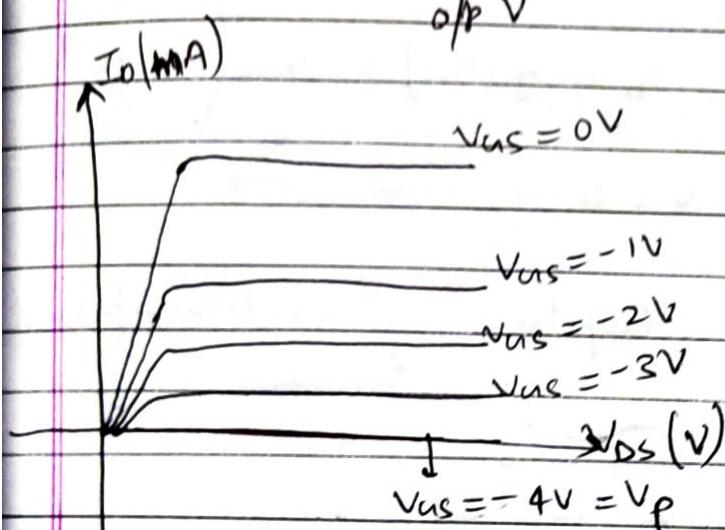Ans I_o vs V_{ds} plot
keeping $V_{gs} \rightarrow$ constant



BJT :-

$$I_c = f(I_B)$$

$$I_C = \beta I_B$$

linear \downarrow
eq n constant

controlled variable


JFET 6-

$$I_D = f(V_{DS})$$


$$I_D = I_{DSS} \left(1 - \frac{V_{DS}}{V_P} \right)^2$$

non-linear eqⁿ
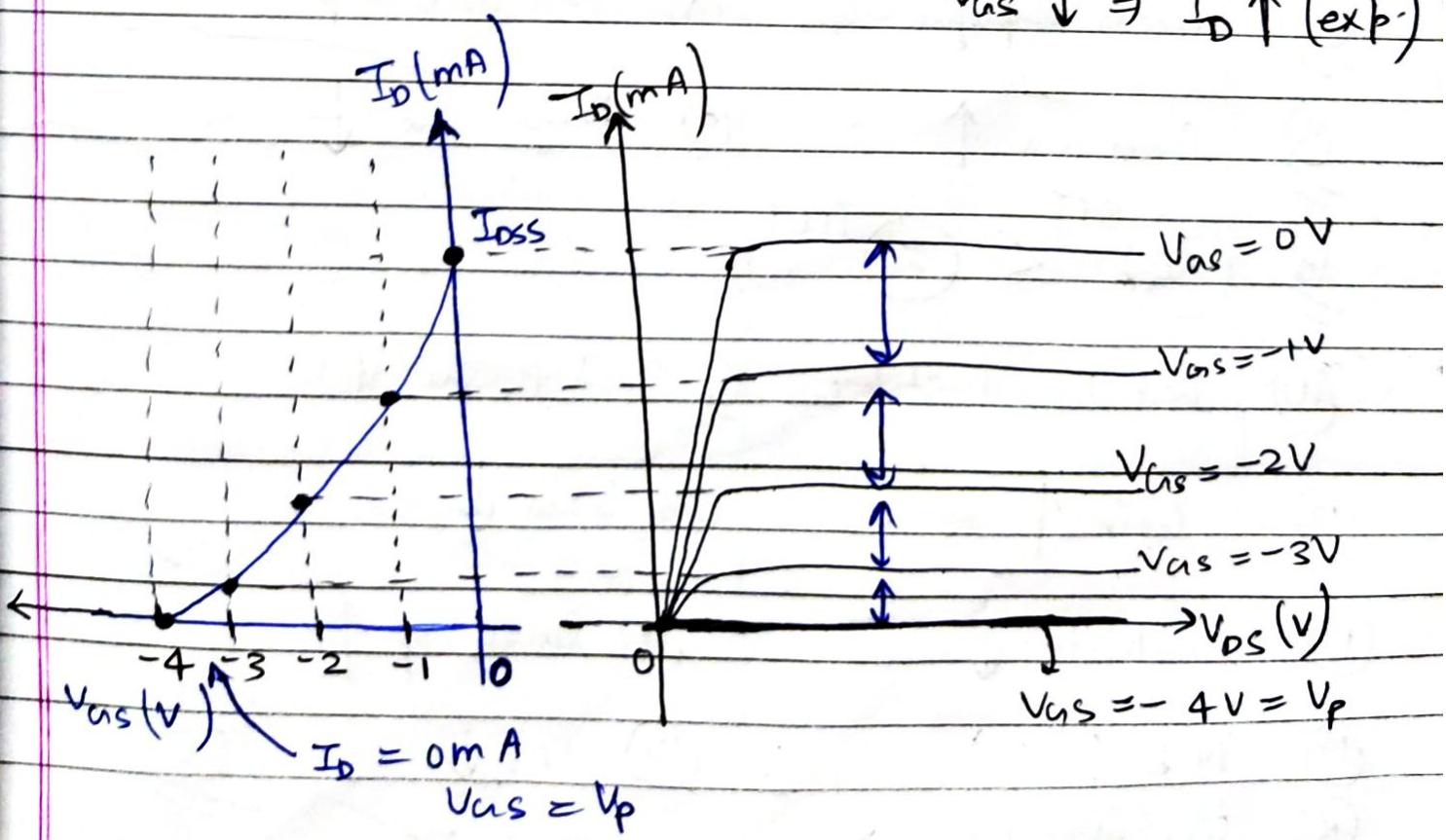
$$V_{us} \downarrow \Rightarrow I_D \uparrow (\text{exp.})$$



-o BJT Vs JFET o-

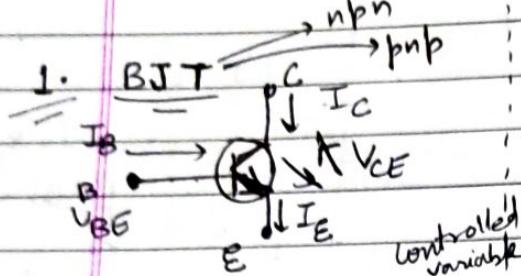

2. $I_C = f(I_B) = \beta I_B$

3. C-C-D

4. Bipolar

5. $I_C \approx I_E$

6. $V_{BE} = 0.7V$ (Si Trans)

7. Good fanout

8. Linear amplifier

9. Power cons. ↑

$$\frac{10}{\textcircled{10}} \quad Z_i^{\text{BJT}} < Z_i^{\text{JFET}}$$


11. Bad thermal stab.

12. Gain ↑

13. Sensitivity ↓

14. N.L ↑

15. Size of BJT >

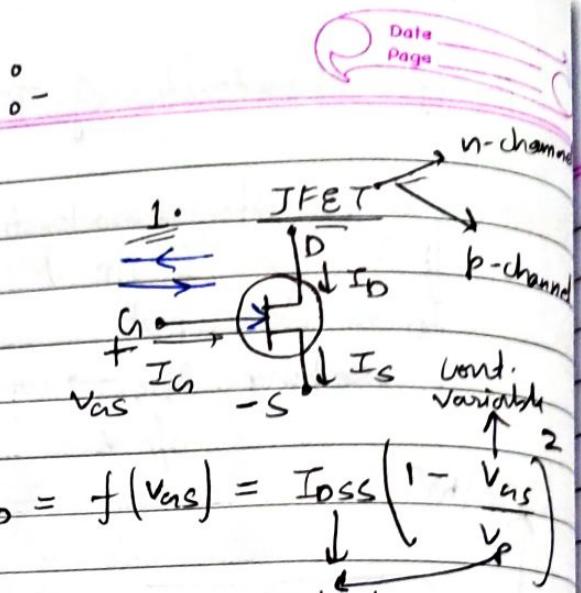

4. Unipolar $\rightarrow e^\Theta$ or holes $\rightarrow p\text{-channel}$
n-channel

5. $I_D = I_S$

6. $I_A = 0A$

7. Bad fanout

8. Non-linear amp.

9. Power cons. ↓

10. Good thermal stab.

11. Gain ↓

12. Sensitivity ↑


13. N.L ↓

14. Size of JFET \rightarrow J.C

Date _____
Page _____

(Base-Bias)

Fixed Bias Configuration:

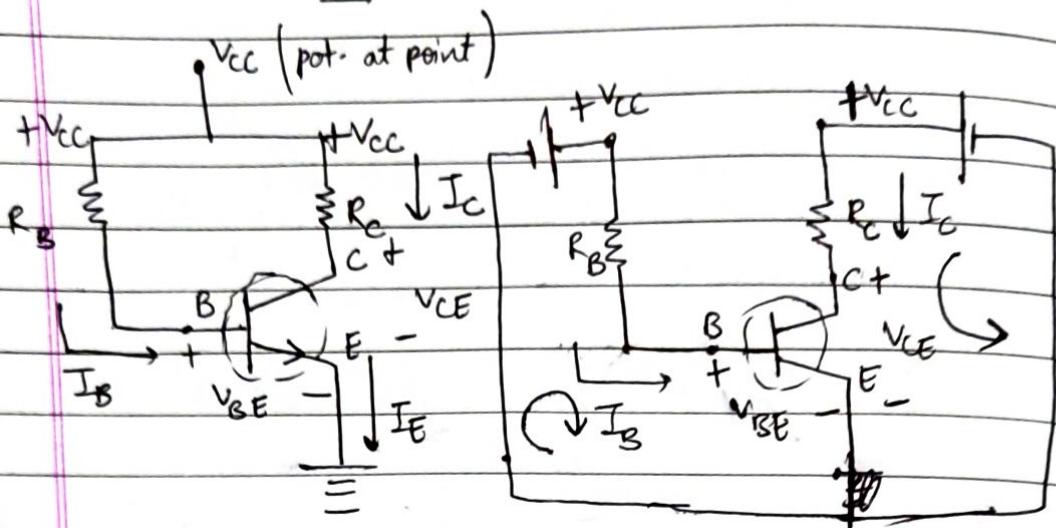

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

$$+V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$


Q. for fixed biased config., determine

a) I_C

b) R_C

c) R_B

d) V_{CE}

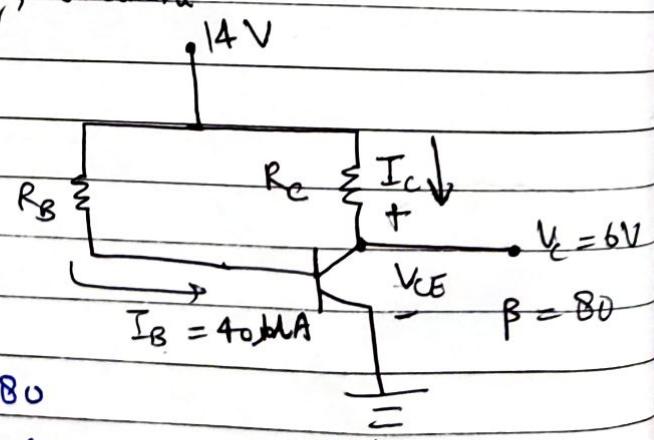

Soln $V_{CC} = 14V \quad \beta = 80$

$I_B = 40\mu A \quad V_C = 6V$

a) $I_C = \beta I_B = 80 \times 40 \Rightarrow 3.2mA$

b) $14V - I_C R_C = 6V$

$R_C = \frac{8}{I_C} = \frac{8}{3.2mA} \Rightarrow R_C$

c) $14V - I_B R_B - V_{BE} = 0$

$$\frac{14V - 0.7}{40} \Rightarrow \frac{3.3V}{40} \Rightarrow 332.5 \text{ k}\Omega \Rightarrow R_B$$

d) $V_{CE} = V_C - V_E$
 $= 6V - 0V$

$$V_{CE} \Rightarrow 6V$$

e) for the fixed-bias config., determine

f) I_C (b) V_C (c) β (d) R_B

Sols: $R_C = 2.7 \text{ k}\Omega$

$$I_B = 20 \text{ mA}$$

$$V_{CE} = 7.2V$$

$$I_E = 4 \text{ mA}$$

(e) $I_E = I_B + I_C$

$$I_C = \beta I_B \quad 4 = 20 + I_C$$

$$I_C \approx I_E$$

$$I_C = 4 \text{ mA} - 20 \text{ mA}$$

$$I_C = 4 \text{ mA} - 0.02 \text{ mA} \Rightarrow 3.98 \text{ mA}$$

(f) $V_{CC} - I_C \times 2.7 - 7.2V = 0$

$$V_{CC} = 7.2V + 3.98 \times 2.7 \Rightarrow 17.946 \text{ V}$$

(g) $\beta = \frac{I_C}{I_B} = \frac{3.98 \text{ mA}}{20 \text{ mA}} \Rightarrow 199$

(h) $V_{CE} - I_B R_B - V_{BE} = 0$


$$\frac{17.946 - 0.7V}{20 \text{ mA}} \Rightarrow 862.3 \text{ k}\Omega \text{ Ans}$$

in fixed biased

[Introduce R_E to improve stability of operating point]

Emitter-Bias Configuration :- Q point = (I_{CQ}, V_{CEQ})

Diode
Stage

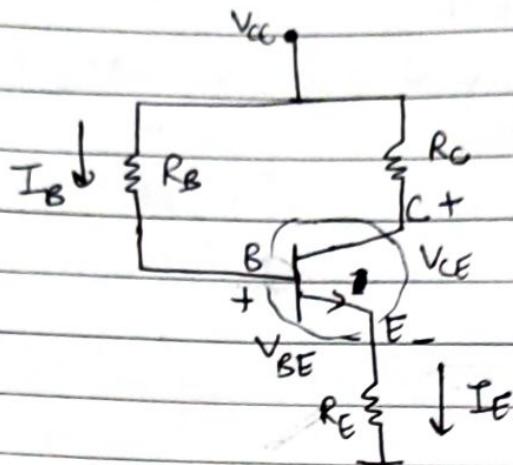

$$V_{CE} - I_B R_B - V_{BE} - I_E R_E = 0 \quad \dots$$

$$I_E = I_c + I_B$$

$$I_E = (\beta + 1) I_B$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} \Rightarrow I_B$$

~~$$I_C = \beta I_B \Rightarrow \beta \left[\frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} \right]$$~~

$$V_{CC} - I_E R_C - V_{CE} - I_E R_E = 0 \quad I_E \approx I_C$$

~~$$V_{CC} - I_C (R_C + R_E) - V_{CE} = 0$$~~

~~$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$~~

Advantages of using R_E :-

$$I_C = \beta \left(V_{CC} - V_{BE} \right)$$

$$\begin{cases} \beta + 1 \approx \beta \\ \beta R_E \gg R_B \end{cases}$$

indpt. of β


$$\text{ii) } T \uparrow = I_C \uparrow \quad \left\{ I_C = \beta I_B + (\beta + 1) I_{ES0} \right\} \quad \text{iii) } I_C = R I_B$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B + (\beta + 1) R_E}$$

$$\Rightarrow \underbrace{I_E R_E}_{\text{Drop}} \uparrow \Rightarrow I_B \downarrow \Rightarrow I_C \downarrow$$

Collector feedback biasing :-

Date _____
Page _____

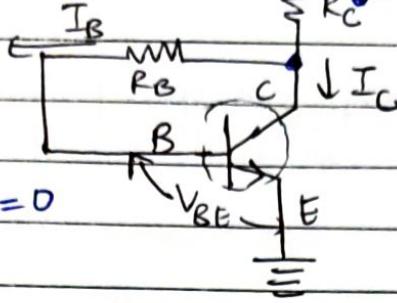

$$I = I_c + I_B$$

$$V_{CC} - I_R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} - [I + I_B] R_C - I_B R_B - V_{BE} = 0$$

$$I_c = \beta I_B$$

$$V_{CC} - (\beta + 1) R_C + R_B I_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + R_B}$$

$$I_c = \beta I_B = \frac{\beta (V_{CC} - V_{BE})}{(\beta + 1) R_C + R_B}$$

$$V_{CC} - I R_C - V_{CE} = 0$$

$$V_C - (I_c + I_B) R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - (I_c + I_B) R_C$$

Advantages :- ① Stabilizes the Q-point \Rightarrow i) against variation of T

ii) " " " " V_{CC}
iii) " " " " β

$$I_c = \frac{\beta (V_{CC} - V_{BE})}{(\beta + 1) R_C + R_B} \Rightarrow \frac{\beta (V_{CC} - V_{BE})}{\beta R_C + R_B} \Rightarrow \frac{\beta (V_{CC} - V_{BE})}{\beta R_C}$$

$\beta (R_C > R_B)$

Disadvantages :- i) for $\beta R_C > R_B$

$R_C \uparrow \uparrow$ $V_{CE} \uparrow \uparrow$ cost \uparrow
 $R_B \downarrow \downarrow$ $R \cdot B$ of C-B \downarrow

Bias Stabilization & Stability factors :-

$$Q - pt \equiv \left(\frac{V_{CEQ}}{x}, \frac{I_{CQ}}{y} \right)$$

Stabilization :- The process of making operating point independent of temperature changes & variations in transistor parameters is known as stabilization.

\rightarrow Source of unstabilization :- \Rightarrow B-point will shift $\rightarrow I_c \uparrow \downarrow$

i) changes in β

$$I_E = \beta I_B + (\beta + 1) I_{CBO}$$

iii) Change in T^o -

$$T \uparrow \neq I_{CBO} \uparrow \Rightarrow I_e \uparrow$$

$(10^\circ \uparrow T) \rightarrow \text{double } I_{CBO}$

V_{BE} (decreased by $2-5 \text{ mV}/{}^\circ\text{C} \uparrow T$)

$$I_B \rightarrow V_{BE}$$

(Ic)

Stability factor: The rate of change of collector current with respect to the leakage current at constant input voltage & amplification factor is called stability factor.

$$S = \frac{dI_C}{dI_{CBO}} \Big|_{\text{at const. } V_{BE} \text{ & } B}$$

$S \downarrow \rightarrow$ More stable
the system

$$\text{Ex: } T_1 \rightarrow S_1 = 8$$

$$T_2 \rightarrow S_2 = 5$$

Stability of $T_2 > T_1$

$$S' = \frac{dI_C}{dV_{BE}} \quad \text{at const } -I_{CBO} \text{ & } \beta$$

$$S'' = \frac{dI_C}{dV} \Big|_{\text{at const. } I_{C0} \text{ & } V_{RE}}$$


Stability factor for fixed-Bias Config.

Date _____
Page _____

Step ① KVL in I/p loop:

$$V_{CC} - I_E R_E - V_{BE} = 0$$

$$I_E = \frac{V_{CC} - V_{BE}}{R_E}$$

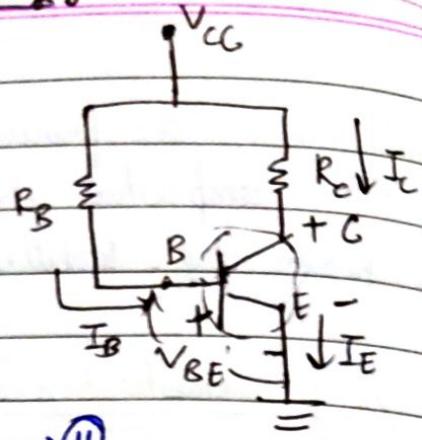

Step ② $I_C = \beta I_B + (\beta+1) I_{CBO} \rightarrow \text{①}$

$$I_C = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right) + (\beta+1) I_{CBO} \rightarrow \text{②}$$

Step ③ Diff. eq. ② wrt to I_C (at const. V_{BE} & β)

$$S = \frac{d I_C}{d I_{CBO}} \Big|_{\text{at const. } V_{BE} \& \beta}$$

$V_{BE} \& \beta \rightarrow \text{const.}$

$V_{CC} \& R_B \rightarrow \text{const.}$

$$\frac{d I_C}{d I_C} = \frac{\beta}{R_B} \frac{d}{d I_C} (V_{CC} - V_{BE}) + (\beta+1) \frac{d}{d I_C} I_{CBO}$$

$$1 = \frac{\beta}{R_B} (0 - 0) + (\beta+1) \frac{1}{S}$$

$$\boxed{S = \beta+1}$$

General exp. of SF :-

Diff. ① wrt to I_C (at const. V_{BE} & β)

$$1 = \beta \frac{d I_B}{d I_C} + (\beta+1) \frac{d I_{CBO}}{d I_C}$$

$$1 = \beta \frac{d I_B}{d I_C} + (\beta+1) \times \frac{1}{S}$$

General exp.
of SF

for any
biasing

$$\boxed{S = \frac{\beta+1}{1 - \beta d I_B / d I_C}}$$

$$S = \frac{\beta+1}{1 - 0} \Rightarrow \beta+1$$

diff eq (11) wrt to I_c keeping I_{CBO} & β as const.

$$1 = \frac{\beta}{R_B} \left(\frac{dV_{ac}}{dI_c}^0 - \frac{dV_{BE}}{dI_c} \right) + (\beta+1) \frac{dI_{CBO}}{dI_c}^0$$

$$1 = \frac{\beta}{R_B} \left(0 - \frac{1}{s'} \right) \Rightarrow s' \Rightarrow -\frac{\beta}{R_B}$$

Stability factor for Emitter-Bias Config.:-

Step ① KVL in i/p loop


$$V_{cc} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = I_B + I_C$$

$$V_{cc} - I_B R_B - V_{BE} - I_C R_E - I_B R_E = 0$$

$$V_{ac} = I_B (R_B + R_E) - V_{BE} - I_C R_E = 0$$
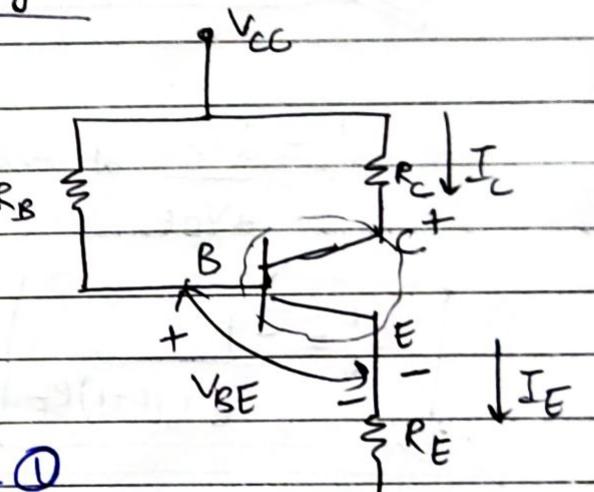
$$\boxed{I_B = \frac{V_{cc} - V_{BE} - I_C R_E}{R_B + R_E}} \rightarrow ①$$



$$\frac{dI_B}{dI_c} = \frac{1}{R_B + R_E} \quad \boxed{\frac{dI_B}{dI_c} = \frac{V_{cc} - V_{BE} - I_C R_E}{R_B + R_E}}$$

$$\frac{dI_E}{dI_c} = -\frac{R_E}{R_B + R_E}$$

Step ② $I_c = \beta I_B + (\beta+1) I_{CBO}$

$$I_c = \frac{\beta (V_{cc} - V_{BE} - I_C R_E)}{R_B + R_E} + (\beta+1) I_{CBO} \rightarrow ⑪$$

Step ③ Diff. eq ⑪ wrt to I_c (at const. V_{BE} & β)

$$\frac{dI_c}{dI_c} = \frac{\beta}{R_B + R_E} \frac{d}{dI_c} (V_{cc} - V_{BE} - I_C R_E) + (\beta+1) \frac{dI_{CBO}}{dI_c}$$

$$1 = \frac{\beta}{R_B + R_E} [0 - 0 - R_E \cdot 1] + (\beta+1) \frac{1}{s}$$

$$I = \frac{-\beta R_E}{R_B + R_E} + \frac{(\beta+1)}{S}$$

Date _____
Page _____

$$1 + \frac{\beta R_E}{R_B + R_E} = \frac{\beta+1}{S}$$

$$S = \frac{(\beta+1)}{1 + \frac{\beta R_E}{R_B + R_E}}$$

General form
↑ for any biasing

$$S = \frac{\beta+1}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

or

$$\cancel{E.B.C.} \quad S = \frac{(\beta+1)(R_B + R_E)}{R_B + (\beta+1)R_E}$$

$$S = \frac{\beta+1}{1 - \beta \left(\frac{-R_E}{R_B + R_E} \right)}$$

$$\rightarrow S' = \frac{dI_C}{dV_{BE}} \text{ at const } \beta \text{ & } I_{CB0}$$

$$S' = \frac{-\beta}{R_B + (\beta+1)R_E}$$

$$S = \frac{(\beta+1)(R_B + R_E)}{R_B + (\beta+1)R_E}$$

★ Stability factor for collector feedback biasing

$$I = I_C + I_B$$

$$\textcircled{1} \rightarrow V_{CC} - (I_C + I_B) R_C - I_B R_B - V_{BE} = 0 \rightarrow \textcircled{1} \quad \begin{array}{c} I_B \\ \parallel \\ R_C \\ \downarrow I \end{array}$$

$$V_{CC} - I_B (R_B + R_C) - V_{BE} - I_C R_C = 0 \quad \begin{array}{c} R_B \\ \parallel \\ C \\ \downarrow I_C \\ + B \\ V_{BE} = - \end{array}$$

$$I_B = \frac{V_{CC} - V_{BE} - I_C R_C}{R_B + R_C}$$

$$\textcircled{2} \quad I_C = \beta I_B + (\beta+1) I_{CB0} \frac{R_C}{R_E}$$

$$I_C = \beta \left(\frac{V_{CC} - V_{BE} - I_C R_C}{R_B + R_C} \right) + (\beta+1) I_{CB0} \rightarrow \textcircled{1}$$

(3) $\frac{dI_C}{dI_C}$ keeping β & V_{BE} → const.

$$S = \frac{(\beta+1)(R_B + R_C)}{R_B + (\beta+1)R_C} \rightarrow C.F.B$$

$$s' = \frac{dI_c}{dV_{BE}} \quad \left| \begin{array}{l} I_{CBO} \text{ & } \beta \text{ are const.} \end{array} \right.$$

$$\frac{dI_c}{dI_c} = \frac{\beta}{R_B + R_C} \frac{d}{dI_c} \left(V_{CC} - V_{BE} - I_c R_C \right) + (\textcircled{2}) 0$$

$$1 = \frac{\beta}{R_B + R_C} \left[0 - \frac{dV_{BE}}{dI_c} - R_C \right]$$

$$1 = \frac{\beta}{R_B + R_C} \left[\frac{-1 - R_C}{s'} \right]$$

~~C.F.B~~

$$s' = -\frac{\beta}{R_B + (\beta+1)R_C}$$

Compare

$$s' = -\frac{\beta}{R_B + (\beta+1)R_E}$$

~~E.B.C~~