

Boolean Algebra

It is a set of rules used to simplify the given logic expression without changing its functionality.

$$\text{eg. } f = \overbrace{\bar{A}B}^{\text{NOT}} \oplus \underbrace{\overbrace{BC}^{\text{OR}}}^{\text{AND}} \oplus \underbrace{\overbrace{ABC}^{\text{NOT}}}^{\text{AND}}$$

$$= \overbrace{\bar{A}B}^{\text{NOT}} \oplus \underbrace{\overbrace{BC}^{\text{OR}}}^{\text{AND}}$$

↗ Compliment Rule - $(\bar{A} \Leftrightarrow A')$ or $(\text{Not } A)$



↗ AND Operator :-



A	B	Y
0	0	0
1	0	0
0	1	0
1	1	1

$$\text{eg. } A \cdot A = 0 \quad , \quad A \cdot 0 = 0 \quad , \quad A \cdot 1 = A$$

$$\text{if } A = 0$$

$$A \cdot A = 0$$

$$\downarrow 0 = 0$$

$$1 = 1$$

$$\text{if } A = 1$$

$$A \cdot A = 1, 1 = 1$$

Priority $\rightarrow \text{NOT} > \text{AND} > \text{OR}$

$$\rightarrow A \cdot A' = 0$$


$$\text{if } A = 0.$$

$$0 \cdot 1 = 0.$$

$$\text{if } A = 1.$$

$$1 \cdot 0 = 0.$$

↗ OR Operators :-

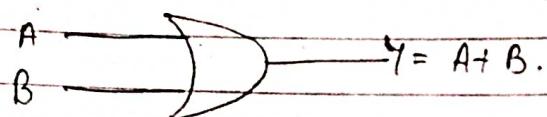

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$$(A')' = A$$

$$\boxed{A + A = A}, \boxed{A + 0 = A}, \boxed{A + 1 = 1}$$

$$\boxed{A + A' = 1}$$

$$\begin{aligned} Q. \quad F &= A + AB + ABC \\ &= A(1 + B + BC) \\ &= A. \end{aligned}$$

↗ Distributive Law :-

$$A \cdot (B + C) = AB + AC.$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$\begin{aligned} Q: \quad Y &= BAC + BA\bar{C} + B\bar{C} \\ &= \bar{A}\bar{C}(B + \bar{B}) + B\bar{C} \\ &= \bar{A}\bar{C} + B\bar{C} = \bar{C}(A + B) \end{aligned}$$

↗ Commutative Law :-

$$A+B = B+A$$

$$A \cdot B = B \cdot A$$

↗ Associative laws :-

$$A.(B.C) = (A.B).C$$

↗ De-morgan's law :- (break the line, change signs)

$$\overline{(A+B)} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

↗ Any function can be expressed in 2 ways:-

SOP form

POS form

L. SOP form (Sum of Product)

$$2^3 = 8$$

A	B	C		F
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		1

$$F(A, B, C) = \sum m(m_2 + m_4 + m_5 + m_6 + m_7),$$

$$\sum m(2, 4, 5, 6, 7).$$

~~or~~
by writing with
(-) sign & without (-)

$$= \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + ABC + \bar{ABC}$$

$$= A + \bar{A}\bar{B}\bar{C}$$

~~eg~~

$$A\bar{A} + A + \bar{A} = (\bar{A} + \bar{A})(A + \bar{B}\bar{C})$$

$$\therefore (A + \bar{B}\bar{C}).$$

Q) Simplify the expression.

$$Y(A, B) = \sum m(0, 2, 3)$$

$$Y = \bar{A}\bar{B} + A\bar{B} + AB$$

$$= \bar{B}(A + \bar{A}) + AB$$

$$= \bar{B} + AB$$

$$= (B + A)(B + \bar{B}) \quad (\text{By distrib. law})$$

$$= A + \bar{B}$$

Digital Electronics.

$$A + 0 = A$$

$$A \cdot 1 = A$$

$$A + \bar{A} = 1$$

$$A\bar{A} = 0$$

OR

AND

NOT

NAND

NOR


$\min \bar{w} \rightarrow 0 \in \bar{A}$
 $1 \rightarrow A$

$\max \bar{w} \rightarrow 0 \in \bar{B}$
 $1 \rightarrow \bar{B}$

	A	B	C	AB	BC	AB + BC
0, 0, 0	0	0	0	0	0	0
0, 1, 0	0	0	1	0	0	0
0, 0, 1	0	1	0	0	1	1
0, 1, 1	0	1	1	0	0	0
1, 0, 0	1	0	0	0	0	0
1, 0, 1	1	0	1	0	0	0
1, 1, 0	1	1	0	1	1	1
1, 1, 1	1	1	1	1	1	1

$$F = \sum_{i=1}^n w_i x_i \quad \& \quad \sum_{i=1}^n z_i$$

$$F = AB\bar{C} - ABC + A\bar{B}C.$$

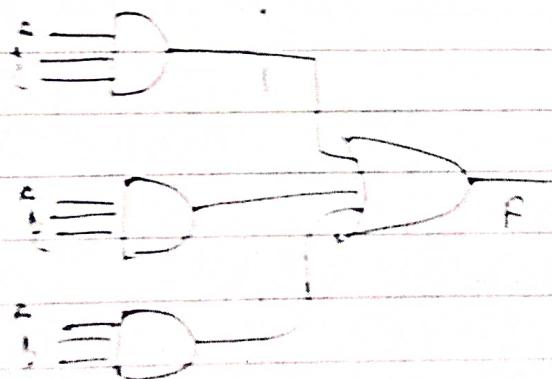

1st phase
 AND

2nd phase
 OR

OR

$$Q. \quad \overline{AB} + B\bar{C} = \overline{AB} \cdot \overline{B\bar{C}}$$

$$(\bar{A} + \bar{B}) \cdot (\bar{B} + \bar{C})$$

$$(\bar{A} + \bar{B}), (\bar{B} + C)$$

\bar{Y}	A	B	y	\bar{y}
0	0	0	0	1
0	1	0	1	1
1	0	1	1	0
1	1	0	0	1

$$Y = A\bar{B}$$

$$Y = \Sigma(2)$$

$$\bar{Y} = \Sigma(0, 1, 3)$$

$$= m_0 + m_1 + m_3$$

$$\bar{Y} = \bar{A}\bar{B} + \bar{A}B + AB.$$

$$\bar{Y} = \bar{A}(\bar{B} + B) + AB$$

$$= \bar{A} + AB$$

$$\bar{Y} = \bar{A} + B$$

$$Q. \quad Y = AB + A\bar{B}$$

Convert SOP \rightarrow POS

$$\underbrace{\underline{AB}}_x + \underbrace{\underline{A\bar{B}}}_y + \underbrace{\underline{\bar{B}}} \quad (\text{use distributive law})$$

$$(AB + A) \cdot (A\bar{B} + \bar{B})$$

$$(A + A)(B + A) \cdot (A + \bar{B})(\bar{B} + \bar{B})$$

$$A \cdot (B + A) \cdot (A + \bar{B})$$

$$Q. \quad Y = ABC + \bar{A}\bar{B}C + A\bar{B}\bar{C} \quad \text{Convert it to POS.}$$

$$Y = \underbrace{\underline{ABC} + \underline{\bar{A}\bar{B}C}}_x + \underbrace{\underline{A\bar{B}\bar{C}}}_y$$

$$(ABC + \bar{A}\bar{B}C) \cdot ABC + A\bar{B}\bar{C} +$$

$$(ABC + \bar{A}\bar{B}C + AB) \cdot (ABC + A\bar{B}C + \bar{C})$$

$$(ABC + \bar{A}\bar{B}C + A) \cdot (ABC + \bar{A}\bar{B}C + B) \cdot (ABC + A\bar{B}C + \bar{C})$$

1 K-map (Karnaugh map)

$$2^n$$

$n \rightarrow$ no. of variables

e.g. A, B

$$\text{Cells} = 2^2 = 4.$$

Minimise

$$f(A, B, C) = \sum_m (1, 3, 5, 7).$$

$$\text{Number of Cells} = 2^3 = 8.$$

		BC	00	01	11	10
		$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC	$B\bar{C}$
0 \leftarrow \bar{A}	0 \leftarrow \bar{A}	000	001	011	010	
	1 \leftarrow A	100	101	111	110	

		BC	00	01	11	10
		$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC	$B\bar{C}$
0	0	0	1	3	2	
	1	4	5	7	6	

		BC	00	01	11	10
		$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC	$B\bar{C}$
0	0	0	1	1		
	1	1	1			

$$\therefore f = C.$$

$\sum_m (1, 3, 5, 7)$

$$Q f(A, BC) = 0, 1, 2, 4, 7$$

No. $2^3 = 8$
9 cells

	00	01	11	10
0	(1)			
1	(1)	0		

$$f \leftarrow A\bar{B}C + A\bar{B}\bar{C}$$

$$F = ABC + \bar{B}C + \bar{A}\bar{B} + \bar{A}\bar{C}$$

$$Q f(A, B, C, D) = \Sigma m(0, 2, 3, 7, 11, 13, 14, 15)$$

No. 9 $2^4 = 16$

$\bar{C}\bar{D}$	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	AB	$\bar{C}D$	$\bar{C}D$	$\bar{C}D$	CD	CD
$\bar{C}D$	0	4	12	8	$\bar{A}\bar{B}$	0	1	3	2
CD	1	5	13	9	$\bar{A}B$	4	5	7	6
$C\bar{D}$	3	7	15	11	AB	12	13	15	14
$\bar{C}\bar{D}$	2	6	14	10	$A\bar{B}$	8	9	11	10

$$\Sigma m(0, 2, 3, 7, 11, 13, 14, 15)$$

	$\bar{A}\bar{B}$	$A\bar{B}$	AB	\bar{B}
$\bar{C}\bar{D}$	1	0	1	8
$\bar{C}D$	1	5	13	6
$C\bar{D}$	1	3	15	11
$\bar{C}\bar{D}$	1	2	6	10

$$f = ACD + ABC + ABD + \bar{A}\bar{B}\bar{D}$$

$$Q) f(A, B, C, D) = \sum m(2, 3, 4, 5) + \sum d(6, 7)$$

$\bar{A}B$

$\bar{A}\bar{B}$

$A\bar{B}$

AB

$\bar{C}\bar{D}$

$\bar{C}D$

CD

$C\bar{D}$

$$f = \bar{A}B + C\bar{A}$$

Q: Simplify the boolean function

$$f(A, B, C, D, E) = \sum m(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$

$$\text{No. of cells} = 2^5 = 32$$

first overlap & take corner.

$$f = B\bar{D}E + AEC + \bar{A}\bar{B}\bar{E}$$

1 Redundancy term.

$$F(A, B, C) = \Sigma m(13, 6, 7)$$

$2^3 = 8$ cells.

A	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
$\bar{A}+0$	0	1	0	1
$A+1$	0	1	1	0

$$f = \bar{A}C + \underbrace{ABC}_{+} + AB$$

Redundancy term.

$$f = \bar{A}C + AB$$

According to redundancy theorem.

- 1) Three variables φ must represent in ~~exponents~~ ans.
- 2) each variable is repeated twice.
- 3) One variable must be in complement form.
- 4) Result is complimented variable.

$$\text{eg. } g \cdot A\bar{B} + BC + AC.$$

$$\text{Ans} \rightarrow A\bar{B} + BC$$

$$\text{eg. } (A+B) \cdot (\bar{A}+C) \cdot (B+C)$$

$$\text{Ans} \rightarrow (A+B) \cdot (\bar{A}+C)$$

$$\Rightarrow \bar{A}C + AB + BC (A+\bar{A})$$

$$\Rightarrow \bar{A}C + AB + ABC + \bar{A}BC$$

$$\Rightarrow \bar{A}C (1+B) + AB (1+C)$$

$$\Rightarrow \bar{A}C + AB$$

Minimise

$$f = AB + A\bar{B}C + A\bar{B}\bar{C}$$

$$f = A$$

$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
$\bar{A} \Rightarrow 0$			
$A \Rightarrow 1$	1	1	1

LOGIC GATE


Basic Gates \rightarrow AND, OR, NOT

Universal Gates \rightarrow NAND, NOR

Arithmetic Gates \rightarrow XOR, X-NOR.

Q. Design NOR Gate with the help of NAND Gate.

$$Y = \overline{A+B}$$

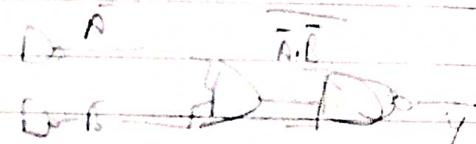

$$= \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} + \overline{B}}$$


$$= \overline{A+B}$$

Design NAND gate with the help of NOR gate

$$Y = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} + \overline{B}}$$

$$= \overline{\overline{A} \cdot \overline{B}}$$

NOR		Y
A	B	
0	0	1
0	1	0
1	0	0
1	1	0

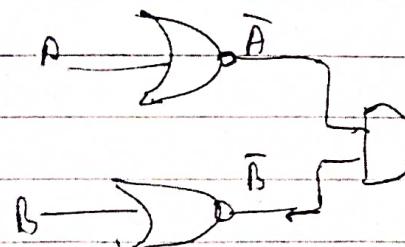



Q) Design a XOR gate using NAND gate.

Input \rightarrow NAND gate $\rightarrow \overline{A \cdot B} = Y$.

Output \rightarrow X-OR gate $\rightarrow Y = \overline{AB} + A\overline{B}$

$$Y = \overline{\overline{AB} + A\overline{B}}$$
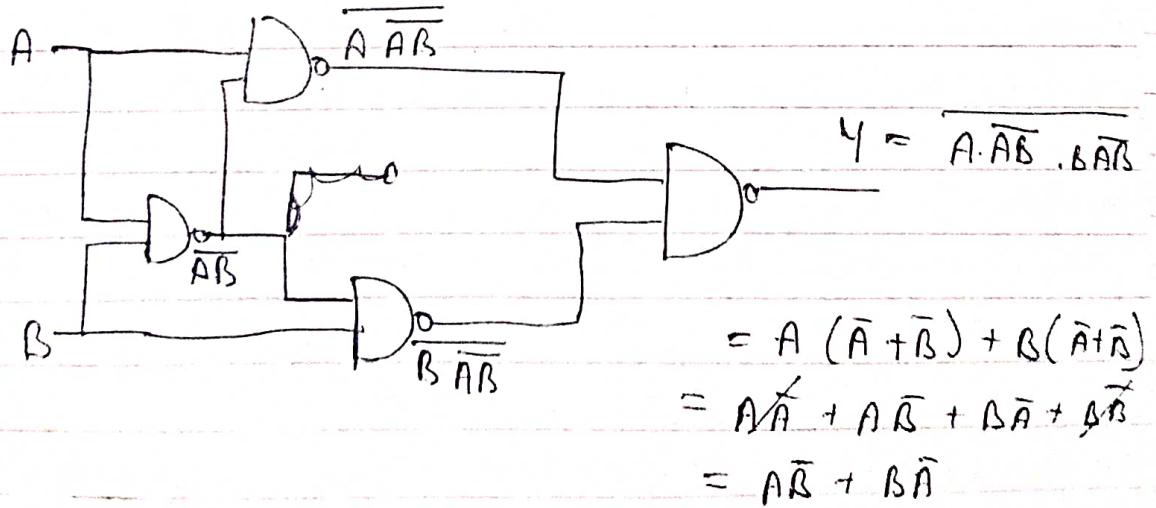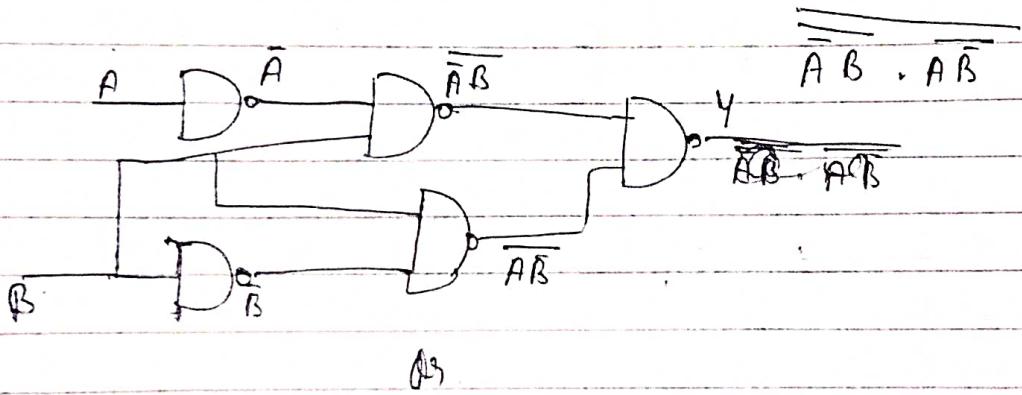
$$Y = \overline{\overline{AB}, A\overline{B}} = \overline{AB} + A\overline{B}$$




↗ Basic Combinational Circuits

- Adder
- Subtractor.


Half Adder :- (2-bit)

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

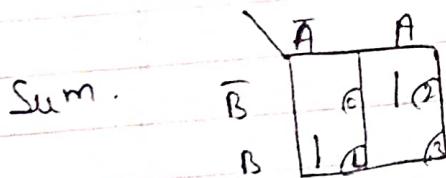


$$\begin{aligned} S &= \bar{A}\bar{B} + A\bar{B} \\ &= A \oplus B \end{aligned}$$

Carry:

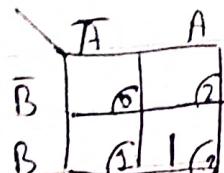


$$C = A \cdot B$$

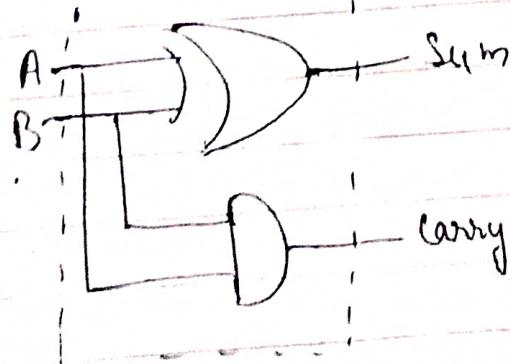

Full Adder :- (3 bit)

A	B	Cin	Sum	Carry
0	0	0	0	0.
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1.
1	0	0	1	0
1	0	1.	0	1
1	1	0	0	1.
1	1	1	1	1

$$\text{No. of cells} = 2^3 = 8.$$

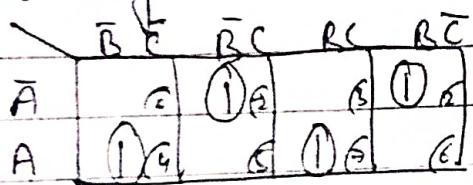

$$\text{Sum} = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$


$$\begin{aligned}
 &= \bar{A} [\bar{B}\bar{C} + B\bar{C}] + A [\bar{B}\bar{C} + B\bar{C}] \\
 &= \bar{A} (\underbrace{B \oplus C}_X) + A (B \oplus C)
 \end{aligned}$$

$$= \bar{A} X + A \bar{X}$$

$$= A \oplus X$$



$$\text{Sum.} = A \oplus B \oplus C$$

Carry:

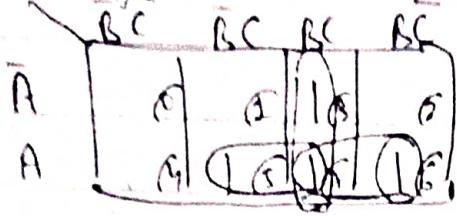


$$\text{Carry} = AC + ABC + \overline{AB} \cdot AB$$
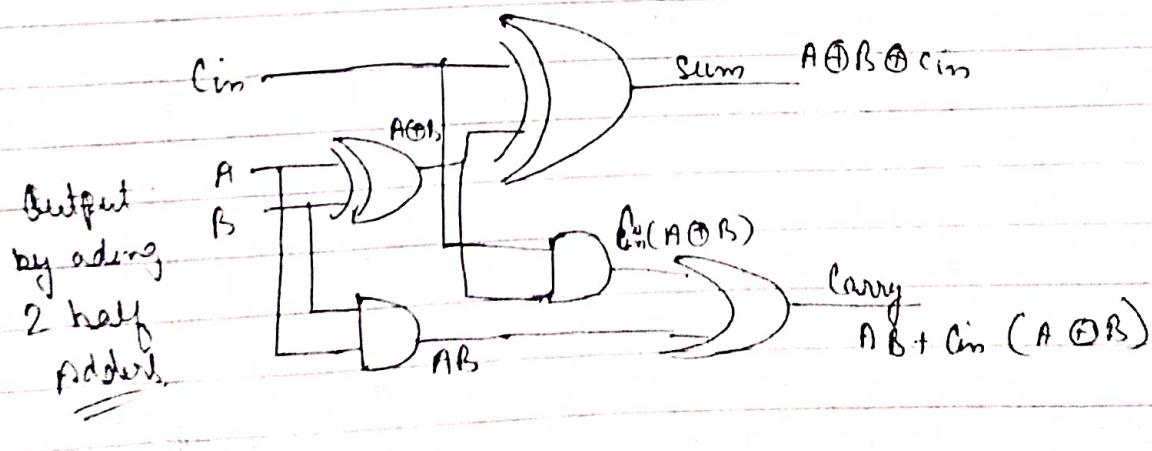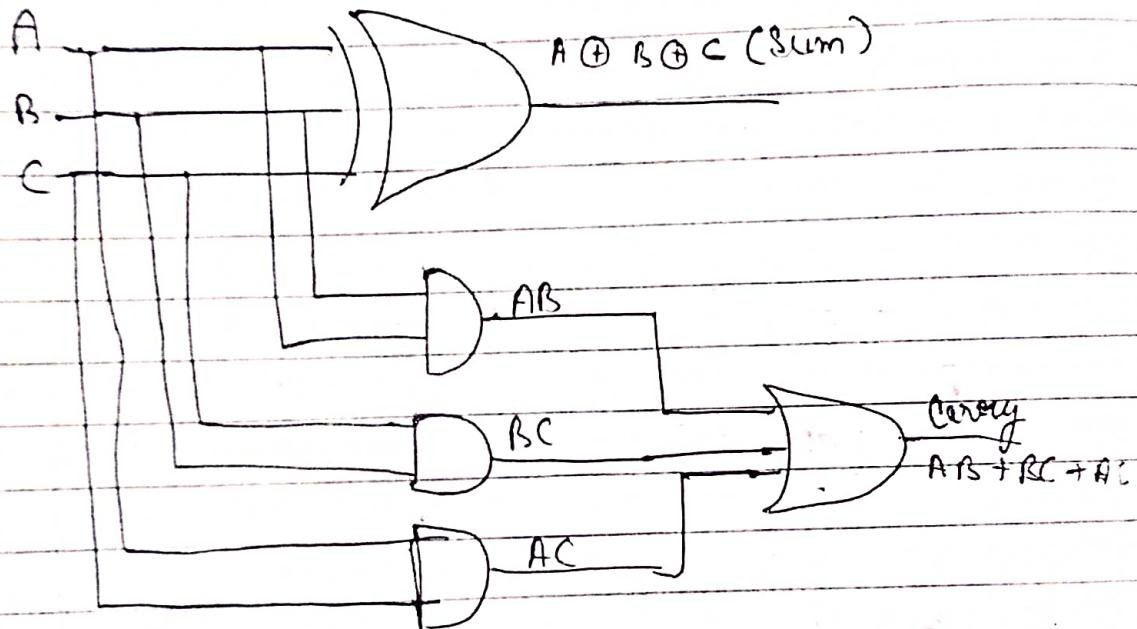
$$\begin{aligned}\text{Carry} &= AB + BC + AC \\ &= AB + \text{Cin}(A \oplus B)\end{aligned}$$




1) Half Subtractor :-

$(A-B)$	A	B	Difference	Borrow
0	0	0	0	0
0	1	0	1	1
1	0	1	1	0
1	1	1	0	0

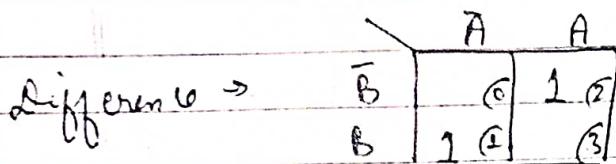
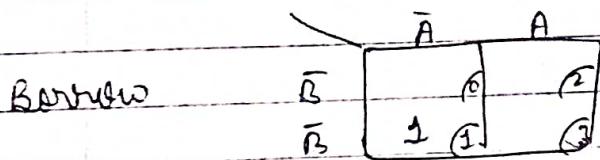
$$D = A\bar{B} + \bar{A}B \\ = A \oplus B$$



2) Full Subtractor :- $(A-B)-C$


A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = A \oplus B \oplus C$$


	$\bar{B}C$	$B\bar{C}$	BC	$\bar{B}\bar{C}$
\bar{A}	0	1	0	1
A	1	0	1	0

	$\bar{B}C$	$\bar{B}\bar{C}$	BC	$\bar{B}\bar{C}$
\bar{A}	0	1	1	0
A	1	0	1	0

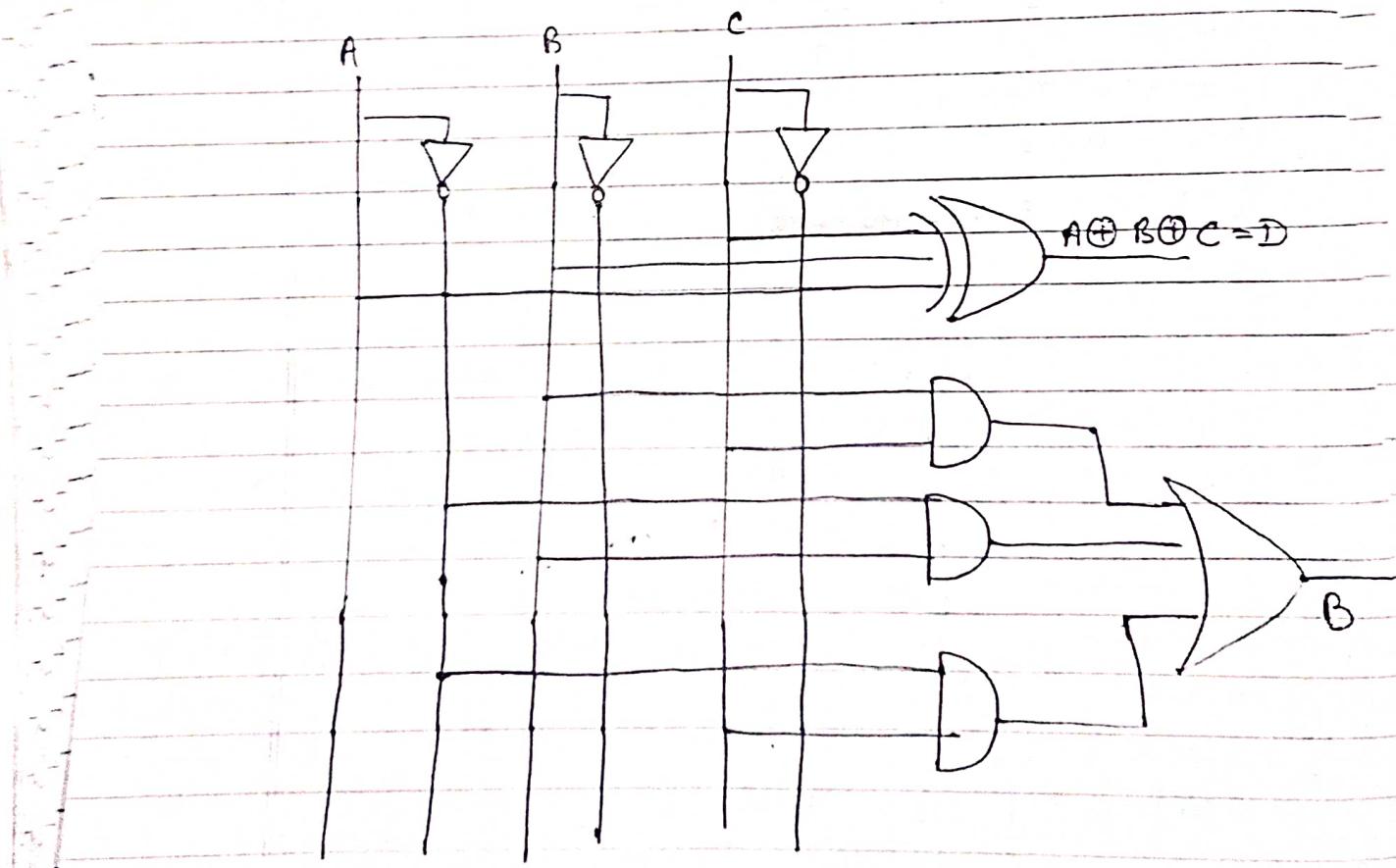
$$\text{Borrow} = \bar{A}C + B\bar{A} + BC$$



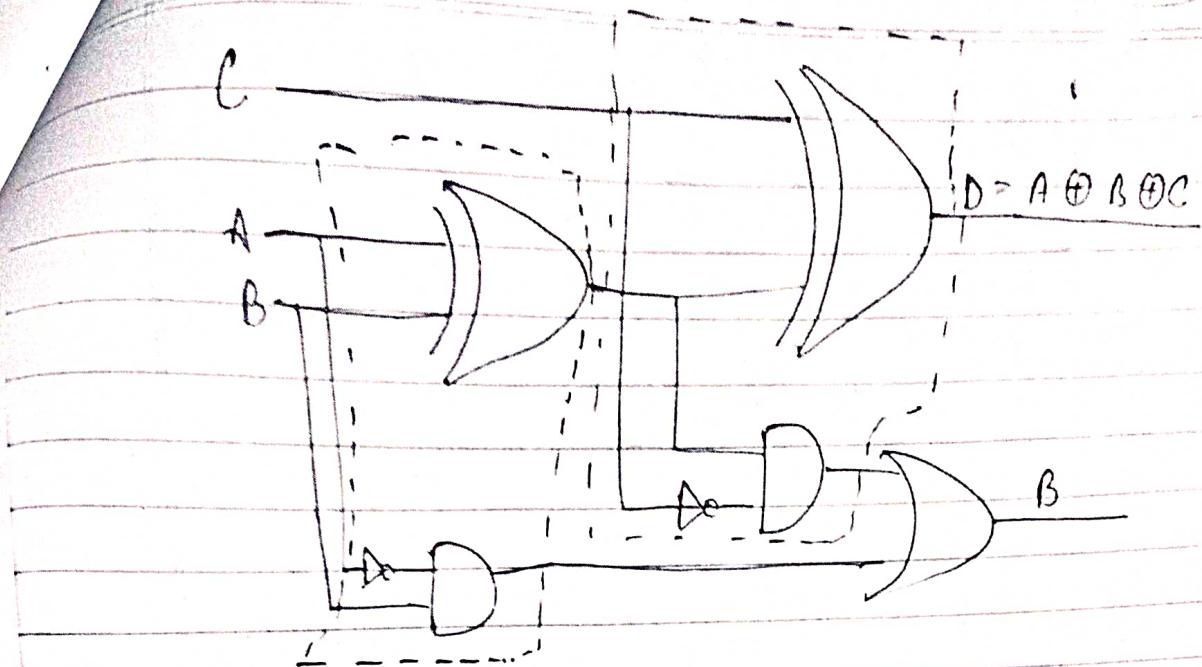
$$\begin{aligned}
 \text{Borrow} &= BC + A\bar{C} + B\bar{A} \\
 &= \bar{A}B + \bar{A}\bar{B}C + AB\bar{C} \\
 &= AB + [A \oplus B]C
 \end{aligned}$$




↗ Sequential Circuits \Rightarrow

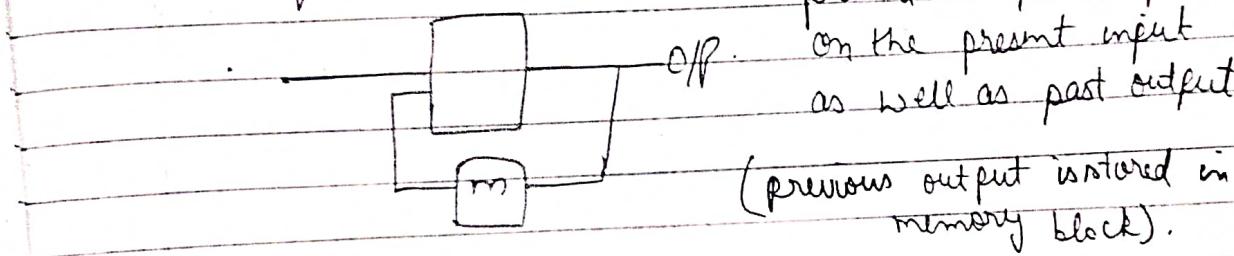

↗ Combinational Circuit

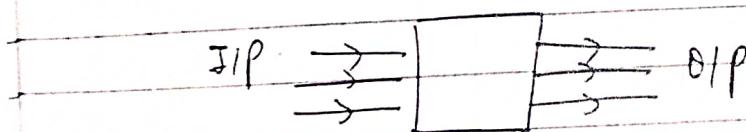


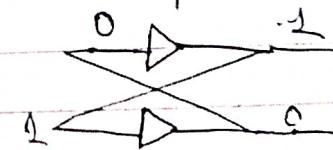present output depends only on present input




↗ Latch and flip-flop.

(set)

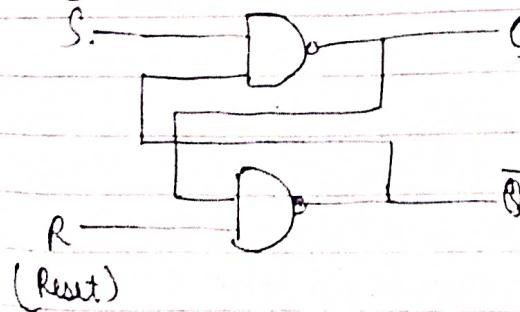

A	B	Y	NAND
0	0	1	
0	1	0	
1	0	0	
1	1	1	

S	R	Q	\bar{Q}
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	undefined	

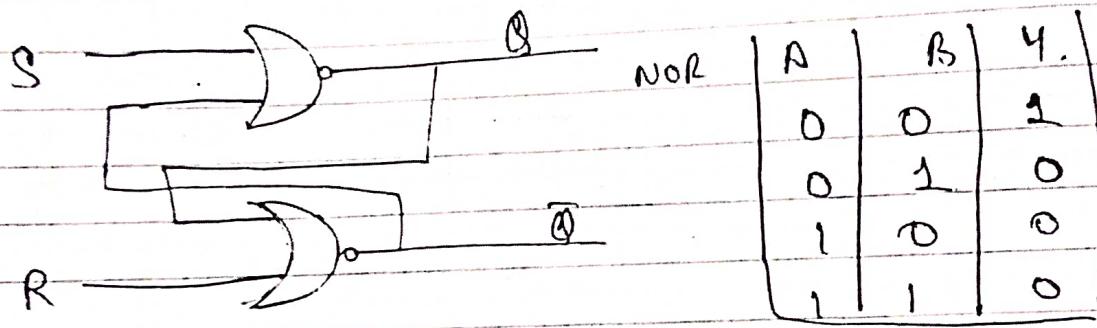

S R Q \bar{Q}

1	0	0	1
0	0	0	1
0	1	1	0
0	0	1	0

1 1 undefined