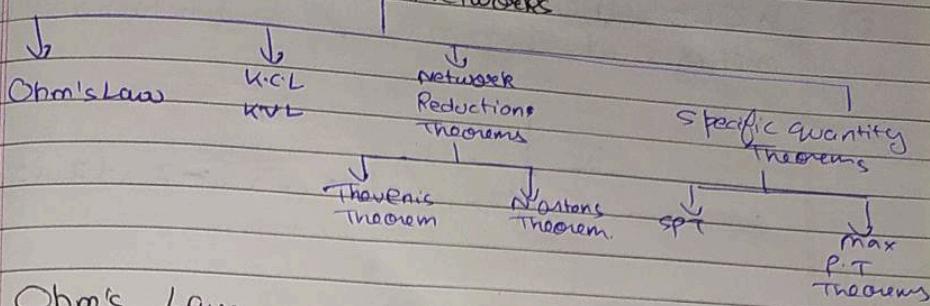


## DC Networks



→ Ohm's Law

The potential difference across any two points of the conductor, will be directly proportional to the current flowing through it.

$$V \propto I$$

$$V = IR$$


$$R \rightarrow (1) \text{ ohms}$$

→ Kirchhoff's Laws:-

- 1) KVL - In any closed circuit or mesh, the algebraic sum of all the emfs and voltage drops will be zero.


$$\sum \text{Emf's} + \sum \text{IR} = 0$$

2) KCL

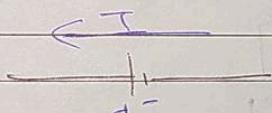

Rise in potential  
(+)ive

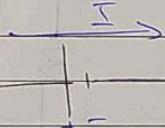(Current from lower potential to higher " " )




Drop in potential  
(-)ive  
(Potential/voltage drop)


(Current from higher to lower potential)



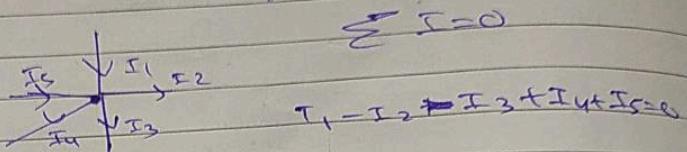2) KCL - The algebraic sum of all the currents meeting at a point are a function will be zero.




\* Mesh analysis Method

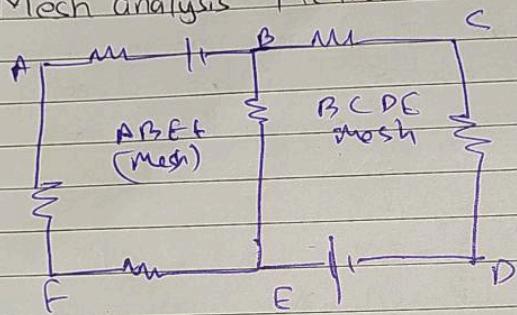

Loop can have inner loops  
but Mesh can't have inner loops.

→ Numerical Types

i) Type - 1

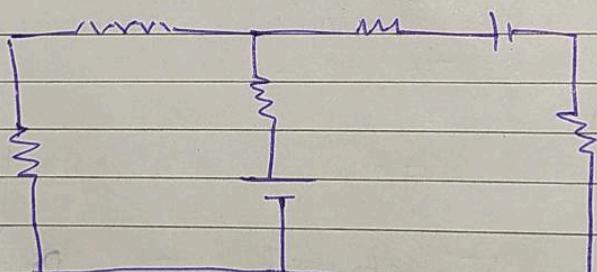


Having voltage source and current source




REDMI NOTE 8  
AI QUAD CAMERA

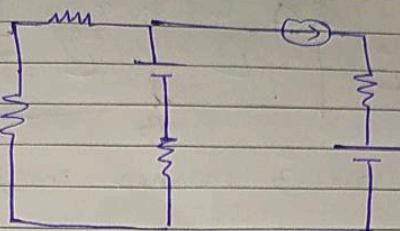
2) Type-2 Having Resistance and voltage source along with current source but in outer loop.



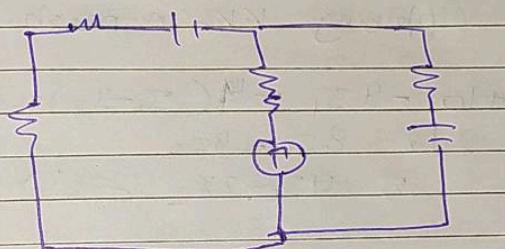3) Type-3 Having Resistance and voltage Source along with current source in inner loop.



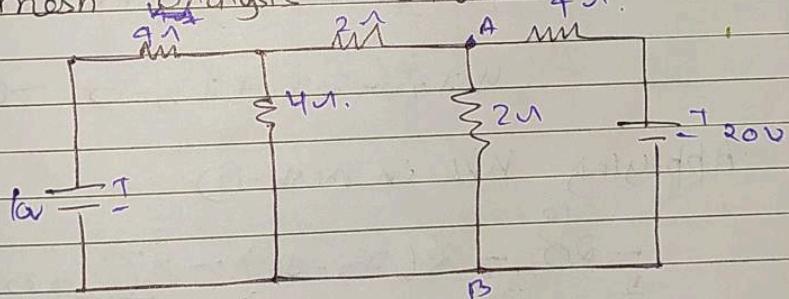
Q1) Calculate the current in Branch A-B of  $2\Omega$  resistance for the given circuit using mesh analysis method.



<sup>across</sup>  
Voltage, Resistance in KVL should always be taken  $\leftarrow$  type.

Turn Page

Sol-

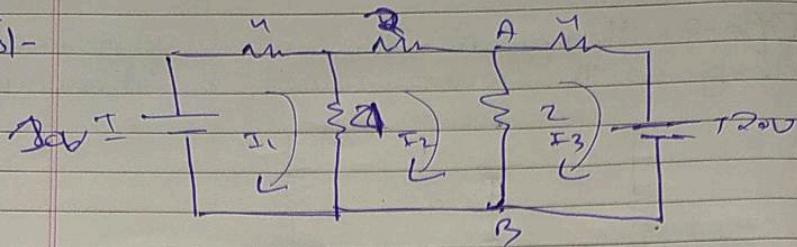

There are 3 meshes in given circuit.

Let all the current be in  $\leftarrow$  direction.

$$+20 - 4I_1 - 4I$$

Applying KVL in mesh (1)

$$+10 - 4I_1 - 4(I_1 - I_2) = 0$$

$$10 = 8I_1 + 4I_2$$

$$5 = 4I_1 + 2I_2 \quad \text{--- (i)}$$

Applying KVL in mesh (2)

$$-2I_2 - 2(I_2 - I_3) - 2(I_2 - I_1) = 0$$

$$-I_2 - I_2 - I_3 - 2I_2 + 2I_1 = 0$$

$$4I_2 - 2I_1 + I_3 = 0 \quad \text{--- (ii)}$$

Applying KVL in mesh (3)

$$-20 - 2(I_3 - I_2) - 2I_3 = 0$$

$$10 = -3I_3 + I_2 \quad \text{--- (iii)}$$

$$4I_2 - 2I_1 + I_2 - 10 = 0$$

$$\begin{aligned} 5I_2 - 2I_1 - 10 \times 2 &\Rightarrow 10I_2 - 4I_1 = 20 \\ -2I_2 + 4I_1 = 5 & \\ \hline 8I_2 &= 25 \\ I_2 &= \frac{25}{8} \end{aligned}$$



Solving eqn 1, 2, 3.

$$I_1 = 1.093 \text{ A} \quad I_2 = -0.312 \text{ A}$$

$$I_3 = -3.432 \text{ A}$$

$$\begin{aligned} I_{AB} &= I_2 - I_3 = 0.312 - (-3.432) \\ &= 3.744 \text{ A} \end{aligned}$$

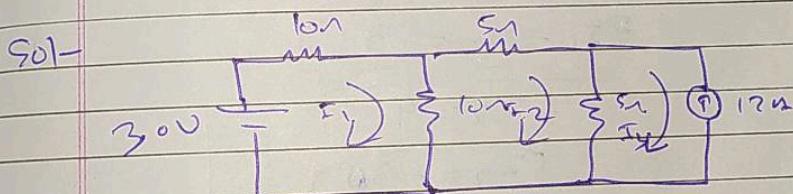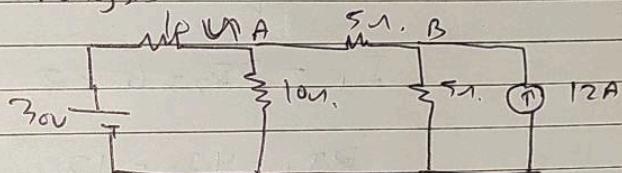(Q2) Find the current in AB Branch using mesh analysis.



3 meshes.

Let all the current in C-W dirn.  
Applying KVL in mesh ①

$$\begin{aligned} +30 - 10I_1 - 10(I_1 - I_2) &= 0 \\ 30 &= 2I_1 - I_2 \quad (i) \end{aligned}$$

Applying KVL in mesh ②

$$+8I_2 + 8(I_2 - I_3) + 10(I_2 - I_1) = 0$$

$$4I_2 - 2I_1 - I_3 = 0$$

$I_3 = -12A$  because we have assumed it in C.W dir<sup>n</sup> but actually it is flowing A.C.W Dir<sup>n</sup> (P12m)

$$4I_2 - 2I_1 - (-12) = 0$$

$$2I_2 - 2I_1 + 12 = 0$$

~~2I~~

$$I_1 - 2I_2 = 6 \quad -(ii)$$

From eq 1 and 2

$$I_1 - 2I_2 = 6 \times 2$$

$$2I_1 - 4I_2 = 12$$

$$\begin{array}{r} 2I_1 - I_2 = 3 \\ \hline -3I_2 = 9 \end{array}$$


$$I_2 = -3A$$

$$I_1 = 0$$


In AB branch

$$= I_2 = -3A$$

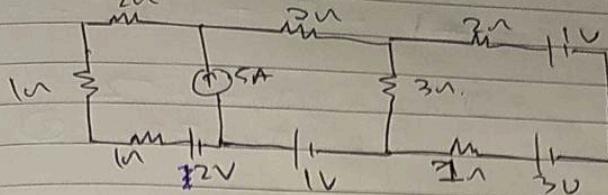(Q-3) Find the voltage across  $\frac{2}{3}A$  resistor using KVL.



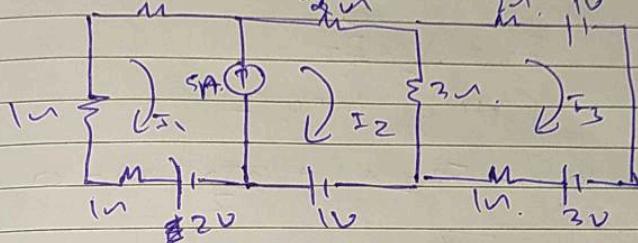
Sol- Method of Super Mesh (Used when the current source is now two meshes).



$$I_2 - I_1 = 5 \text{ (By super mesh)}$$

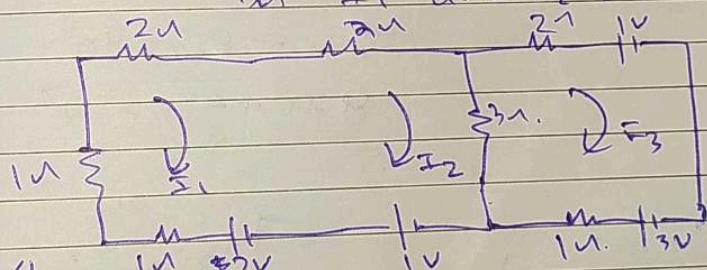-(i) as  $I_2$  and  $5A$  dir. is down

(After this remove ( $5A$ ) current source from the circuit, but  $I_1$  and  $I_2$  will remain)



Applying KVL in mesh 1 and 2 by super mesh

$$I_1 + I_2 - I_3 = 1(\Sigma) - 2I_1 - 2I_2 - 3(I_2 - I_3) - 4I_1 - 5I_2 + 3I_3 + 1 = 0 \quad (ii)$$

Applying KVL in mesh 3

$$-2I_3 + 1 + 3 - 1(I_3) - 3(I_3 - I_2) = 0$$

$$\begin{aligned} -6I_3 + 3I_2 &= -2 \\ 2 &= 6I_3 - 3I_2 \quad (3) \end{aligned}$$

From eq 1 & 2 and 3

$$I_3 = \frac{2 + 3I_2}{6} \quad (3)$$

$$I_3 = \frac{1}{2} + \frac{I_2}{2}$$

Putting in eq 2

$$-4I_1 - 5I_2 + 1 + \frac{3I_2}{2} + 1 = 0$$

$$- \cancel{\frac{3I_2}{2}} - 4I_1 + 2 = 0$$

$$4I_1 + \frac{3I_2}{2} = 2$$

$$8I_1 + 3I_2 = 4$$

$$I_1 + I_2 = 5 \times 8$$

$$-8I_1 + 8I_2 = 40$$

$$\begin{array}{r} 8I_1 + 3I_2 = 4 \\ -8I_1 + 8I_2 = 40 \\ \hline 11I_2 = 44 \end{array}$$

$$11I_2 = 44$$

$$I_2 = \frac{44}{11} = 4A$$

$$I_2 - 5 = I_1$$

$$\frac{44}{11} - 5 = I_1$$

$$\frac{44}{11} - 5 = I_1 = -2.06A$$

$$I_3 = I_2 + \frac{88}{15}$$

$$\frac{88}{15} = \frac{9.3}{15} = 6.2 \text{ A}$$



Voltage across 3Ω resistor

$$3(I_2 - I_3)$$

$$3(6.2 - 2.93)$$



$$3 \times 3.27 = 9.81 \text{ V}$$

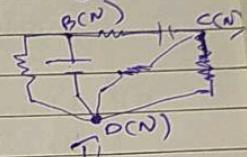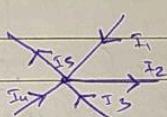② KCL - The algebraic sum of all the currents meeting at a point or junction will be zero.



$$\sum I = 0 = I_1 - I_2 + I_3 + I_4 - I_5 = 0$$

→ Junction (J) and a node (N)

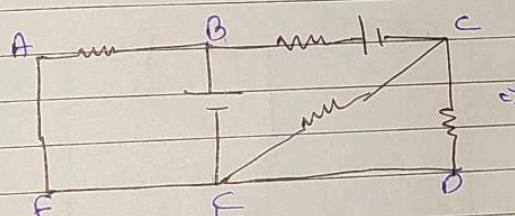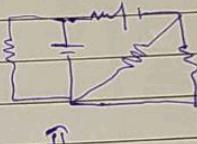

Junction → is a point in circuit where 3 or more branches combine (current must divide)


Node → where two or more branches combine (current may or may not divide)

→ Steps for solving numericals using nodal analysis-


- i) Identify the principle nodes or junctions present in the network.
- ii) Assign a junction potential on each junction w.r.t the assigned reference junction having high value  $V_o = 0V$ .
- iii) Assuming all the currents in outgoing direction from each junction form KCL equations.
- iv) Solve the equations to calculate the value of junction potentials.
- v) Using individual junction potentials find the value of required electrical quantity.

→ Variety of Numericals-

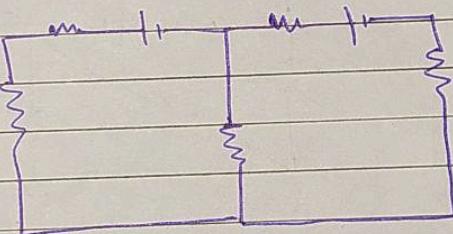
- i) Type-1  
only contain  
resistance  
and voltage  
source





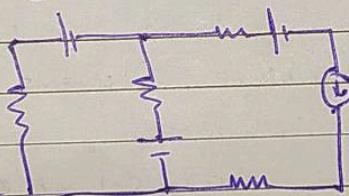
- 2) Type-2  
also contain  
current source



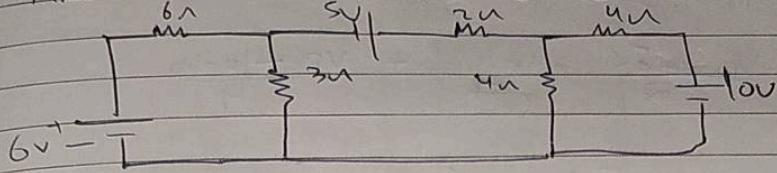Q1) Find the current in  $3\Omega$  resistor using KCL



Q2-

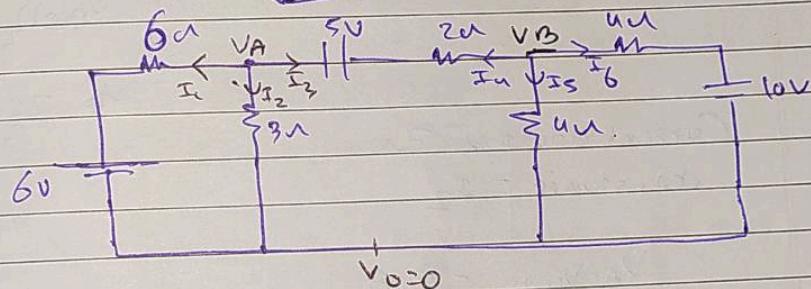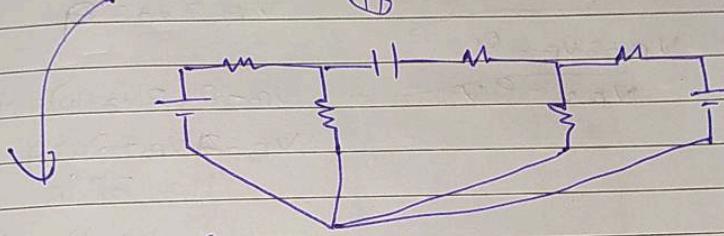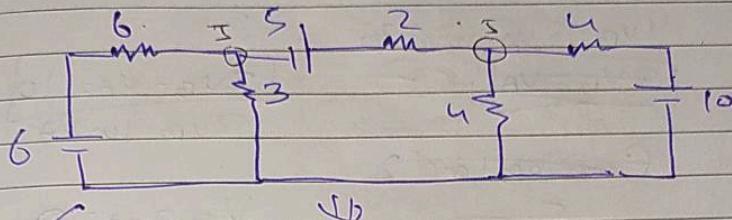

$$I_1 = \frac{V_A - V_o - 6}{6} \quad (\text{Not doing like this.)}$$

Form a eqn in systematic way

Applying KCL at junction A

$$\frac{V_A - V_o - 6}{6} + \frac{V_A - V_o}{3} + \frac{V_A - V_B + 5}{2} = 0$$

$$\frac{V_A - V_o - 6}{6} + \frac{2V_A - 2V_o + 3V_B - 3V_B + 9}{6} = 0$$

$$6V_A - 3V_o - 3V_B + 9 = 0$$

$$6V_A - 3V_B + 9 = 0 \Rightarrow 2V_A - V_B = -$$

Applying KCL at junct B

$$\frac{V_B - V_A + S}{2} + \frac{V_B - V_0}{4} + \frac{V_B - 10 - V_0}{4}$$

$$2V_B - 2V_A + S + V_B - V_0 + V_B - V_0 - 10 = 0$$

$$\frac{4V_B - 2V_A - 2V_0 - 10}{2} \\ \boxed{2V_B = V_A} \quad (1)$$

$$\frac{2V_B - V_A = 10}{2V_B - 10 = V_A} \quad (2)$$

From eqn 1 and 2

$$V_B - 2V_A = 9 \\ V_B = -9V_A$$

$$V_B - 2V_A = 9$$

$$V_B - 2(2V_B - 10) = 9$$

$$V_B - 4V_B + 20 = 9$$

$$11 = 3V_B$$

$$V_B = \frac{11}{3} = 3.66$$

$$V_A = \frac{22}{3} - 10$$




$$= \frac{-8}{3} = -2.66$$

Current across  $Z_1$

resistance  $= I_2$

$$\frac{V_A - V_0}{2} = -\frac{8}{9} A$$

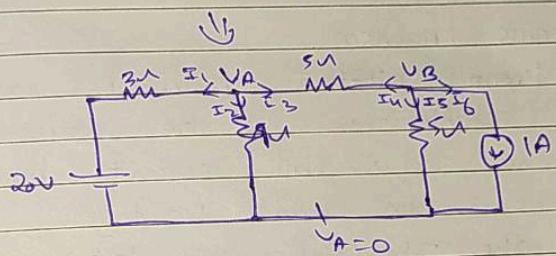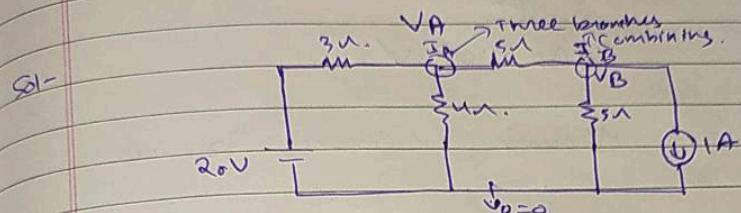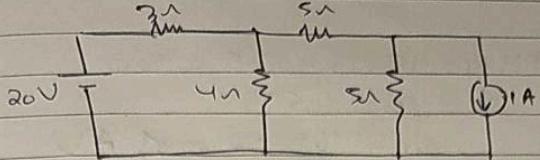Q32) Using nodal analysis find the current in  $4\Omega$  branch.



There are two junctions  
Applying KCL at Junction A

$$\frac{VA - VO - VD}{3} + \frac{VA - VO}{4} + \frac{VA - VB}{5} = 0$$

~~$$5VA - 100 - 3VA + 3VA - 3VB = 0$$~~

~~$$+ 8VA - 11VA$$~~

$$\frac{20VA - 400 + 15VA + 12VA - 12VB}{60} = 0$$

$$47VA - 12VB = 400 \quad \textcircled{1}$$

Applying KCL at Junction B

$$\frac{VB - VA}{5} + \frac{VB - VO}{5} + 1 = 0$$

$$2VB - VA + 5 = 0 \quad \textcircled{2}$$



REDMI NOTE 8  
AI QUAD CAMERA

from eq 1 and 2

$$12(V_A + 5) - 12V_B = 400$$

$$14V_B - 12V_B + 120 = 400$$

$$8V_B = 160$$

$$V_B = \frac{160}{8} = 20 \text{ V}$$

$$V_A = 9.02 \text{ V}$$

$$\text{Current through } 4\Omega \text{ branch} = I_2 = \frac{V_A - V_B}{4}$$


$$= \frac{9.02}{4}$$

$$= 2.25 \text{ A}$$

#
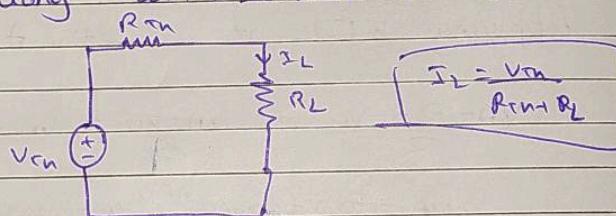
### Thevenin's Theorem

Any linear bilateral network irrespective of its complexities can be reduced into a Thevenin's equivalent circuit having the Thevenin's open circuit voltage 'V<sub>th</sub>' in series with the Thevenin's equivalent resistance R<sub>th</sub> along with Load Resistor R<sub>L</sub>




31

→ Steps for solving


- 1) Identify the Load resistor  $R_L$
- 2) Remove the Load resistor and calculate the open circuit potential across two open ends. This will be Thevenin's equivalent voltage  $V_{TH}$ .
- 3) Again remove the load resistor and replace all the active sources by their internal resistances.
- 4) Calculate the equivalent resistance across the open ends. This will be Thevenin's equivalent resistance  $R_{TH}$ .
- 5) Draw the Thevenin's equivalent for given circuit
- 6) Calculate the load current  $I_L$  by using the identity. 
$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

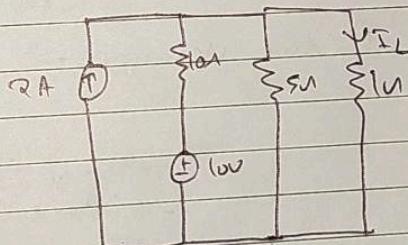- Q1) Find the current through  $1\Omega$  resistor in the given circuit using Thevenin's theorem-



sol-  $R_L = 1 \Omega$ . (Step 1)

Step-2 Removing  $R_L$ .

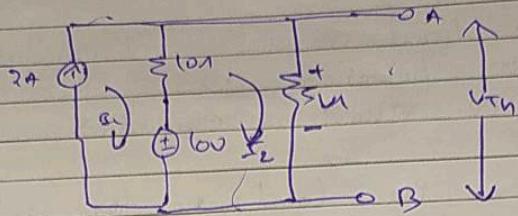

Mesh 1 :

$$I_1 = 2A$$

$$+10 - 10(I_2 - I_1) - 5I_2 = 0$$

$$10 - 10(I_2 - 2) - 5I_2 = 0$$

$$10 + 20 = 15I_2$$

$$I_2 = 2A$$

Voltage across  $\text{RL}$  is  $V_{RL} = 10V$

$$V_{TH} = 10V$$


Step-3)  
and 4

A (Active resources  $\rightarrow$  Voltage and current source)

internal resistance  $0\Omega$   
replaced with short circuit branch  
internal  $\rightarrow$  replaced by  
resistor open circuit  
branch.



REDMI NOTE 8  
AI QUAD CAMERA

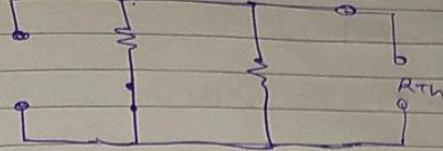


$$R_{Th} = 10\,115$$

$$R_{RH} = \frac{10+5}{10+5} = \frac{15}{15} = \frac{10}{3} = 3.33\text{A}$$

$$\text{R}_{\text{ch}} = 333 \mu$$


## Step-5

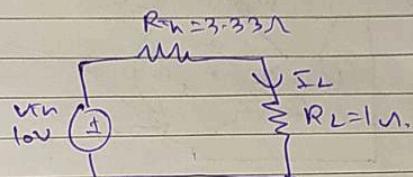

$$I_L = \frac{V_{TH}}{R_{CH} + R_L}$$



$$I_L = \frac{16}{3.33+1} = \frac{16}{4.33} \text{ Ans}$$

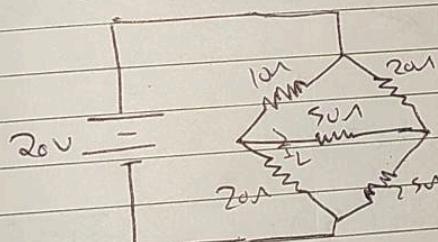Q-2) Find the current through  $5\Omega$  resistor using the vinins Thevenin.



Sol -  $R_L = 5\Omega$  (Step 1)

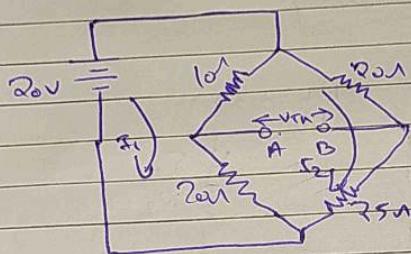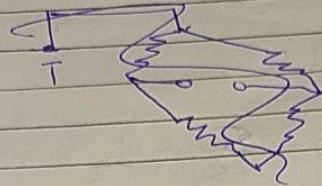Step (2) Remove  $R_2$  calculate  $V_{th}$ .



$$\begin{aligned} 20 - 10I_1 - 20I_2 &= 0 \\ \frac{20}{30} = I_1 &= 0.667A \\ -20I_2 - 20I_1 - 20(\frac{I_2}{2} - I_1) - 10(I_2 - I_1) &= 0 \\ -75I_2 + 30I_1 &= 0 \\ \frac{-75}{2} I_2 + \frac{30}{2} I_1 &= 0 \end{aligned}$$

$$IR \quad \sum I_2 - I_2 = \frac{2}{3}$$

$$\begin{aligned} I_2(\frac{3}{2}) &= \frac{2}{3} \\ I_2 &= \frac{4}{9}A \\ &= 0.444A \end{aligned}$$

$$\begin{aligned} I_1 &= \frac{5}{9}A \\ I_1 &= \frac{10}{9}A \\ &= 1.111A \end{aligned}$$


Assuming  $A \rightarrow V_{TH} \rightarrow B$

$$+10(I_1 - I_2) = 20I_2 + V_{TH} = 0$$





$$+10(11 - 0.44) = 20(0.44) + V_{TH} = 0$$

$$+10(0.06) = 8.88 + V_{TH} = 0$$

$$V_{TH} = 2.22V$$

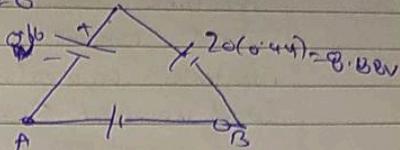

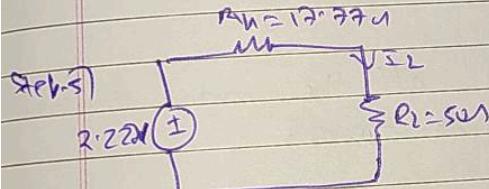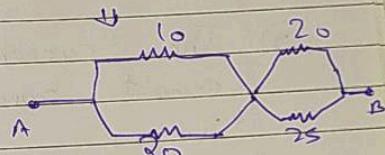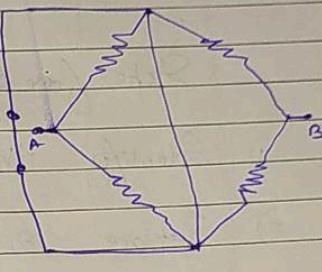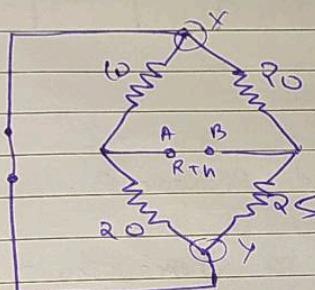Step 4 Again removing  $R_L$  and replacing all the active sources by their internal resistances.



$$R_{TH} = \frac{10 \times 20 + 20 \times 25}{45} = 45\Omega$$

$$R_{TH} = \frac{2 \cdot 2 + 100}{60 + 100} = \frac{100}{160} = \frac{5}{8}\Omega$$

$$R_{TH} = \frac{160}{9} = 17.77\Omega$$


$$I_L = \frac{2.22}{17.77} = \frac{V_{TH}}{R_{TH} + R_L}$$

$$(I_L = 0.12A)$$



REDMI NOTE 8  
AI QUAD CAMERA
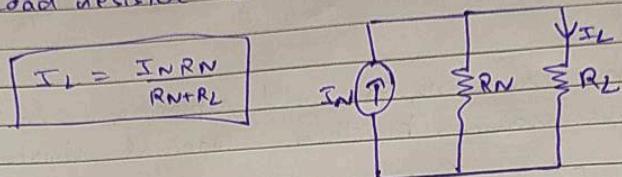
# Norton's Theorem:  
 Any linear bilateral network irrespective of its complexities can be reduced into a Norton's equivalent circuit having a Norton's short circuit current 'In' in parallel with Norton's equivalent resistance  $R_N$  in parallel with Load resistor  $R_L$ .




Steps for solving


- 1) Identify the Load Resistor  $R_L$ .
- 2) Replace  $R_L$  with a short circuit Branch.
- 3) The current flowing through this short circuit branch will be the Norton's current 'In'.
- 4) Remove  $R_L$  and replace all the active sources by their internal resistances.
- 5) The equivalent resistance across the two openends will be the Norton's resistance  $R_N$ .
- 6) Draw the Norton's equivalent circuit.
- 7) Calculate  $I_L$  by  $I_L = R_N I_N / (R_N + R_L)$



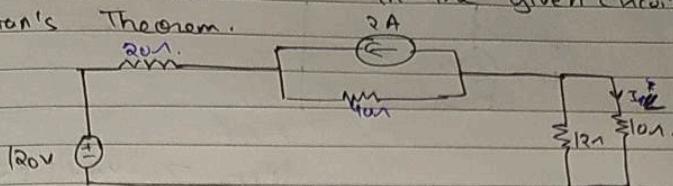Q1) Find the current  $I$  in the given circuit by  
Newton's Theorem.



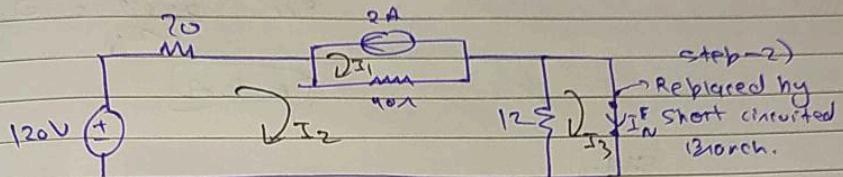Sol →  $10\Omega \rightarrow RL$  (Load resistance) step 1



$$I_1 = -2A \text{ (Mesh 1)}$$

Applying KVL in Mesh 2.

$$-72I_2 + 40I_1 + 12I_3 = -120$$

$$12I_3 - 72I_2 = -40 \quad \text{---(1)}$$

Step 3

Applying KVL in Mesh 3

$$12(I_3 - I_2) = 0$$


$$I_3 = I_2 \quad \text{---(2)}$$

$$+60I_2 = +40$$

$$I_2 = \frac{2}{3} = 0.66A = I_3$$

$$I_B = I_2 = 0.66A$$

Step 4)

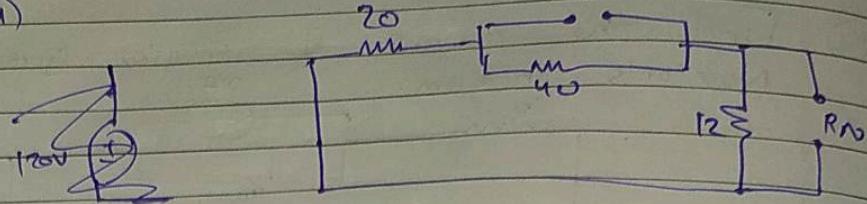


$$R_N = 20 + 40 = 60 \Omega$$

$$\frac{60 \times 12}{60 + 12}$$

$$R_N = \frac{60 \times 12}{72} = 10 \Omega$$

$$(R_N = 10 \Omega)$$

Step 5)

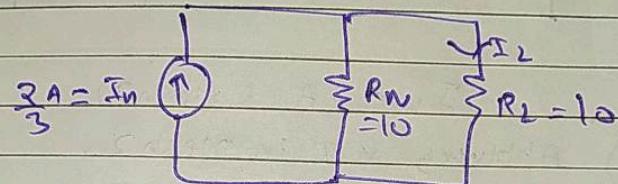


$$I_L = I_N \frac{R_N}{R_N + R_L}$$


$$\frac{10}{3} \times \frac{10}{20}$$

$$= 0.33 A$$

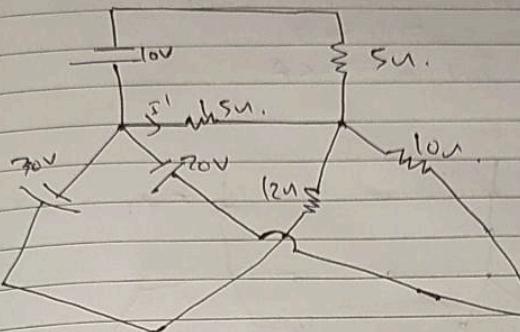Find the current  $I_1$  in the given circuit using  
Norton's Theorem.



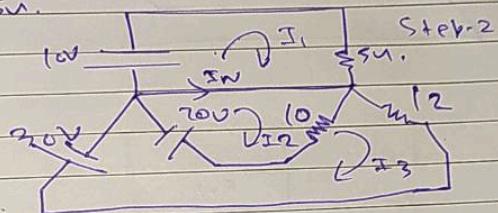Sol - Step 1  $R_L = 1 \text{ m} \Omega$ .



Applying KVL in mesh 1

$$-5I_1 = +10 \\ I_1 = -2A$$

Applying KVL in mesh 2

$$-10I_2 + 10I_3 - 20 = 0$$

$$10(I_3 - I_2) - 20 \\ I_3 - I_2 = 2 \quad \text{---(1)}$$

Applying KVL in mesh 3

$$-20I_3 + 10I_2 - 30 + 20 = 0$$

$$-20I_3 + 10I_2 = 10$$

$$-20I_3 + 10(I_3 - 2) = 10 \Rightarrow -10I_3 = 10 \Rightarrow I_3 = -1A$$

$$I_2 = 4.5A$$



$$I_N = I_2 - I_1$$

$$I_N = I_2 - I_1 \quad (\text{Gmp})$$

$$= -4.5 \text{ A}$$

$$I_N = -2.5 \text{ A}$$

Step-4)

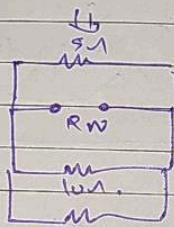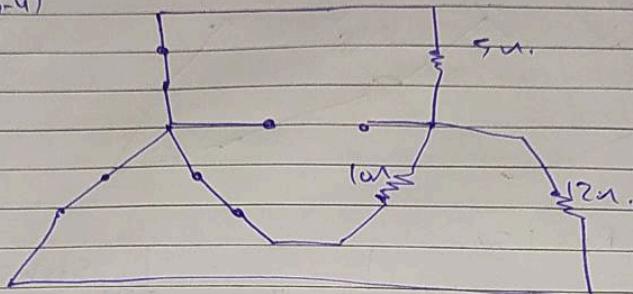


12 ohm

Step-5

$$R_N = \frac{1}{\frac{1}{4} + \frac{1}{10} + \frac{1}{12}}$$

$$R_N = \frac{1}{\frac{12+6+5}{60}} = \frac{60}{23} = 2.6 \Omega$$

Step-6)

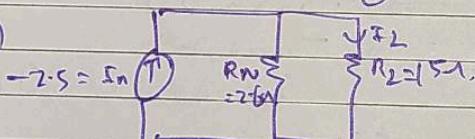

$$I_L = I_N R_N = -2.5 \frac{2.6}{2.6 + 12}$$

$$= -0.37 \text{ A}$$


## # Superposition Theorem

In any linear, bilateral multisource networks, the current or voltage across any branch can be calculated by taking the algebraic sum of values calculated by taking one source at a time and replacing the other active sources by their internal resistances.

→ Steps for solving

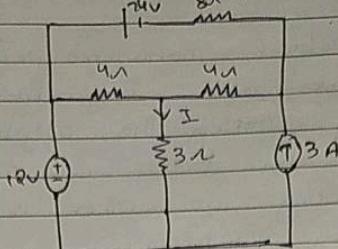
- 1) Identify the branch and quantity to be calculated along with the presence of more than 1 active source.
- 2) Consider any 1 active source and replace the remaining by their internal resistances.
- 3) Calculate the required electrical quantity for that particular source.
- 4) Repeat last two steps for all the active sources.
- 5) Algebraic sum of all these individual values will be the final value of all the required electrical quantity working together.

Q> Find  $I$ , using Superposition Theorem.



Sol: There are 3 active sources in the given network.

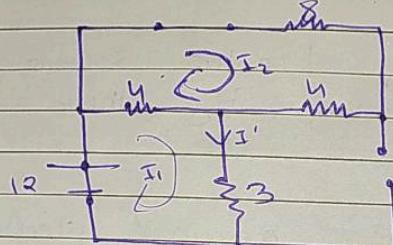→ Taking 12V source and replacing other A.S by their internal resistances.



Applying KVL in Mesh 1

$$-7I_1 + 12 + 4I_2 = 0$$
$$-7I_1 + 4I_2 = -12 \quad \text{---(1)}$$

KVL in mesh 2


$$-6I_2 + 4I_1 = 0$$
$$I_1 = 4I_2 \quad \text{---(2)}$$

From eq 1 and 2

$$I_2 = 0.5 \text{ A} \quad I_1 = 2 \text{ A}$$

$$\boxed{I'_{R_N} = 2 A}$$

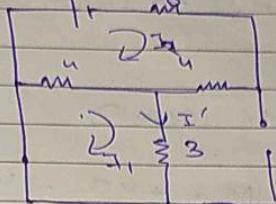→ Taking 24 V source and replacing other active sources by their internal resistances.



KVL in Mesh 1

$$-3I_1 + 4I_2 = 0 \quad \textcircled{1}$$

KVL in Mesh 2

$$-74 - 16I_2 + 4I_1 = 0$$

$$4I_1 - 16I_2 = 74$$

$$I_1 - 4I_2 = 6 \quad \textcircled{2}$$


$$-6I_1 = 6$$

$$I_1 = -1 A$$

$$I_2 = \frac{-7}{4} A = -1.75 A$$

$$\boxed{I'_{R_N} = -1 A = I_1}$$

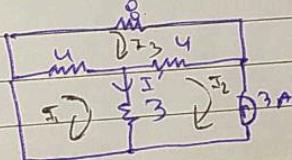→ Taking 3A Source and replacing other active sources by their internal resistances.



REDMI NOTE 8  
AI QUAD CAMERA

$$I_2 = -3A$$

KVL in mesh 1

$$\begin{aligned} -7I_1 + 3I_2 + 4I_3 &= 0 \\ -7I_1 + 4I_3 &= 9 \quad \text{--- (1)} \end{aligned}$$

KVL in Mesh 2

$$\begin{aligned} -16I_3 + 4I_2 + 4I_1 &= 0 \\ -4I_3 + I_2 + I_1 &= 0 \\ I_1 - 4I_3 &= 3 \quad \text{--- (2)} \end{aligned}$$

$$-6I_1 = 12$$

$$I_1 = -2A$$

$$I_3 = -\frac{5}{4} = -1.25A$$

$$I'_{3A} = I_1 - I_2$$


$$I'_{30} = -2 + 3 = 1A$$

$$\begin{aligned} I_T &= I'_1 + I'_2 + I'_3 \\ &= 2 - 1 + 1 \\ &= 2A \end{aligned}$$

for high efficiency  ~~$R_{\text{load}} < R_{\text{internal}}$~~   
for max power transfer  $R_{\text{load}} = R_{\text{internal}}$
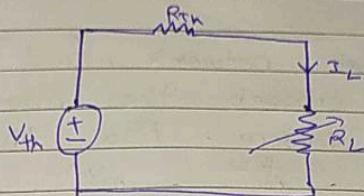
## # Maximum Power Transfer Theorem

The condition for maximum power flow through Load resistor  $R_L$  can be achieved when the Load resistor equals the Thevinin's equivalent resistance of the circuit.



Power through  $R_L$

$$P = I_L^2 R_L \rightarrow \textcircled{1}$$

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$P = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L \rightarrow \textcircled{2}$$

Diffr. wrt  $R_L$

$$\frac{dP}{dR_L} = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 + 2R_L \left( \frac{V_{th}}{R_{th} + R_L} \right) \cdot 0 - V_{th} \cdot \frac{0 - V_{th}}{(R_{th} + R_L)^2} = 0$$

$$1 + 2 \frac{R_L}{R_{th} + R_L} = 0$$

$$\frac{R_{th} + R_L - R_{th}}{R_{th} + R_L} = 0 \rightarrow \boxed{R_{th} = R_L} \rightarrow \textcircled{3}$$


This is the required condition for max power flow

Putting the value of  $R_L = R_{Th}$  in eq. 2


$$P_{Max} = \frac{V_{Th}^2}{4R_{Th}} \times 19W.$$

$$P_{Max} = \frac{V_{Th}^2}{4R_{Th}}$$

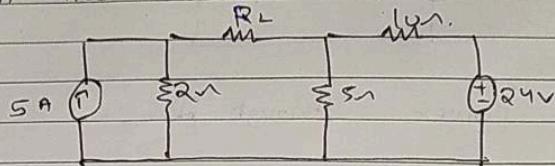- Q) In the given network, find the value of  $R_L$  which will absorb the maximum power from the source. Also the maximum power.




Sol-

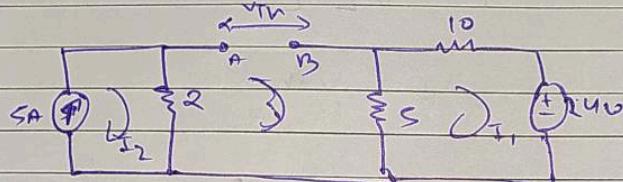

$$I_2 = SA$$

$$-15I_1 = 24$$

$$I_1 = \frac{-24}{15} = -1.6A$$

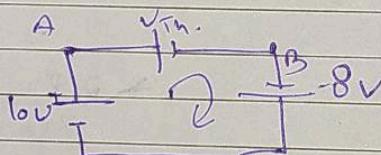


$$-8 + 10 = V_{Th} = 2V$$


$$V_{Th} = 2V$$



REDMI NOTE 8  
AI QUAD CAMERA

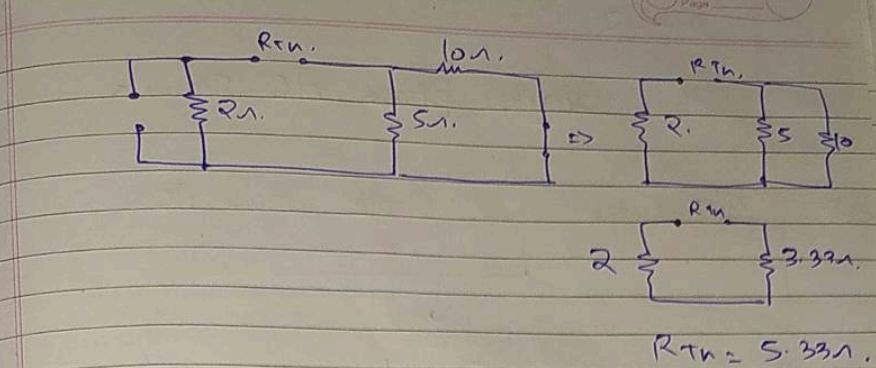

Ans.  $R_L = R_{Th} = 5.33\Omega$

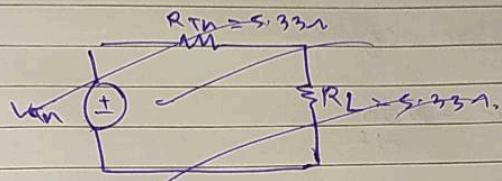

$$P_{max} = \frac{V_m^2}{4R_{Th}}$$

$$= \frac{Q}{4(5.33)}$$

Ans.  $P_{max} = 0.187W$